

Welcome!

# CSSE2010/CSSE7201

## Learning Lab 3

# Binary Arithmetic✓

<http://responsewaresg.net>

**Session ID: CSSE2010EXT**

School of Information Technology and Electrical Engineering  
The University of Queensland

# Learning Lab 3

## Binary Arithmetic

---

- Binary arithmetic revision✓
- Circuits which do arithmetic✓
- IN students – use Logic Ics or Logisim
- EX students – use Logisim✓

# What is -16 (base 10) expressed in 8-bit two's complement format?

6% **A.** 10010000

13% **B.** 11101111

16% **C.** 10010001

65% ✓ **D.** 11110000 ✓

0% **E.** I don't know

Method 1:

	-128	64	32	16	8	4	2	1
-16:	1	1	1	1	0	0	0	0
	-128	-64	-32	-16				

Method 2:

16:	0	0	0	1	0	0	0	0
-16	1	1	1	0	1	1	1	1

+

1	1	1	1	0	0	0	0	0
---	---	---	---	---	---	---	---	---

✓

# What is the result of adding the 6-bit two's complement numbers 001110 and 110100?

39% A. 000010 with overflow

52% B. 000010 with no overflow

6% C. 000110 with overflow

0% D. 000110 with no overflow

0% E. 001100 with overflow

0% F. 001100 with no overflow

0% G. 111110 with overflow

3% H. 111110 with no overflow

0% I. I don't know

-32 to 31: 31 + 0 → 31

-32 to → -32

+ve + -ve } no overflow  
-ve + +ve }

$$\begin{array}{r}
 \text{Cin of MSB} \\
 \text{Cout of MSB} \\
 \begin{array}{r}
 001110 \\
 + 110100 \\
 \hline
 000010
 \end{array}
 \end{array}$$

A	B	Σ
0	0	0
0	1	1
1	0	1
1	1	0

at MSB, Cin ≠ Cout  
→ overflow has occurred

Cin ⊕ Cout = 0 → no overflow  
= 1 → overflow

Which of the following operations will result in an overflow in 4-bit two's complement arithmetic? ✓

46% **A. 0100 + 0101** (add overflow)

19% **B. 0100 - 0101** +ve -ve  
+ve + -ve → cannot overflow

5% **C. 1001 - 0001** -ve - +ve  
-ve + -ve → could overflow

3% **D. 1001 + 0001** -ve + +ve → cannot overflow

27% **E. None of the above**

0% **F. I don't know**

$$\begin{array}{r} 0100 \text{ +ve} \\ + 0101 \text{ +ve} \\ \hline \rightarrow 1001 \text{ -ve} \end{array}$$


Cin MSB = 1

Cout MSB = 0

1 ≠ 0 → overflow has occurred



$$\begin{array}{r} 0100 \\ - 0101 \\ \hline 0000 \\ + 1010 \\ \hline 1111 \end{array}$$

# 1-bit Full Adder (from lecture)

 

- Draw a circuit schematic diagram for a circuit which implements a full adder
  - Use switches for the 3 inputs ✓ and LEDs for the 2 outputs ✓
- Have it checked by a tutor ✓
- Build it or simulate it *LogicSim*
- Test it systematically


# Circuit schematic

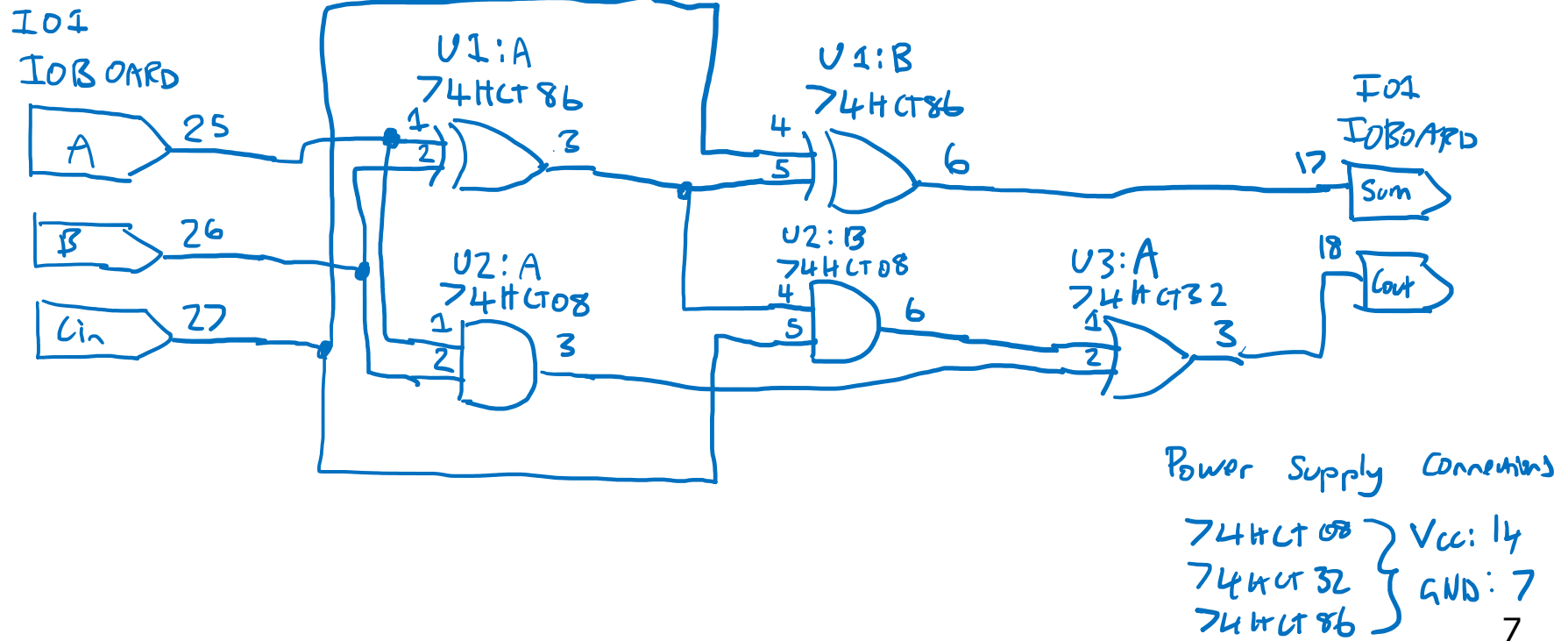 

$$\bar{A}_3 \bar{B}_3 S_3 + A_3 B_3 \bar{S}_3 = 1 \rightarrow \text{overflow}$$
 
# 4-bit adder: 74HCT283 ✓

- 74HCT283 = Single chip 4-bit adder
- Draw a circuit schematic that uses this chip ✓  
to add two 4-bit numbers (on switches) ✓ and  
shows the result (4-bit output and carry out) ✓  
on LEDs. Connect the carry-in to a push button ✓
  - Use the symbol shown here
    - See details on Blackboard ✓
    - Don't forget power supply connections (16 pin chip) ✓
- Have the schematic checked by a tutor
- Wire up and test the circuit or simulate the circuit
  - Try some unsigned and two's complement test cases ✓
    - Are the results as you expect?
- Extension – add a 2's complement overflow detector circuit with LED output ✓



**EX students: use Logisim adder block with gates as required to simulate**