

CSSE2010/CSSE7201

Lecture 5 ✓

Flip-flops

School of Information Technology and Electrical Engineering
The University of Queensland

Today

- Admin
- Recap from week 2
- Circuits that remember values
 - Flip-flops
 - Latches

Admin


- Weekly quizzes:
 - ✓ ■ Quiz 1 – closed – 414 attempts, 15.1/17 average, 17/17 median
 - ✓ ■ Quiz 2 – open now and due Friday 13-Aug 4pm AEST
- Labs:
 - ✓ ■ **IN students** – use Logisim to simulate logic circuits and also construct on breadboard if you have borrowed a kit
 - **EX students** – use Logisim to simulate the logic circuits. Start acquiring your Arduino based hardware items required from week 7. Details on Blackboard

Prac Equipment - IN students


- ✓ ● Treat it carefully
- ✓ ● Report damage / missing parts
- Don't use parts you're not familiar with and wait until we get into the relevant prac activity.
- ✓ ● Pay extra attention to the I/O board USB connector when you are using it
- ✓ ● Switch the power off before you build/change circuits
 - Check your wiring before you apply power

Recap from Last Week


4-bit Ripple carry adder

 


4-bit Adder/subtractor

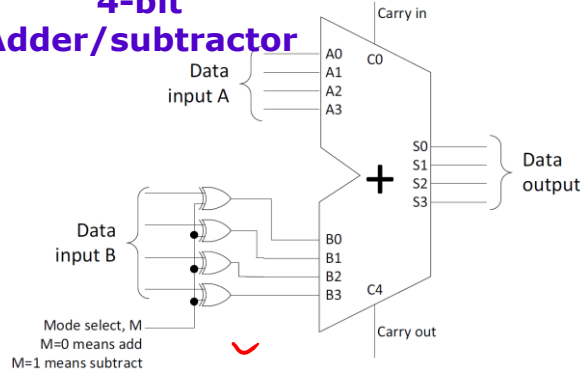

4:1 MUX

 

3:8 Decoder

 

Combinational Logic Circuits – Adder, Adder/subtractor, Multiplexer, Decoder




Logic Gates – NOT, AND, OR, NAND, NOR, XOR, XNOR and Boolean algebra



Binary representations – unsigned, sign-mag, 1's comp, 2's comp, excess- 2^{N-1}



Recap from Last Week (cont...)

 

Practical application of the 3-input majority function $X=AB+BC+AC$

When a majority of tanks is low the output will be driven high indicating low-level of water

  Timing diagrams to represent logic circuits




$$X = A(B + C) = AB + AC$$

Clicker Question

 4:1

Consider the multiplexer shown.
What must the inputs A,B,C,D be
so that the multiplexer output is

$$X = S_1 \cdot S_0 + \overline{S_1} \cdot G$$



$S_1 S_0$
~~0 0~~
~~0 1~~
~~1 0~~
~~1 1~~

$A \rightarrow 0 + 1 \cdot G = G$
 $B \rightarrow 0 + 1 \cdot G = G$
 $C \rightarrow 0 + 0 = 0$
 $D \rightarrow 1 + ? = 1$

- 6% A=0, B=0, C=0, D=1
- 50% A=G, B=G, C=0, D=1
- 12% A=G, B=0, C=0, D=1
- 6% A=0, B=G, C=0, D=1
- 5% None of the above
- 24% I don't know

0

Circuits that remember values

- The output of any logic gate or **combinational circuit** is dependent on the **current value of inputs only**
- If an input changes, the output can also change and the previous value is lost forever
- **Sequential circuits**: the current output depends not only on the current inputs but also on the past outputs.
- Circuits with **memory** can remember values, even if the input changes





0
1
2
3
4
5
7

→



Memory element: D Flip Flop

- **D** is input ✓
- **Q** is output ✓
- **CLK** (clock) is control input
- How does it work?

    - Q copies the value of D (and remembers it) whenever CLK goes from 0 to 1 (rising edge)



D Flip Flop

  

+ve edge triggered
D FF

- Remember: Q changes ONLY when clock (CLK) goes from 0 to 1

Characteristic Tables

- **Characteristic table** defines operation of flip-flop in tabular form

- D flip-flop

D	Q(t+1)
0	0
1	1

Input

Reset



Set

What the output will be on the next clock edge (i.e., CLK goes from 0 to 1).

+ve edge.



CSSE2010

 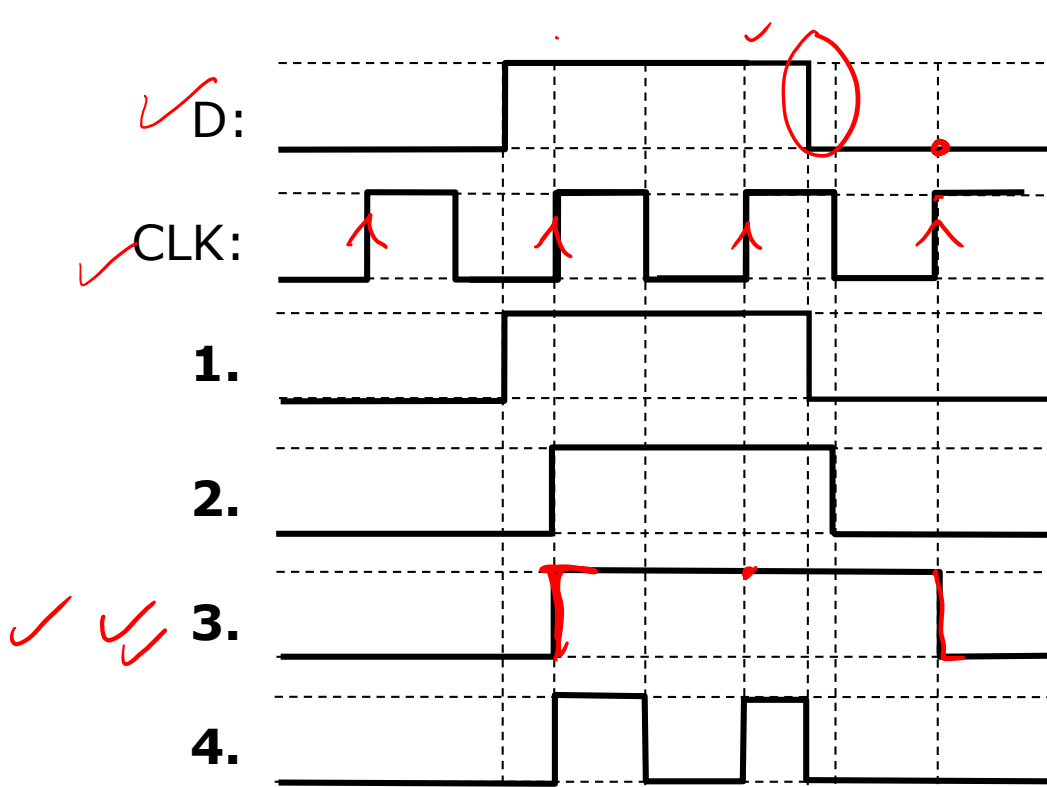Using the D flip-flop presented previously, what is the output waveform for Q?




D Flip-flops

- Summary: D flip-flop remembers either a "1" or "0" – i.e. a single bit. That is the flip-flop remembers the value till the next clock edge, upon which the D input is transferred to output Q.
- So to remember n bits, you will need n D flip-flops
- ✓ Definition: A n -bit **register** can be made using n D flip-flops
- There are other types of flip-flops, e.g.
 - JK flip-flops
 - T flip-flops
- Flip-flops can be made out of logic gates

  


Short Break

- Stand up and stretch

 

SR Latch – to be completed in class

 Try to complete this at home before the lecture. You can assume an initial value for Q output or treat it generic as Q and work out the rest for different combinations of inputs S and R



Remember, this is what a NOR gate does

Active high

S	R	Q	\bar{Q}
0	0	Q_{n-1}	\bar{Q}_{n-1}
0	1	0	1
1	0	1	0
1	1	0	0

← REMEMBER (STORE) ✓

← RESET ✓

← SET ✓


← not valid ✗

Useful states (operation)
 { set
 reset
 storage }

A	B	NOR
0	0	1
0	<u>1</u>	0
<u>1</u>	0	0
1	1	0

Latches from NAND gates

 Homework: Analyse the S-R latch circuit in the previous slide when NOR gates are replaced with NAND gates and complete the truth table.




active low


HW

Flip-Flops vs Latches


- **Latches** are **level triggered** devices – i.e. able to latch the output and respond to changes of logic levels on the inputs
- Latch circuits can be modified such that they become sensitive to an **edge** (i.e. **momentary transitions**) of a control input (i.e. a clock signal)
- Such circuits are called “**flip flops**” and a flip flop can **store 1 bit of information while being sensitive to a clock edge** (i.e., flip flop will change its output only at the clock edges, based on the inputs)
- **Latches are level triggered** devices while **flip flops are edge triggered** devices
- A clock signal has two edges
 - Positive edge – 0 to 1 transition
 - Negative edge – 1 to 0 transition
- There are different types of flip flops
 - **D flip flop – we will only discuss this**
 - JK flip flop – not covered in this course
 - T flip flop – not covered in this course
- So, a D flip flop can be positive edge triggered or negative edge triggered
- **Positive edge triggered D flip flop → Input D is copied to output Q at the positive edge of the clock. In between the clock edges, flip flop is not responsive, thus stores the value.**

 


A Real D Flip-flop

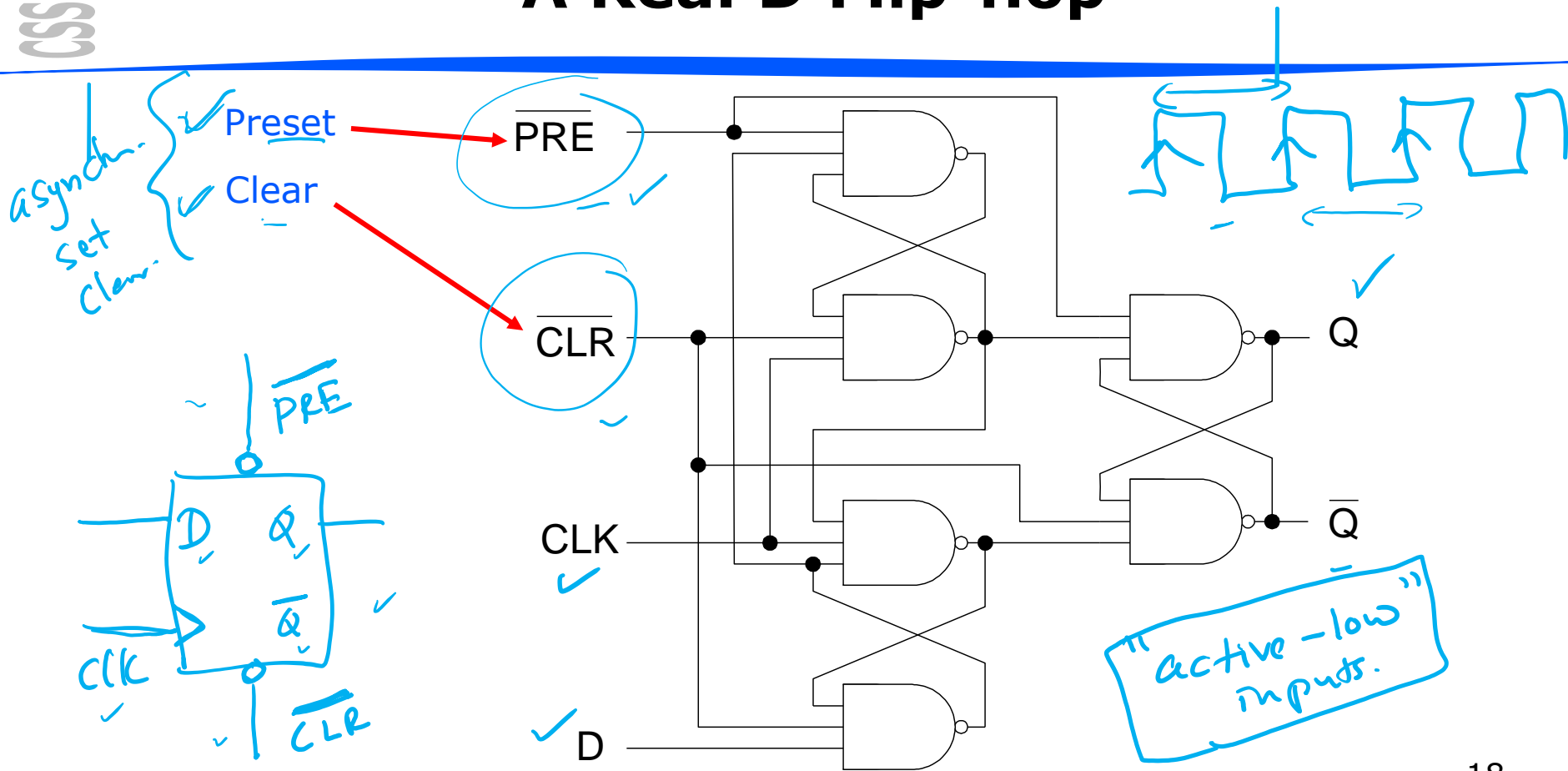

D Latches and Flip-flops – Symbols Used

 

 
- Triangle indicates edge-triggered (therefore flip-flop)
 - (c) sensitive to rising edge of clock
 - (d) to falling edge
- **State** of a flip-flop is the value stored
- Flip-flops more useful than latches




D Flip-flop Chips

- (a) 74HCT74 chip (Dual D flip-flop)
- (b) 74HCT273 chip (Eight D flip-flops)
 - can hold one byte of information (8 bits).

See device symbols PDF on Blackboard

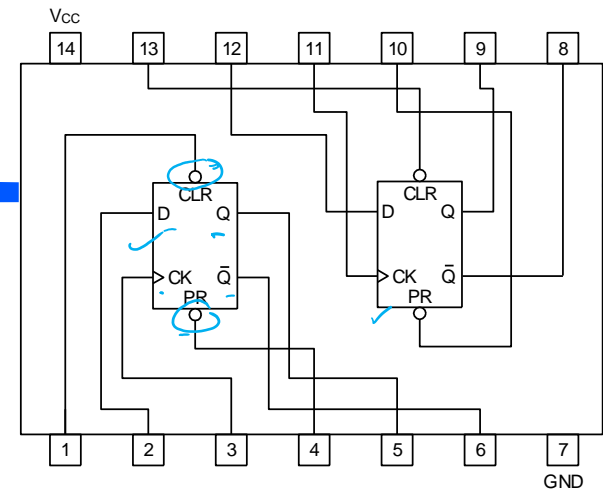

(a)

 


(b)

Combinational vs. Sequential Circuits

Combinational Circuits (last week)

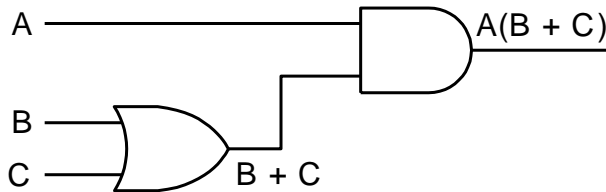- Logic gates only (no flip-flops)
- Output is uniquely determined by the inputs
 - i.e. you'll always get the same output for a given set of inputs
- Example from previously:



Adders
Multiplexers
Decoders
Demultiplexers
Encoders

Sequential Circuits


- Include flip-flops
- Output determined by current inputs and current **state** (values in the flip-flops)
- Output can only change when clock 'ticks'

Counters

Registers

Sequential Circuits

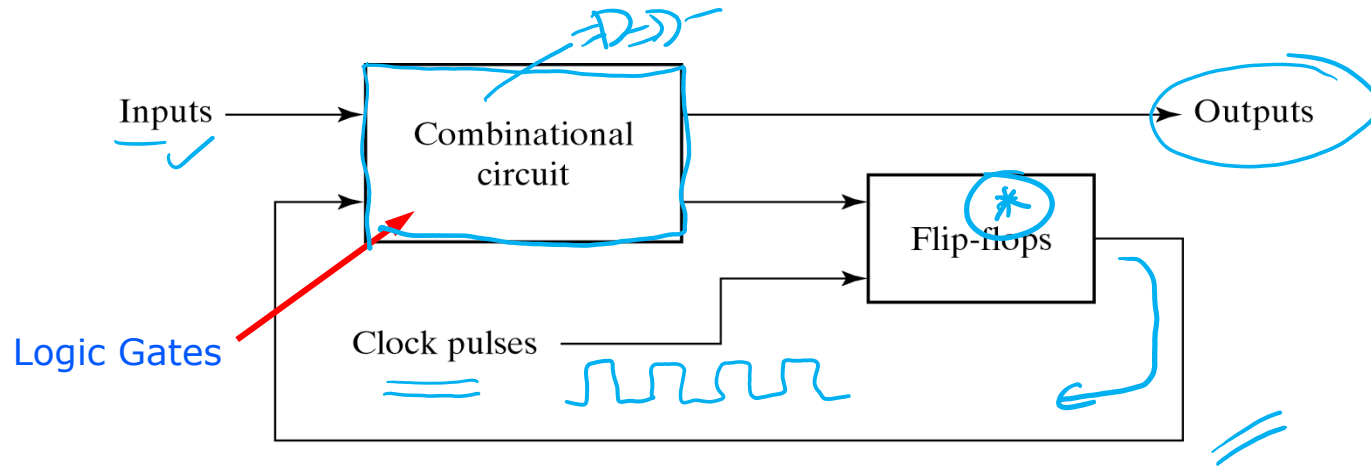- **State** = value stored in flip-flops
- Output depends on input and state
- Next state depends on inputs and state




Synchronous Sequential Circuit

- Storage elements (flip-flops) can only change at discrete instants of time

- Assume

- We have a clock signal:

 



Synchronous

Asynchronous

- Output of storage elements change only on the edges of control signal
 - (compare with logic gates whose output changes whenever the input changes)

Registers

 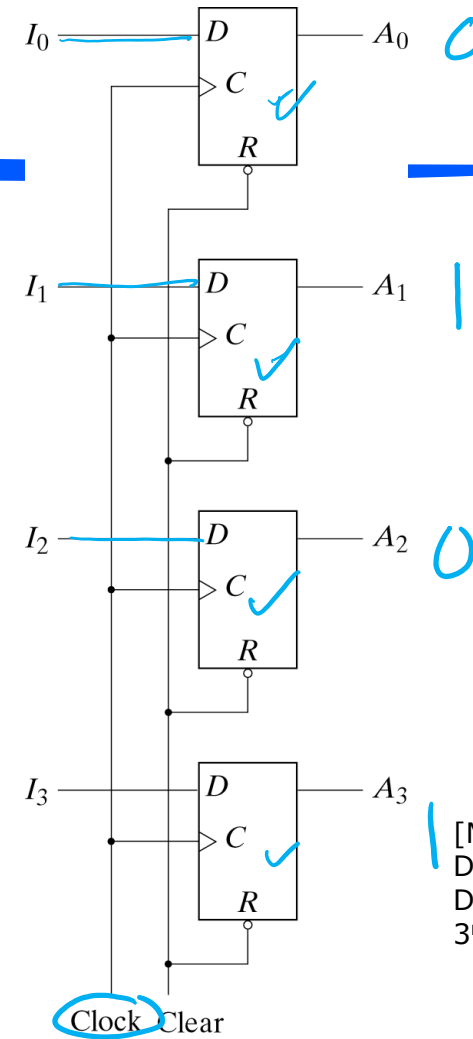- A **register** is a group of flip-flops
 - n -bit register consists of n flip-flops capable of storing n bits
- Example
 - 4-bit register
- A register is a sequential circuit *without* any combinational logic



[Mano,
Digital
Design,
3rd ed.]

Coming up...

✓ ● Quiz 2 – due Friday 4pm this week

● Lab 4

■ Combinational Logic

✓ ■ Make sure you attempt the preparation task

■ Use logic ICs or Logisim software to test your circuits

● Lab 5

✓ ■ Flip-flops

■ Use Logisim software to test the circuits