

CSSE2010/CSSE7201

Lecture 9

From Digital Logic to Processors - ALU

School of Information Technology and Electrical Engineering
The University of Queensland

Outline

- Recap of what's covered so far
- Part of a CPU – mainly ALU

What We've Covered So Far

Binary number representation

- Unsigned/signed
- Two's complement
- Binary addition

Combinational logic circuits

- Adder/subtractors
- MUX/DEMUX
- Encoders/decoders

Basic logic gates


- NOT/AND/OR/NAND/NOR/XOR/XNOR
- Boolean expressions
- Logic diagrams and schematic diagrams
- Truth tables, timing diagrams

Sequential logic circuits

- Latches and Flip-flops
- Shift registers
- Counters
- State machines

We are now in a position to look at internal hardware details of a microprocessor


Where Are We Heading To?

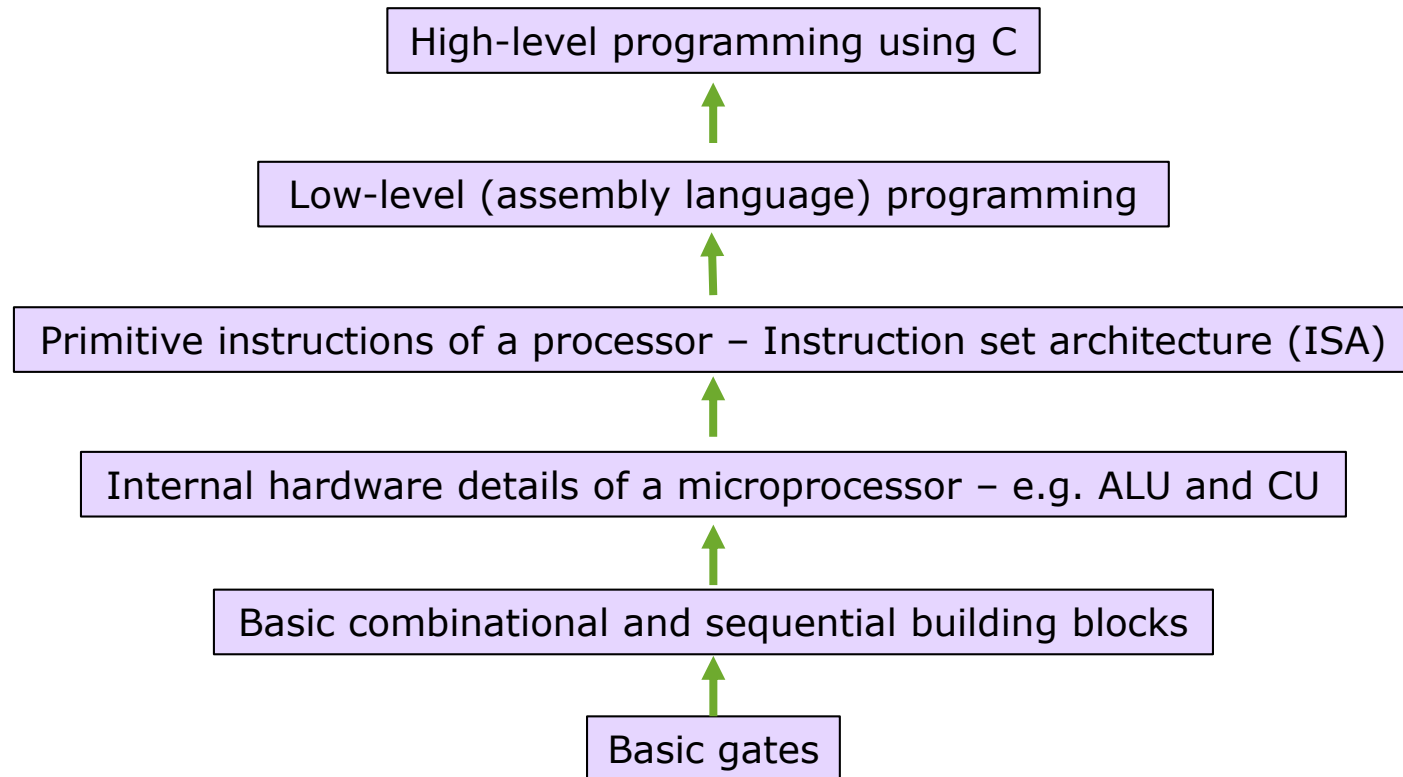

| Wk | Day | Date | Lecture (date) | | Learning Lab | | Assessment due |
|----|---------|-----------|----------------|--|--------------|--|--|
| 1 | Mon-Tue | 26-27 Jul | 1 | Course Introduction and Binary numbers (26 Jul) | | No labs (P2 sessions) on Mon-Tue on week 1 | |
| | Wed-Fri | 28-30 Jul | 2 | Logic gates (28 Jul) | 1 | Signed number representations | |
| 2 | Mon-Tue | 2-3 Aug | 3 | Binary Arithmetic (2 Aug) | 2 | Logic Gates | Quiz 1 (4pm, 6 Aug) |
| | Wed-Fri | 4-6 Aug | 4 | Combinational Logic (4 Aug) | 3 | Binary Arithmetic | |
| 3 | Mon-Tue | 9-10 Aug | 5 | Flip flops (9 Aug) | 4 | Combinational Logic | Quiz 2 (4pm, 13 Aug) |
| | Wed-Fri | 12-13 Aug | 6 | Sequential Circuits 1 - Shift Registers (11 Aug) Pre-recorded lecture due to public holiday on 11/08/21 | 5 | Flip flops | |
| 4 | Mon-Tue | 16-17 Aug | 7 | Sequential Circuits 2 - Counters (16 Aug) | 6 | Sequential Circuits 1 | Quiz 3 (4pm, 20 Aug) |
| | Wed-Fri | 18-20 Aug | 8 | Sequential Circuits 3 - State Machines (18 Aug) | 7 | Sequential Circuits 2 | |
| 5 | Mon-Tue | 23-24 Aug | 9 | From Digital Logic to Processors, ALU (23 Aug) | 8 | Sequential Circuits 3 | Quiz 4 (4pm, 27 Aug) |
| | Wed-Fri | 25-27 Aug | 10A | Memory and Control Unit (25 Aug) | | Cath-up labs, Assignment 1 release end of week 5 | |
| 6 | Mon-Tue | 30-31 Aug | 10B | Introduction to C language (pre-recorded) Review session for Assignment 1 part 1 (30 Aug) | | Assignment 1 working time Part 1: 1-hour timed quiz Part 2: Digital logic design | Assignment 1 - part 1 due date (4pm, 3 Sep) |
| | Wed-Fri | 01-03 Sep | 11 | Introduction to AVR and Assembly Language (1 Sep) | | | |
| 7 | Mon-Tue | 06-07 Sep | 12 | Instruction Set Architecture 1 (06 Sep) | 9 | C Programming | Assignment 1 - part 2 submission (4pm, 6 Sep) Quiz 5 (4pm, 10 Sep) |
| | Wed-Fri | 08-10 Sep | 13 | Instruction Set Architecture 2 (08 Sep) | 10 | Atmel Assembly | |
| 8 | Mon-Tue | 13-14 Sep | 14 | C for AVR Microcontroller (13 Sep) | 11 | AVR Hardware Introduction | Quiz 6 (4pm, 17 Sep) |
| | Wed-Fri | 15-17 Sep | 15 | Flow Control and AVR Timers (15 Sep) | 12 | AVR C Programming | |
| 9 | Mon-Tue | 20-21 Sep | 16 | Pulse Width Modulation (PWM) (20 Sep) | 13 | AVR Timers | Quiz 7 (4pm, 24 Sep) |
| | Wed-Fri | 22-24 Sep | 17 | Interrupts (22 Sep) | 14 | AVR PWM | |

Computer Organisation

- **Simplified** view:

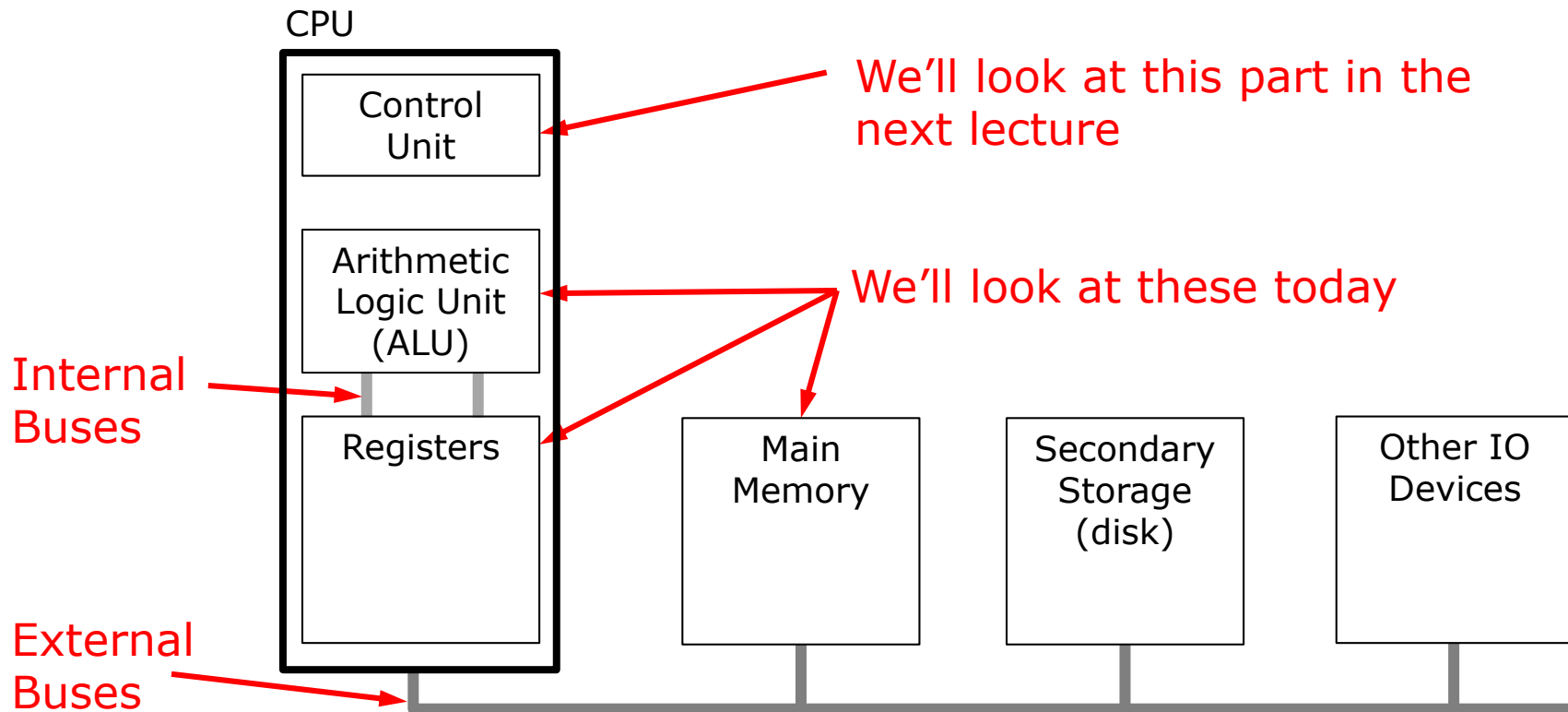

Parts of a CPU

- **Control Unit**

- Fetches instructions from memory, makes the ALU and the registers perform the instruction


→ The topic of next lecture

- **ALU**

- Performs arithmetic and logical operations


- **Registers**

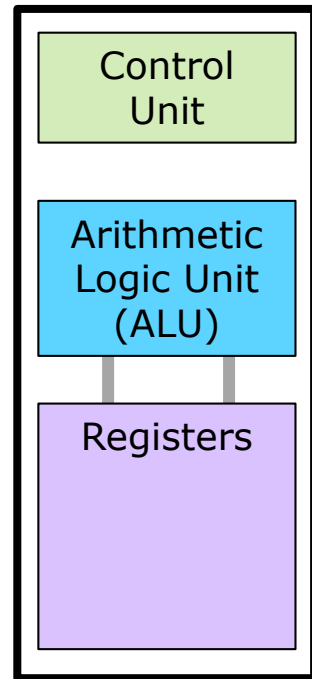- High speed memory – stores temporary results and control information
- e.g. small CPU may have 8 x 8-bit registers
- large CPU may have 64 x 32-bit registers




Registers

- Registers are temporary storage locations inside the CPU.
- Two types of registers
 - **General Purpose Registers**
 - Contains data to be operated on (e.g. data read from memory), results of operations,
 - Also known as register file. Width is the CPU word size
 - **Special Purpose Registers**
 - Used by the system
 - **Program Counter (PC)** – stores the address of the next instruction to be fetched from the memory
 - **Instruction Register (IR)** – stores the current instruction

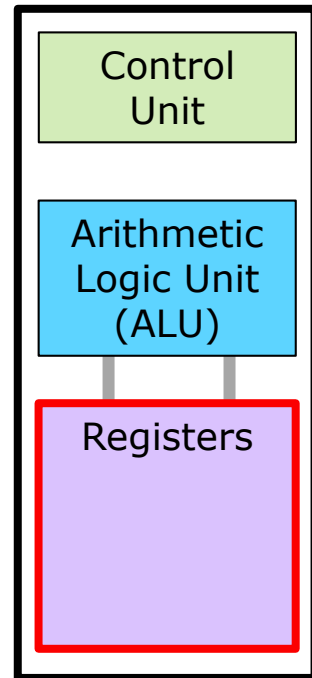



Buses

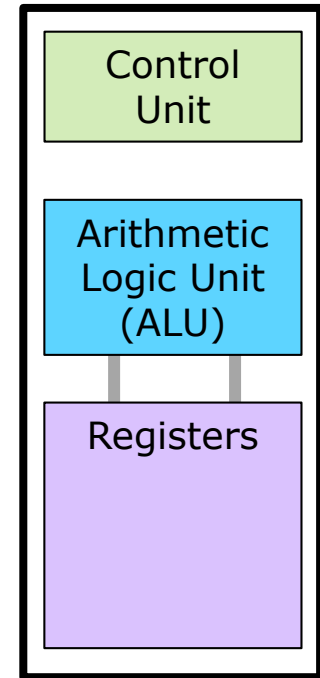- **Bus** = Common pathway (collection of “wires”) connecting parts of a computer
- Characteristics
 - Can be **internal** to CPU (e.g. ALU to registers)
 - Can be **external** to CPU (e.g. CPU to memory)
 - Buses have a **width** – number of bits that can be transferred together over a bus
 - e.g. 1-bit, 8-bits or 32-bits
 - May not always be the same as the word size of the computer



Binary Adder (From Three Weeks Ago)

 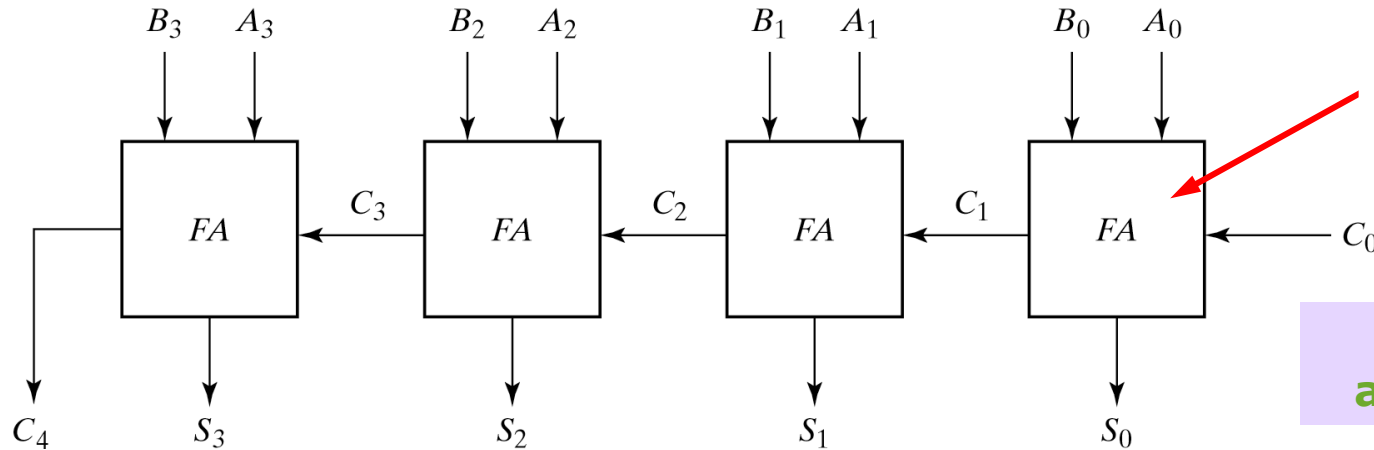- Can cascade full adders to make binary adder
 - Example: for 4 bits...




**Bit-slice
architecture**

- This is a **ripple-carry adder**

Simplifying Representation

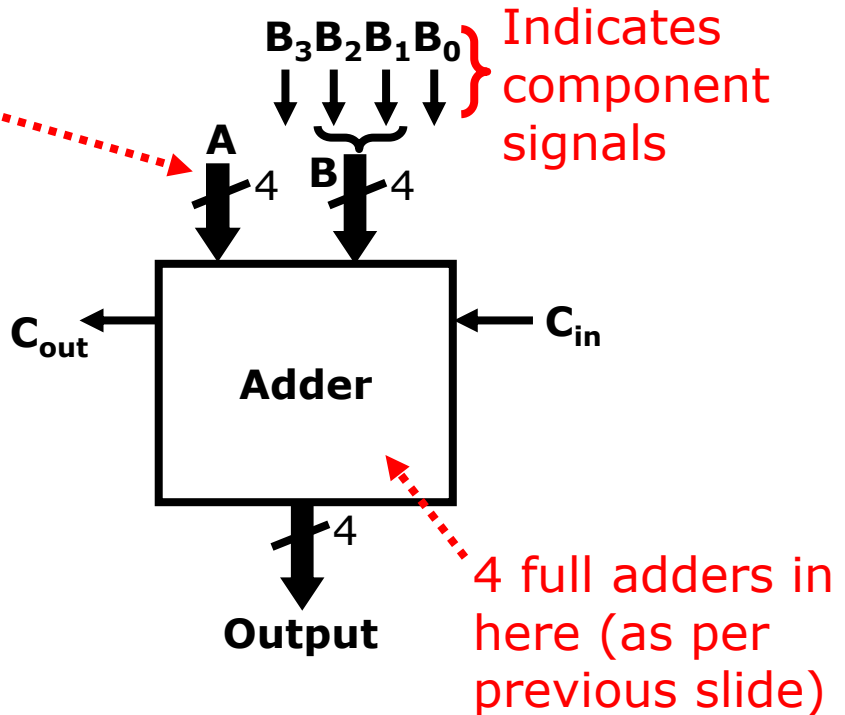
- To simplify representation we group bits together
- **Bus**
 - collection of wires
- **Bus width**
 - number of bits transferred together (in parallel)
 - 4 in this example



Arithmetic Logic Unit (ALU)

- Does more than adding...
- **Function/control** input indicates the operation that the ALU is to perform, e.g.
 - Addition
 - Increment (+1)
 - Subtraction
 - Bitwise AND
 - Bitwise OR
 - ...
- Like adders, ALUs can be made up from 1-bit slices

 Versatile hardware which can perform various operations based on some control inputs



Bitwise Operations

- Operate on corresponding bits, e.g.
bitwise A and B

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

Clicker question: What is the bitwise OR of 0x74 and 0x85?

17% **A.** 0x04

17% **B.** 0x74

17% **C.** 0x85

17% **D.** 0xF1


17% **E.** 0xF5

17% **F.** 0xF9


1-bit ALU (bit slice)

- F_1, F_0 select ALU function

- 00 → A and B
- 01 → invert B
- 10 → A or B
- 11 → A plus B

 

Example 1-bit ALU - Components

 

Data inputs – A, B

Control inputs

- ❑ INVA – invert A- inverts the corresponding input if set to 1
- ❑ ENA, ENB – enable A, enable B – enable the data input if set to 1
- ❑ Also some other function select control inputs (not shown above)


Two levels of control:

- Permutations of data inputs
- Function (operation)

Building the ALU

4 Functions

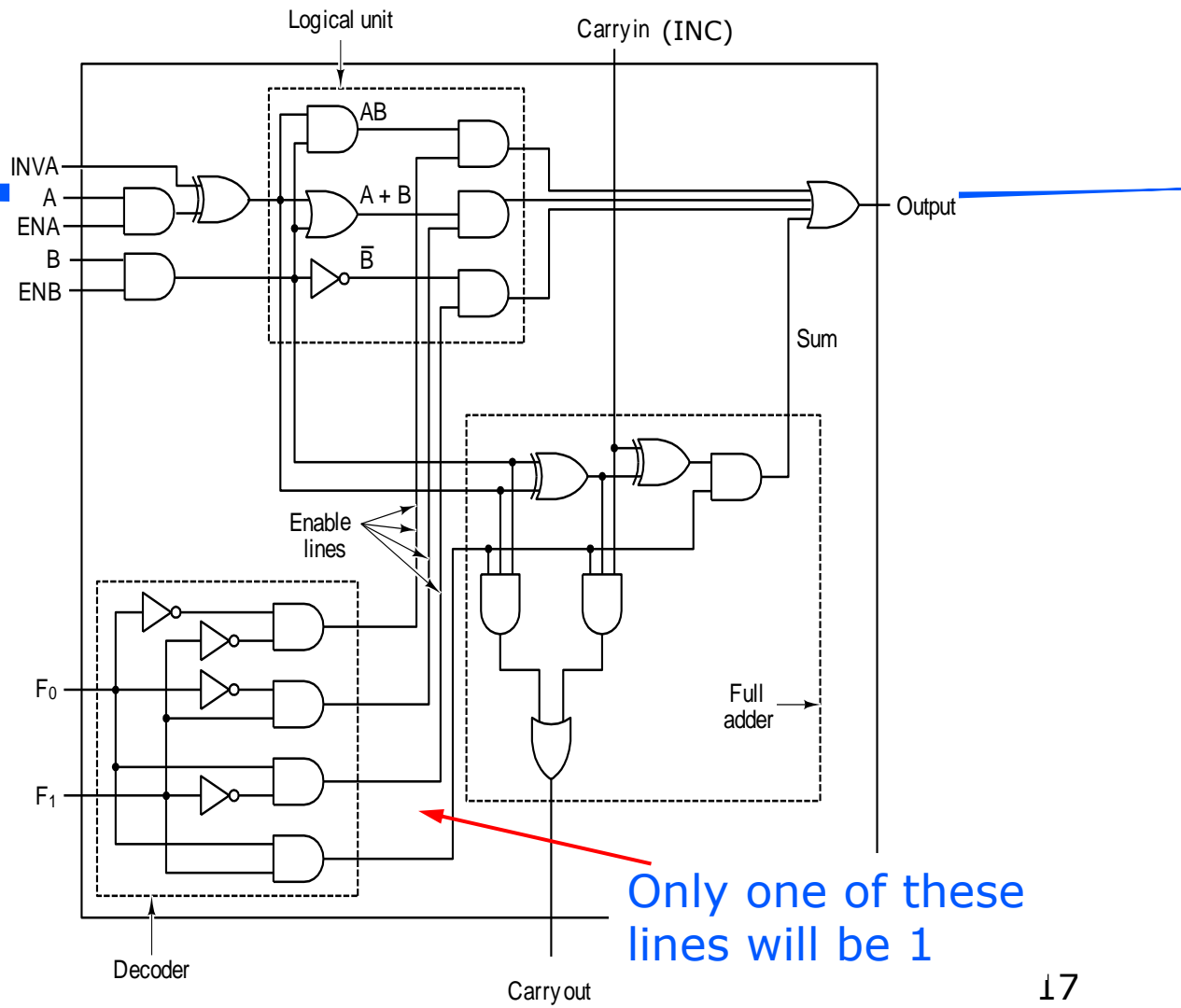
- $A \text{ and } B$
- \overline{B}
- $A \text{ or } B$
- $A \text{ plus } B$



[Figure from
Tanenbaum, "Structured
Computer Organization"]

Arithmetic Logic Unit (ALU)

 
- Remember, machine word = n bits
 - (often 8, 16, 32, ...)
- n -bit ALU can be built up of n identical circuits for the individual bit positions



ALU Bit Slice Architecture

- Can be cascaded to make an n-bit ALU

- Example: 8 bits

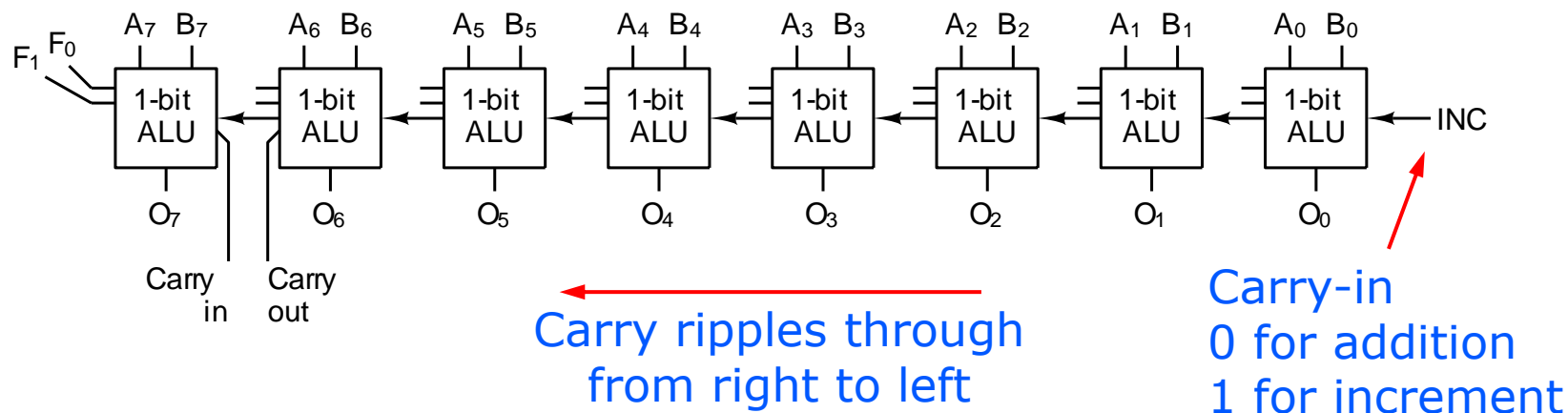

- F₁, F₀, ENA, ENB, INVA inputs are shared between all bit slices

Example

- How can we calculate $B-A$ using this ALU?

- i.e. what are the values of $F_1, F_0, ENA, ENB, INVA, INC$

- Note: $B-A = B+(-A)$
 $= B+(\bar{A} + 1)$
 $= B + \bar{A} + 1$

Two's complement
negation



How can we calculate B+1 (B plus 1) using this ALU?


20% $F_0=0$ $F_1=1$ ENA=0 ENB=1 INVA=1 INC=0

20% $F_0=0$ $F_1=1$ ENA=0 ENB=1 INVA=0 INC=1

20% $F_0=1$ $F_1=1$ ENA=0 ENB=1 INVA=1 INC=0


20% $F_0=1$ $F_1=1$ ENA=0 ENB=1 INVA=1 INC=1

 20% $F_0=1$ $F_1=1$ ENA=0 ENB=1 INVA=0 INC=1




Some Useful Combinations of ALU Inputs

| F ₁ | F ₀ | ENA | ENB | INVA | INC | Function |
|----------------|----------------|-----|-----|------|-----|-----------|
| 1 | 0 | 1 | 0 | 0 | 0 | A |
| 1 | 0 | 0 | 1 | 0 | 0 | B |
| 1 | 0 | 1 | 0 | 1 | 0 | \bar{A} |
| 0 | 1 | 1 | 1 | 0 | 0 | \bar{B} |
| 1 | 1 | 1 | 1 | 0 | 0 | A + B |
| 1 | 1 | 1 | 1 | 0 | 1 | A + B + 1 |
| 1 | 1 | 1 | 0 | 0 | 1 | A + 1 |
| | | | | | | B + 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | B - A |
| 1 | 1 | 0 | 1 | 1 | 0 | B - 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | - A |
| 0 | 0 | 1 | 1 | 0 | 0 | A AND B |
| 1 | 0 | 1 | 1 | 0 | 0 | A OR B |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | - 1 |

 

How the ALU is used ... Data Path

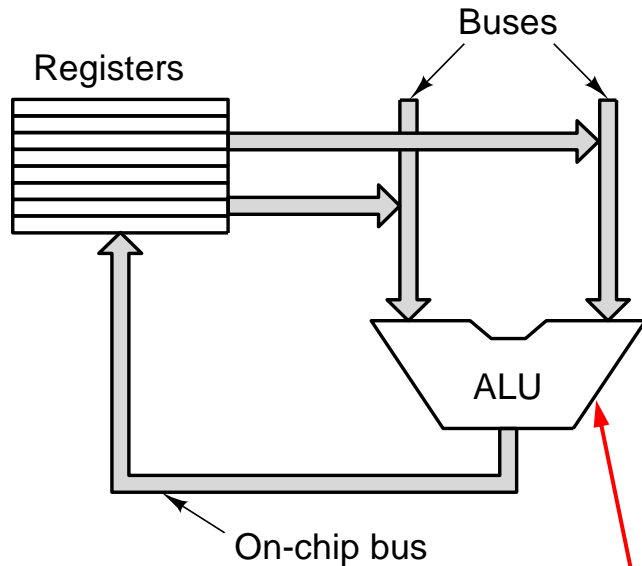

ALU inside a Central
Processing Unit (CPU)

Conventional
ALU Symbol

- Operands come from register file
- Result written to register file
- Implements routine instructions such as arithmetic, logical, shift
- Width of registers/buses is the CPU word size

Data Path (Explanation)

- ALU performs operations on data from the register file
 - CPU control unit determines which registers the operands come from and which operation is performed
- Result returned to a register within the register file
 - Could overwrite one of the operands
- Register \Leftrightarrow memory transfers also possible
 - Read: load a register with data from a memory address
 - Write: store a register's contents to a memory address

ALU: In Reality

- Microprocessor may have a number of processing units, e.g.
 - One or more integer processing units
 - Floating point unit(s)
- Units may be capable of operating in parallel