

CSSE2010/CSSE7201 Lecture 8

Sequential Circuits 3 State Machines

School of Information Technology and Electrical Engineering
The University of Queensland



Outline

- Admin
- State machines
 - State diagrams
 - State tables
 - State encoding




Admin

Quiz 3 is due on Friday 4pm this week



Sequential Circuits

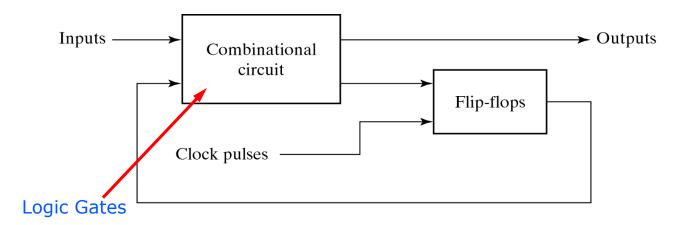- State = value stored in flip-flops
- Output depends on input and state
- Next state depends on inputs and state





State Machines

- Sequential circuits can also be called
 - state machines
 - finite state machines (FSMs)
- State machine has
 - Finite number of possible states
 - Only one current state
 - Can transition to other states based on inputs and current state



State Machines

The states can be defined based on the problem:

E.g. a vending machine accepting 5 cents and 10 cents coins to dispense a candy when it receives 15 cents in total. What can be the different states?




Types of State Machines


- Two types
 - Mealy machines
 - Outputs depend on current state and inputs
 - Moore machines
 - Outputs depend only on current state (flip-flop values)
 - Outputs can only change when state changes



Moore vs Mealy Machine

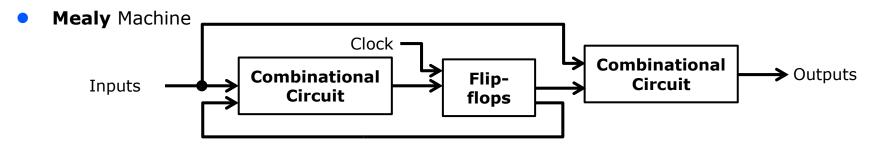

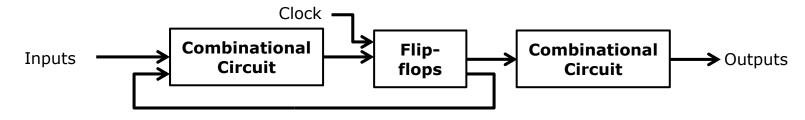Moore Machine – special case of a Mealy Machine



We'll stick to Moore machines in this course




State Diagram

To be illustrated in class



State Diagram (cont.)

- Notation
 - State

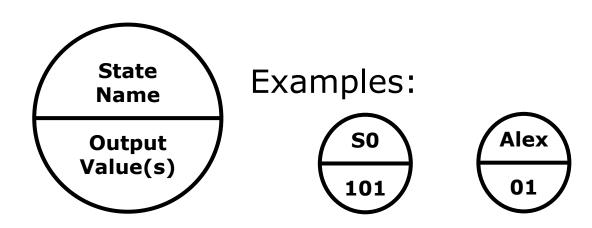

Transition

Logic expression O

 $\xrightarrow{0}$ $\xrightarrow{1}$

Special case for only one input

- If expression is true, state transition is made
- No label means "true" i.e. always transition
- Examples

 \xrightarrow{z}

RESET

 $\xrightarrow{A+B.\overline{C}} \longrightarrow_{1}$



Example – to be worked out in class

Binary counter with 2-bit output



Example

- Binary up/down counter with 2-bit output
 - One input: U
 - 1 means count up
 - 0 means count down



Example

- Binary up/down counter with 2-bit output
 - Two Inputs: U,D
 - U=1, D=0 means count up
 - U=1, D=1 means set to 11

$$U=0$$
, $D=1$ means count down

- Binary up/down counter with 2-bit output
 - U=1, D=0 means count up
 - U=0, D=1 means count down
 - U=1, D=1 means set to 11
 - U=0, D=0 means reset to 00



Completeness

- Each possible combination of inputs should be addressed exactly once for each state
 - i.e. transition arrows from each state must encompass all possibilities (exactly once)
- Example:



State Table

- State diagrams can also be represented in a state table
- Example binary up/down counter with 2-bit output and single input U (1 means up, 0 means down)
- One dimensional state table:

	Current	Input U	Next State	Outputs	
	State			Q1	Q0
Every combination of state and inputs					



State Table (cont.)

- Two-dimensional state table
- Same example

Every combination of inputs

	Current	Next State		Outputs	
	State	Ū	U	Q1	Q0
One row per state					




State encoding

- Must encode each state into flip-flop values
- Choose
 - Number of flip-flops
 - Bit patterns that represent each state
- Ideally
 - Choose state encoding to make combinational logic simple, for both
 - Output logic
 - Next state logic



Example

Binary counter with 2-bit output

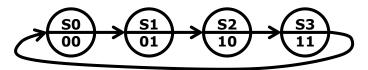



One-hot coding

- Use one flip-flop per state
- Only one flip-flop has 1 at any time
- Example binary counter with 2-bit output



Sequence Detector Example

- Design a state machine which detects the pattern 101 in an incoming bit stream and outputs a 1 whenever it detects this pattern
 - Output is 1 for one clock cycle after the third digit is clocked in
- Example:
 - Input: 00<u>101</u>1<u>101</u>0100
 - Output: 0000100010100