

CSSE2010/CSSE7201

Lecture 2

Intro to Logic Gates

School of Information Technology and Electrical Engineering
The University of Queensland

Today...

- Introduction to Logic Gates
- Logic Diagrams
- Boolean Algebra and Logic Expressions
- There will be several polling questions
 - URL: responsewaresg.net
 - Session ID: csse2010s2

Learning Lab Sessions

- Slides used will be made available
 - After the last session that week
- Only attend the session you are signed-up to
 - Contact eait.mytimetable@uq.edu.au if you have sign-on issues
- If specific preparation is required, you'll get told, by default you should review previous lectures
- Make sure you attend and complete the learning labs for each week

Digital Logic

- **Digital circuits**

- Only **two** logical levels present (i.e. binary)
 - Logic '0' – usually small voltage (e.g. around 0 volts)
 - Logic '1' – usually larger voltage (e.g. 0.8 to 5 volts, depending on the “logic family”, i.e. type/size of transistors)

- **Logic gates**

- are the building blocks of computers;
- Each gate has
 - one or more inputs
 - exactly one output
- perform logic operations (or functions)
 - 7 basic types: **NOT**, **AND**, **OR**, **NAND**, **NOR**, **XOR**, **XNOR**
 - Inputs & outputs can have only two states, 1 & 0 - can be called “true” & “false”
 - **Logic symbol**, **Truth table**, **Boolean expression**, **Timing diagram**

Recall – Levels of Abstraction

Level 5

Problem-oriented language level

Level 4

Assembly language level

Level 3

Operating system machine level

Level 2

Instruction set architecture level

Level 1

Microarchitecture level


Level 0

Digital Logic Level

Basic Logic Gates

Logic
Symbol \Rightarrow

NOT gate

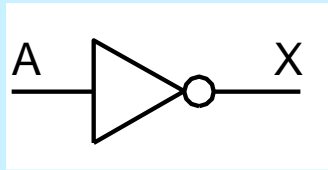


Truth
table \Rightarrow

A	X
0	1
1	0

Inverts the input

Also called
"inverter"


AND gate

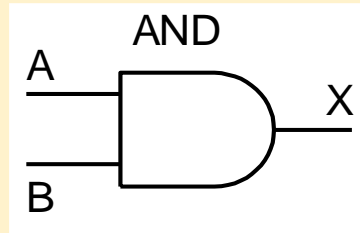

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Output is HIGH when
all the inputs are HIGH

OR gate

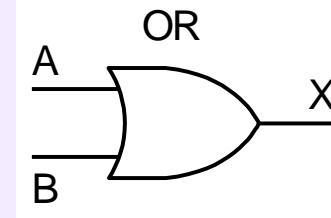


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Output is HIGH when at
least one input is HIGH

Basic Logic Gates (cont...)

NAND gate

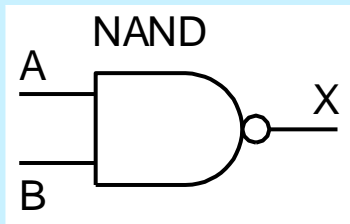


Truth table



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Output is HIGH when at least one input is LOW


NOR gate

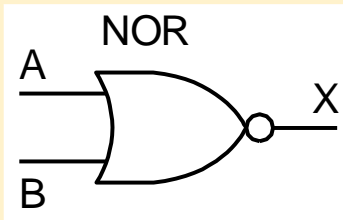

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Output is HIGH when all the inputs are LOW

XOR gate

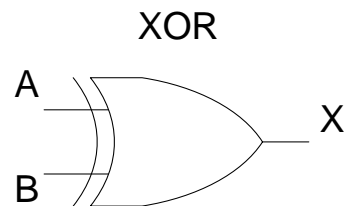


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Output is HIGH when exactly one input is HIGH

Basic Logic Gates (cont...)

XNOR gate

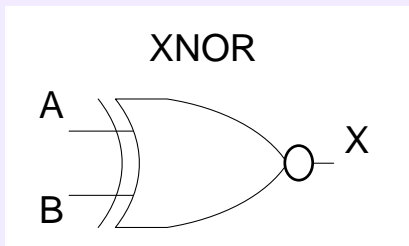

Truth table

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

Output is HIGH
when the inputs
are the same

NOT

AND

OR

NAND

NOR

XOR

XNOR

Useful to
remember:

XOR is the **odd**
function and
XNOR is the
even function

What's the truth table for a 3-input NAND gate

1.

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

2.


A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

3.

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

4.

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

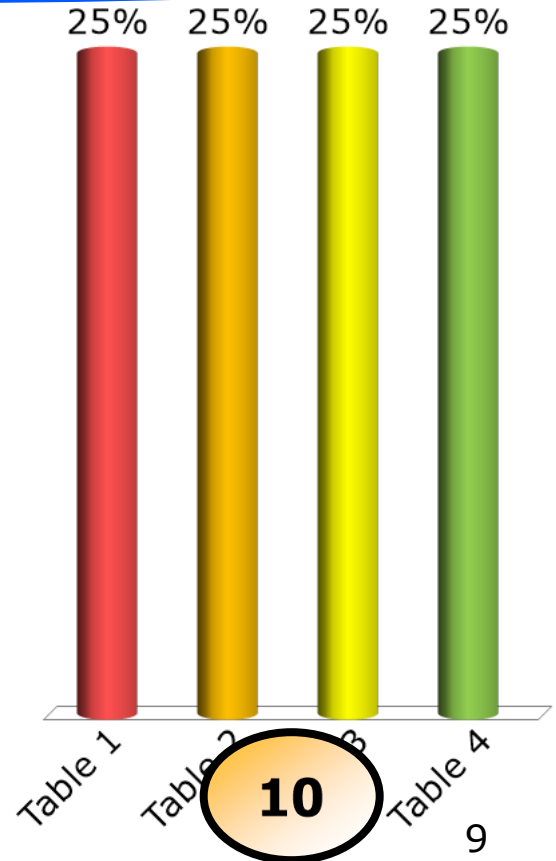

What's the truth table for a 3-input XOR gate

1.

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

2.

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

3.

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

4.

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Boolean Logic Functions

- Logic functions can be expressed as expressions involving:
 - variables (literals), e.g. A B X
 - functions, e.g. $+$ $.$ \oplus $\bar{}$
- Rules about how this works called **Boolean algebra**
- Variables and functions can only take on values **0** or **1**

Boolean Algebra conventions

- Conventions we'll use:
 - **Inversion:** $\bar{}$ (overline)
 - e.g. **NOT(A) = \bar{A}** (pronounced as A bar)
 - **AND:** dot(.) or implied (by adjacency)
 - e.g. **AND(A,B) = $AB = A.B$**
 - **OR:** plus sign
 - e.g. **OR(A,B,C) = $A+B+C$**
- Other examples:
 - **XOR(A,B) = $A \oplus B = \bar{A}B + A\bar{B}$**
 - **NAND(A,B,C) = \overline{ABC}**
 - **NOR(A,B) = $\overline{A+B}$**


Summary of Logic Function Representations

- There are four representations of logic functions (assume function of n inputs)
 - **Truth table**
 - Lists output for all 2^n combinations of inputs
 - Best to list inputs in a systematic way
 - **Boolean function (or equation)**
 - Describes the conditions under which the function output is 1
 - **Logic Diagram**
 - Combination of logic symbols joined by wires
 - **Timing Diagram**

Logic Diagram Conventions

Inputs are conventionally on left

Outputs are conventionally on right


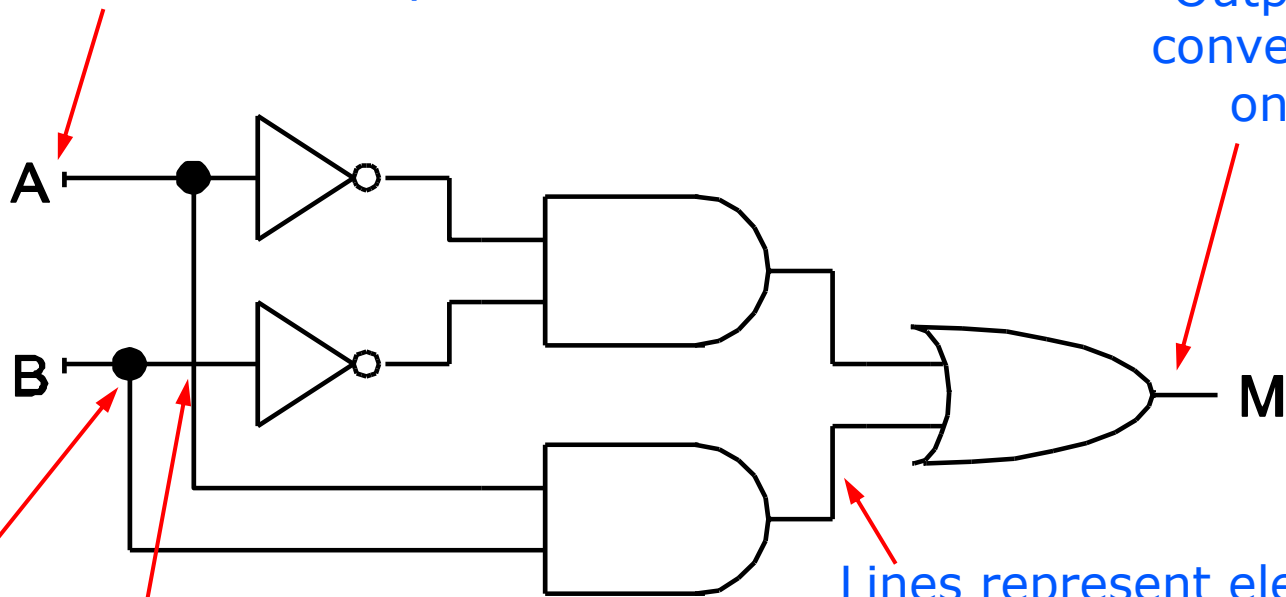


Indicates
Electrical
Connection

No Connection

Lines represent electrical
wires. Can be at high or
low potential (logic 1 or
logic 0 respectively).

Gates on Integrated Circuits (ICs)

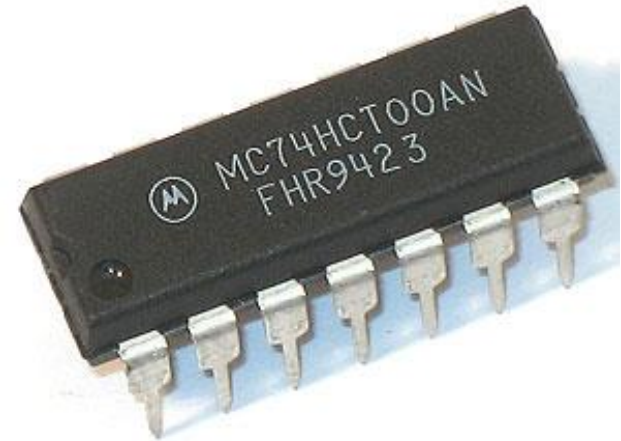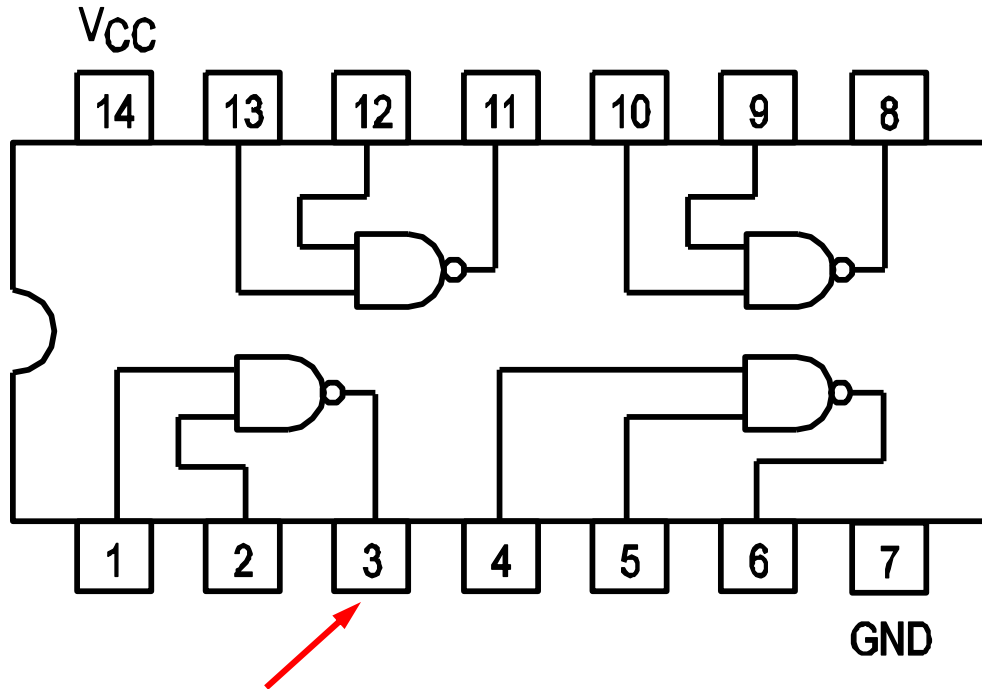


Pin spacing is 0.1" x 0.3"; chip is about 15mm long

- 74HCT00 – has four 2-input NAND gates
- **V_{CC}** = Power (e.g. 5V), **GND** = Ground (0V)

Short Break

- Stand up and stretch

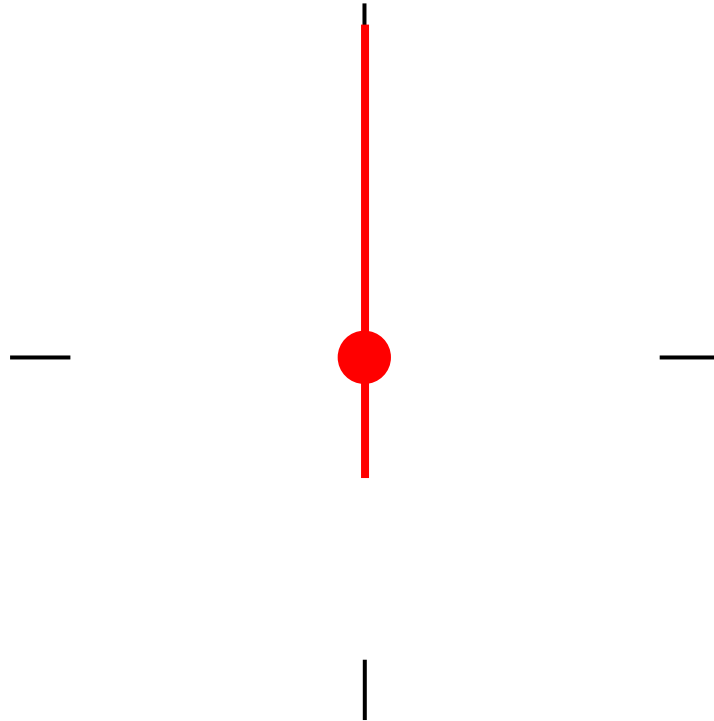

Logic Function Implementation

- Any logic function can be implemented as the OR of AND combinations of the inputs
 - Called **sum of products**
- Example:
 - Consider truth table
 - For each '1' in the output column, write down the AND combination of inputs that give that 1
 - OR these together


A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Logic Function Implementation

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Example (cont.)


Equivalent Logic Diagram

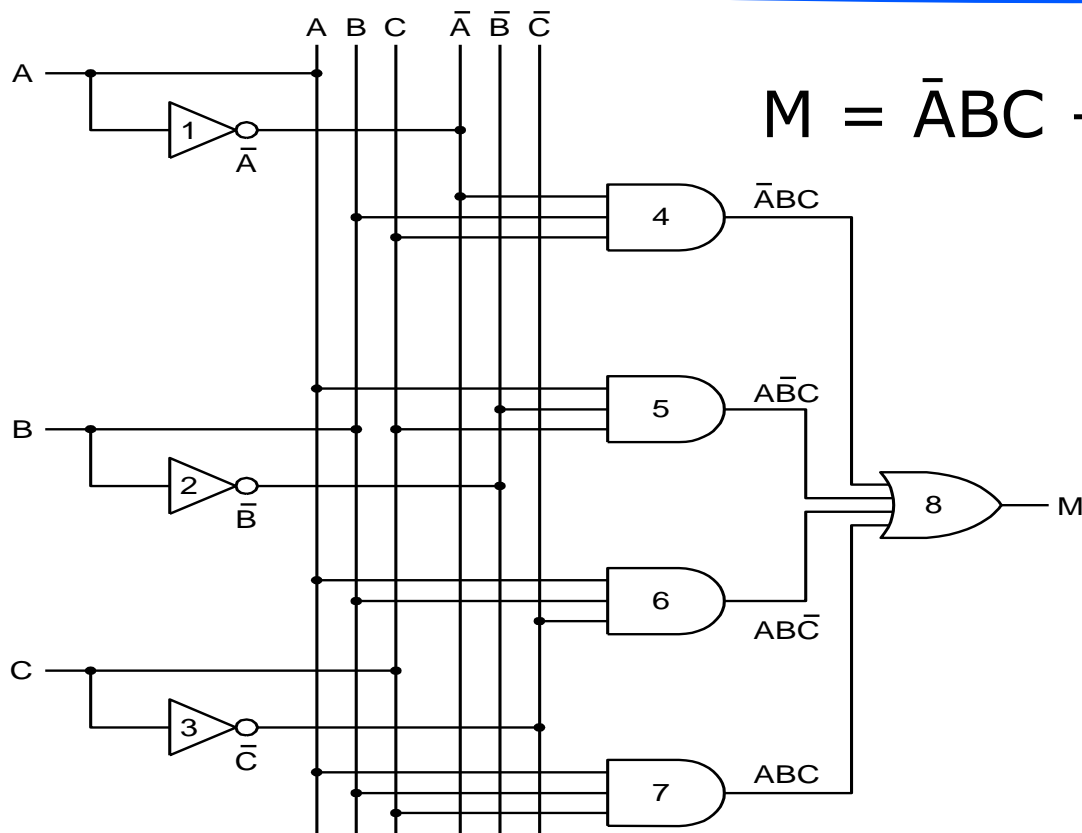


$$M = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Equivalent Functions

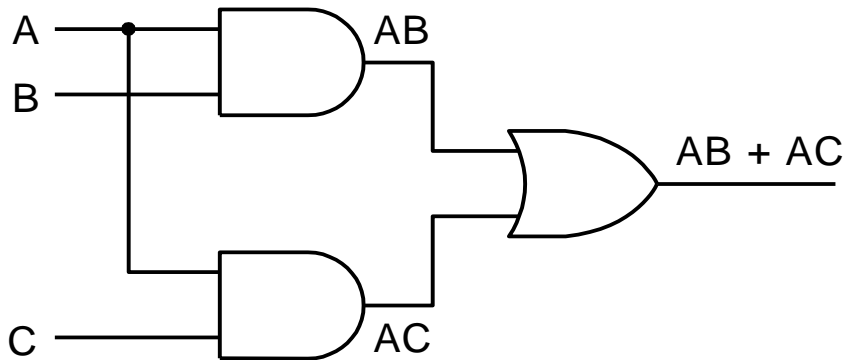- Sum of products does not necessarily produce circuit with minimum number of gates
- Can *manipulate* Boolean function to give an equivalent function
 - Use rules of Boolean algebra (next slide)
- Example: $Z = AB + AC = A(B+C)$



Simplified version

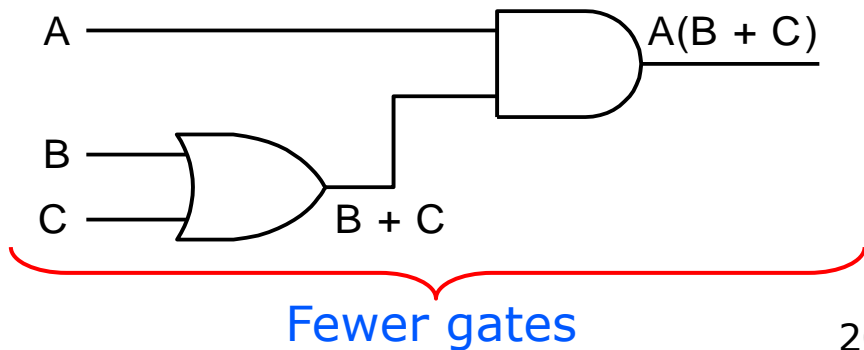

Boolean Identities





Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

Example

- Express $Z = \overline{A(B+C(\overline{A} + \overline{B}))}$ as a sum of products

De Morgan Law/Equivalents



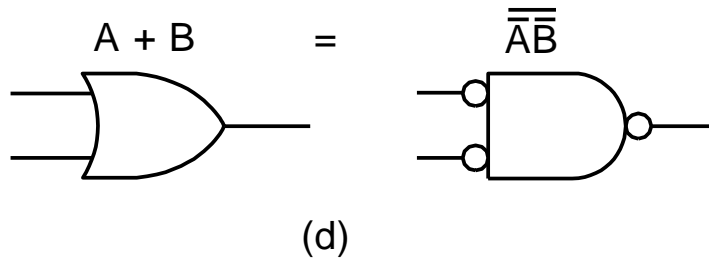
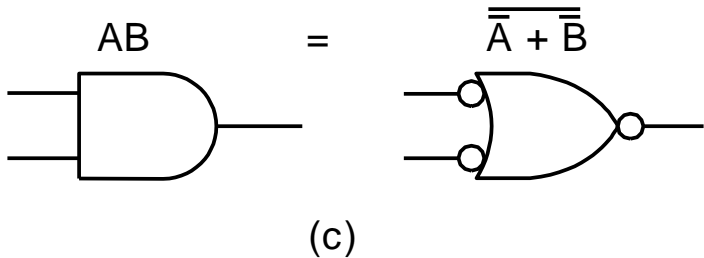
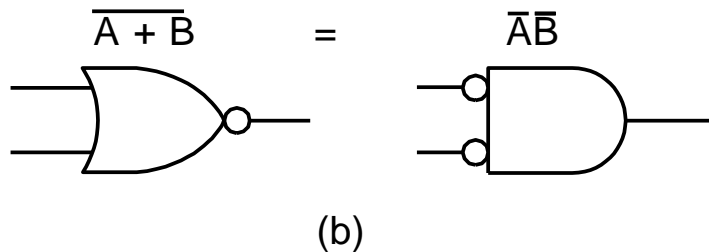
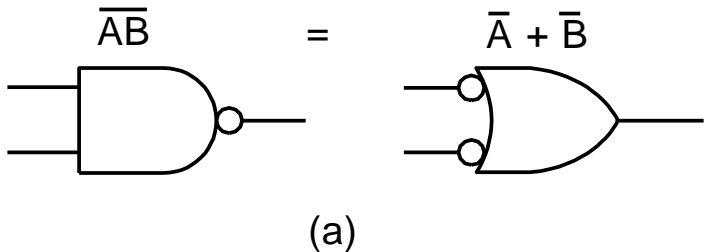
- AND/OR can be interchanged if you invert the inputs and outputs



- Homework: Use truth tables to convince yourself that these are valid

Equivalent Circuits

- All circuits can be constructed from NAND or NOR gates
 - These are called **complete** gates
- Examples:

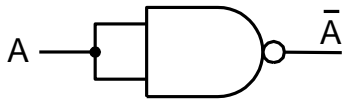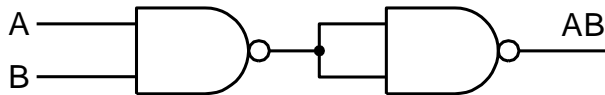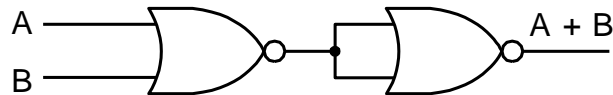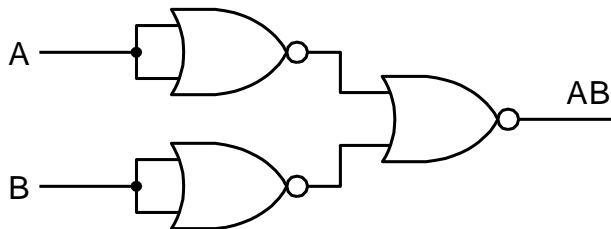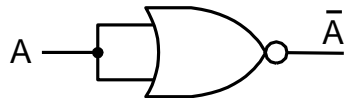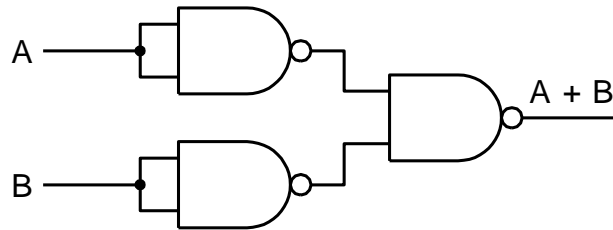NOT**AND****OR**

- Reason: Easier to build NAND and NOR gates from transistors

Reminders

- Quiz 1 due next week Friday
- Attend Learning Lab sessions for the second half of this week
 - Only attend the session you're signed up to
 - Internal (IN) mode students should collect a kit in their face-to-face prac sessions.
 - External (EX) mode students, you do not need your hardware until week 6. But start acquiring your hardware items now.