

**CSSE2010/CSSE7201 – Introduction to Computer Systems  
Semester One, 2019**

**Lab 4 Preparation Task**

You should complete three circuit schematic diagrams as listed below before your Monday/Tuesday/Wednesday lab session in week 3 of semester (**Monday 11 March to Wednesday 13 March**). You should consult the device pinout information on Blackboard. You will be constructing these circuits during the prac session.

**Circuit 1**

Draw a circuit schematic diagram for a 2-to-1 multiplexer that uses only 2-input NAND gates. The data inputs should be connected to push buttons. The select input should be connected to a switch. The output should be connected to an LED.

**Circuit 2**

Draw a circuit schematic diagram for a 2-to-4 decoder - using whichever logic gates you prefer (from those available in the CSSE2010/CSSE7201 lab). The two inputs should be connected to switches. The outputs should be connected to LEDs.


A 2-to-4 decoder has the following truth table (labelling inputs A1, A0 and outputs X0, X1, X2, X3):

| A1 | A0 | X0 | X1 | X2 | X3 |
|----|----|----|----|----|----|
| 0  | 0  | 1  | 0  | 0  | 0  |
| 0  | 1  | 0  | 1  | 0  | 0  |
| 1  | 0  | 0  | 0  | 1  | 0  |
| 1  | 1  | 0  | 0  | 0  | 1  |

**Circuit 3**

Using a 74HCT04, 74HCT157 and a 74HCT283, draw a circuit schematic diagram for a circuit which can act as a 4-bit two's complement adder or subtractor. The output (4-bits from the 74HCT283, which should be shown on LEDs) will have the value  $A+B$  or  $A-B$  (where A and B are the 4-bit inputs which are taken from switches). A push button input (M, mode) will determine whether the circuit performs addition or subtraction - if the value is 0, addition will be performed; if the value is 1, subtraction will be performed by calculating  $A+(-B)$ . The circuit is similar to that shown in lecture 4 (Wednesday 6 March) except the selection of the "B" input bits as B or not(B) is to be performed using multiplexers instead of XOR gates. (The 74HCT157 is a quad 2-to-1 multiplexer with a shared select input.) The carry output should be shown on a LED also.

## Circuit 1 - 2-1 Multiplexer

 

Function Table

| S | F              |
|---|----------------|
| 0 | D <sub>0</sub> |
| 1 | D <sub>1</sub> |

Truth Table

| S | D <sub>1</sub> | D <sub>0</sub> | F |
|---|----------------|----------------|---|
| 0 | 0              | 0              | 0 |
| 0 | 0              | 1              | 1 |
| 0 | 1              | 0              | 0 |
| 0 | 1              | 1              | 1 |
| 1 | 0              | 0              | 0 |
| 1 | 0              | 1              | 0 |
| 1 | 1              | 0              | 1 |
| 1 | 1              | 1              | 1 |

$$F = \bar{S}\bar{D}_1D_0 + \bar{S}D_1D_0 + S\bar{D}_1\bar{D}_0 + S\bar{D}_1D_0$$

|                  |                           |                      |
|------------------|---------------------------|----------------------|
| Distributive law | $A + BC = (A + B)(A + C)$ | $A(B + C) = AB + AC$ |
|------------------|---------------------------|----------------------|

$$= \bar{S}D_0(\bar{D}_1 + D_1) + S\bar{D}_1(\bar{D}_0 + D_0)$$

$$= \bar{S}D_0 + S\bar{D}_1$$

$$= \overline{\bar{S}D_0} \cdot \overline{S\bar{D}_1}$$


OR

AND

DeMorgans Law


IO1

IoBoard

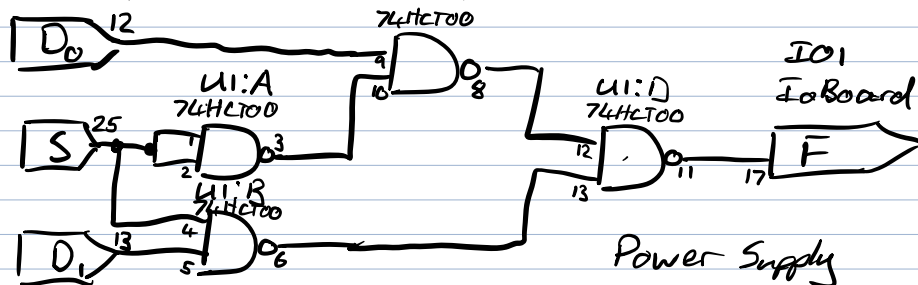


Power Supply

74HC100 Vcc: Pin 14  
GND: Pin 7

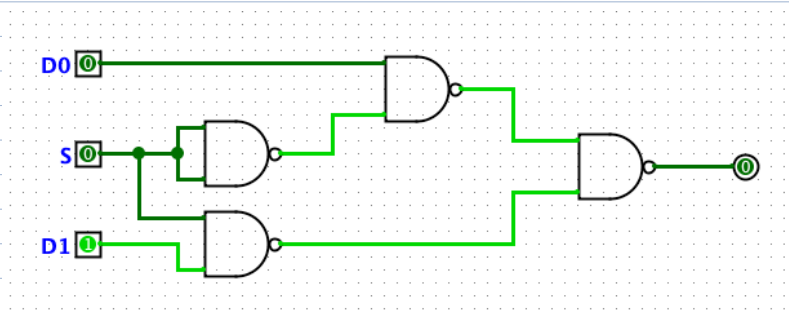

## Circuit 2

 

| A1 | A0 | X0 | X1 | X2 | X3 |
|----|----|----|----|----|----|
| 0  | 0  | 1  | 0  | 0  | 0  |
| 0  | 1  | 0  | 1  | 0  | 0  |
| 1  | 0  | 0  | 0  | 1  | 0  |
| 1  | 1  | 0  | 0  | 0  | 1  |

$$X_0 = \bar{A}_1 \bar{A}_0$$



$$X_1 = \bar{A}_1 A_0$$

$$X_2 = A_1 \bar{A}_0$$

$$X_3 = A_1 A_0$$

Power

 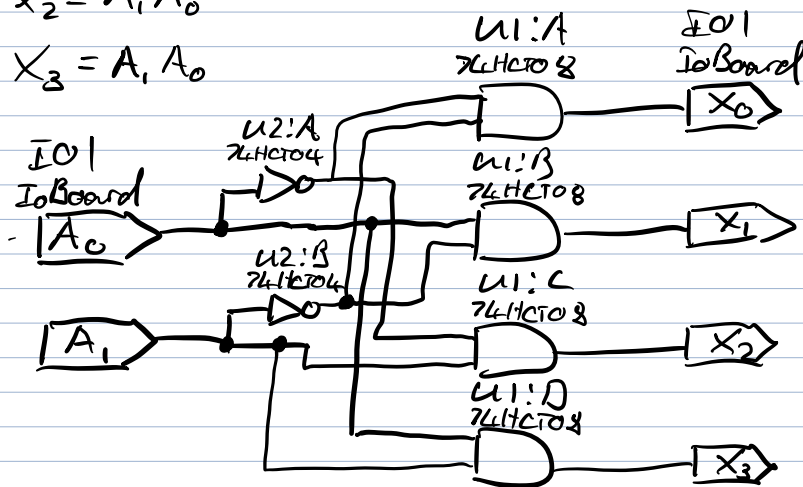74HC104 } Vcc: Pin 14  
74HC108 } GND: Pin 7



# Circuit 3 - 4-bit adder/subtractor (2's comp)

$$S_4 = A_4 + B_4 \quad \text{Addition}$$

or

$$S_4 = A_4 + (-B) \quad \text{Subtraction}$$

$$= A_4 + \bar{B} + 1$$

IC1  
IoBoard

M 12

A<sub>0</sub> 25

A<sub>1</sub> 26

A<sub>2</sub> 27

A<sub>3</sub> 28

B<sub>0</sub> 29

B<sub>1</sub> 30

B<sub>2</sub> 31

B<sub>3</sub> 32

3

6

10

13

EN

U1  
74HCT157

15

4

2

1

12

7

5

14

12

3

5

14

12

3

5

14

12

3

5

14

12

3

5

14

12

3

</

