

CSSE2010 / CSSE7201
Lecture 3

Binary Arithmetic

School of Information Technology and Electrical Engineering
The University of Queensland

Today...

- Admin
 - Recap on signed number representations in binary
 - Logic gates revisited – from previous lecture
 - Binary Arithmetic
 - Arithmetic Circuits
-
- Questions: please put them on to the padlet and I will answer them after the lecture

Admin

- Contact eaits.mytimetable@uq.edu.au if not yet signed up or you're unable to attend the labs you are signed on to
- Two lab sessions per week from this week. Refer to week-by-week teaching outline on Blackboard.
- All labs are now online due to SEQ lockdown. Zoom information is on Blackboard. IN mode labs will return face-to-face mode based on COVID-19 guidelines.
- Weekly exercises (not assessed) are available on Blackboard
- **Quiz 1 – due this week Friday 4pm. Single attempt and need to submit (not auto submitted)**

Quick Recap – Week 1 Lectures & Learning Lab

Number bases

Binary
(base 2)

Decimal
(base 10)

HEX
(base 16)

Octal
(base 8)

Binary Formats

2^{N-1}	2^{N-2}	2^1	2^0	Excess-2^{N-1}	$-2^{N-1} \leq x \leq (2^{N-1} - 1)$
-2^{N-1}	2^{N-2}	2^1	2^0	2's comp	$-2^{N-1} \leq x \leq (2^{N-1} - 1)$
$-2^{N-1}-1$	2^{N-2}	2^1	2^0	1's comp	$-(2^{N-1} - 1) \leq x \leq (2^{N-1} - 1)$
\pm No mag.	2^{N-2}	2^1	2^0	Sign-Mag	$-(2^{N-1} - 1) \leq x \leq (2^{N-1} - 1)$
2^{N-1}	2^{N-2}	2^1	2^0	Unsigned	$0 \leq x \leq 2^N - 1$
<div> <div></div> <div></div> </div>		<div> <div></div> <div></div> </div>			
MSB		N-bit number		LSB	

Logic Gates

NOT, AND, OR, XOR, NAND, NOR, XNOR
Symbols, Truth table, Boolean expression

Logic diagrams, schematic diagrams
Logic expressions, SOP, Simplification using Boolean algebra

What is -32 (base 10) expressed in 8-bit signed magnitude format?

20% **A.** 10100000

20% **B.** 10100001

20% **C.** 11011111

20% **D.** 11100000

20% **E.** I don't know


What is -32 (base 10) expressed in 8-bit two's complement format?

- A. 10100000
- B. 11011111
- C. 10100001
- D. 11100000
- E. I don't know


Equivalent Circuits

- All circuits can be constructed from NAND or NOR gates
 - These are called **complete** gates
- Examples:





NOT

 

AND





 


OR

    

- Reason: Easier to build NAND and NOR gates from transistors

     Which of the following is a NOR only implementation of



Binary Arithmetic

- Addition is quite simple in binary
- We shall see circuits that implement the addition operation later

Addend	0	0	1	1
Augend	+0	+1	+0	+1
Sum	0	1	1	0
Carry	0	0	0	1

- Above ignores carry in


Binary Addition

Decimal	8-bit Unsigned	Decimal	8-bit 2's complement
10	00001010	10	00001010
+ 243	+ 11110011	+ (-13)	+ 11110011
-----	-----	-----	-----
253		-3	

- **Format matters when you interpret the numbers**
- Whatever the format is the bit-wise addition (which leads to the hardware circuit we will be looking at) is the same
- **Two's complement** – you don't need to do anything with the carry out from the MSB to get the correct result
- But in **one's complement** you will **have to add the carry out from the MSB back to the result** to get the correct answer – this is one drawback of one's complement representation – check by yourself

Short Break

- Stand up and stretch

 

Overflow in Binary Addition

Decimal	8-bit Unsigned	Decimal	8-bit 2's complement
15	00001111	125	01111101
+ 243	+ 11110011	+ 4	+ 00000100
-----	-----	-----	-----
258		129	


Overflow: Not enough bits to represent the answer. The result goes out of range. Thus, you get a wrong answer.

How is overflow detected:

- ☐ **Unsigned:** carry-out from the MSB → overflow
- ☐ **2's comp:** carry-in to the MSB and carry-out from the MSB are different → overflow
- ☐ Equivalently, overflow occurs if (in 2's comp)
 - ☐ Two negatives added together give a positive, or
 - ☐ Two positives added together give a negative

What is the result of adding the two 6-bit two's complement numbers 110101 and 001111 in 6-bits?

 - A. 000100
- B. 000101
- C. 001010
- D. 111010
- E. 1000100



What's the truth table for an adder?

Inputs = A, B

Outputs = S(Sum), C(Carry)

1.

A	B	C	S
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

2.


A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

3.

A	B	C	S
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

4.

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Binary Addition

- A device which adds 2 bits (with no carry-in) is called a **half-adder**

Binary Addition


- We have to deal with carry-in. There might be a carry-in from the previous stage.

Addition of Binary Words

- Have to be able to deal with carry-in
- Truth table to be completed in class


A	B	Cin	Cout	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Full Adder

 

Binary Adder

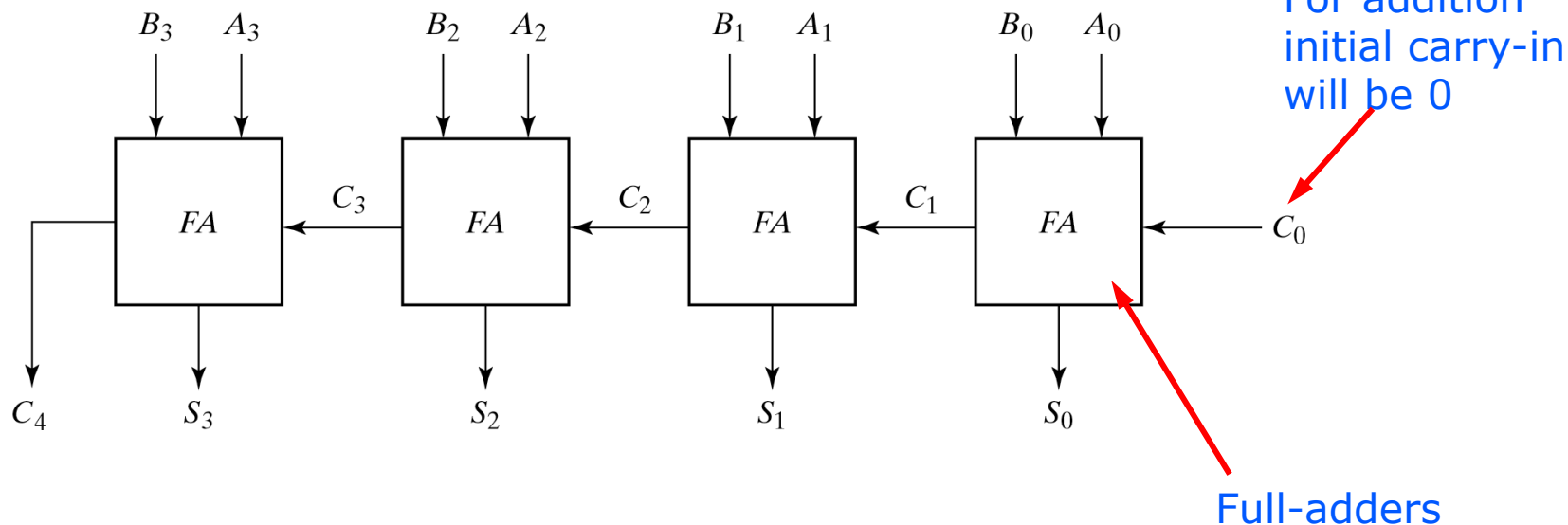- Can cascade full adders to make binary adder
 - Example: for 4 bits...



- This is a **ripple-carry adder**

Reminders for this week

- Lab classes
 - Mon-Tue: Lab 2 (Logic Gates)
 - Wed-Fri: Lab 3 (Binary Arithmetic)
- Quiz due this week Friday 4pm
- This week's labs
 - IN students: if you have borrowed kits then use the kits. Otherwise use the Logisim software to simulate the logic circuits.
 - EX students: Use Logisim software to simulate the logic circuits. Start acquiring Arduino based hardware required in week 6.