

CSSE2010/CSSE7201
Lecture 6

Sequential Circuits 1

Shift Registers

School of Information Technology and Electrical Engineering
The University of Queensland

Outline

- Admin
- Sequential circuits
- Shift registers


Admin

- Quiz 2 is due this week Friday (12-Mar) 4pm
- Labs 6 and 7 for next week (week 4) has preparation tasks which should be attempted before coming to the labs.

Reminder

Memory element: D Flip Flop

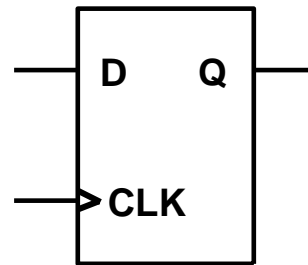
- **D** is input
- **Q** is output
- **CLK** (clock) is control input
- How does it work?
 - Q copies the value of D (and remembers it) whenever CLK goes from 0 to 1 (*rising edge*)



- ❑ **Only D Flip flops are discussed in this course**
- ❑ **Optional asynchronous SET and CLR inputs** to set and clear the output Q even outside clock edges. The SET and CLR inputs are typically **active-low**.
- ❑ **Using D flip flops one can design sequential circuits – e.g. counters**

Combinational vs. Sequential Circuits

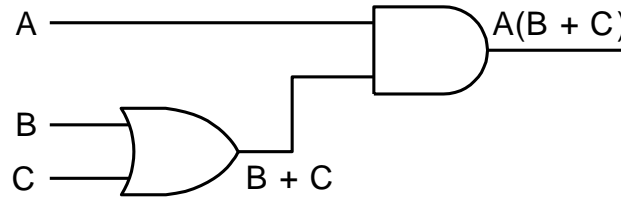
- **Combinational** Circuits (last week and earlier)
 - Logic gates only (no flip-flops)
 - Output is uniquely determined by the inputs
 - i.e. you'll always get the same output for a given set of inputs
 - Example:



- **Sequential** Circuits
 - Include flip-flops
 - Output determined by current inputs and current **state** (values in the flip-flops)
 - Output can change when clock 'ticks'

Sequential Circuits

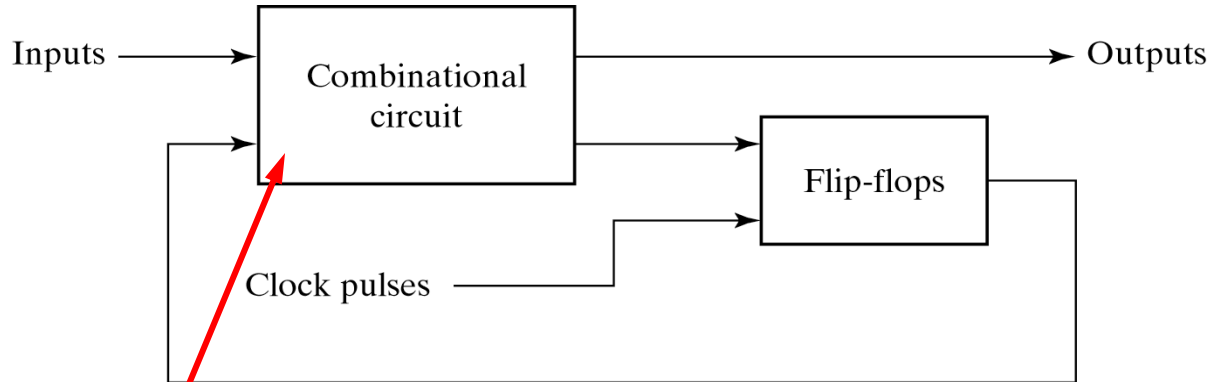- **State** = value stored in flip-flops
- There is a notion of **present state** and **next state**
- Output depends on input and state
 - Or sometimes just the state
- Next state depends on inputs and state




Logic Gates

[Figure from Mano, "Digital Design", 3rd edition]

Synchronous Sequential Circuit

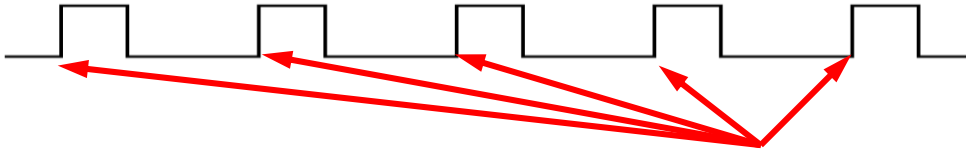- Storage elements (flip-flops) can only change at discrete instants of time
- Assume
 - We have a clock signal:




- Output of storage elements change only on the edges of control signal
 - (compare with logic gates whose output changes whenever the input changes)

In a synchronous sequential circuit, all the sequential elements share a common clock signal. i.e., they are synchronised to a common clock.

Registers

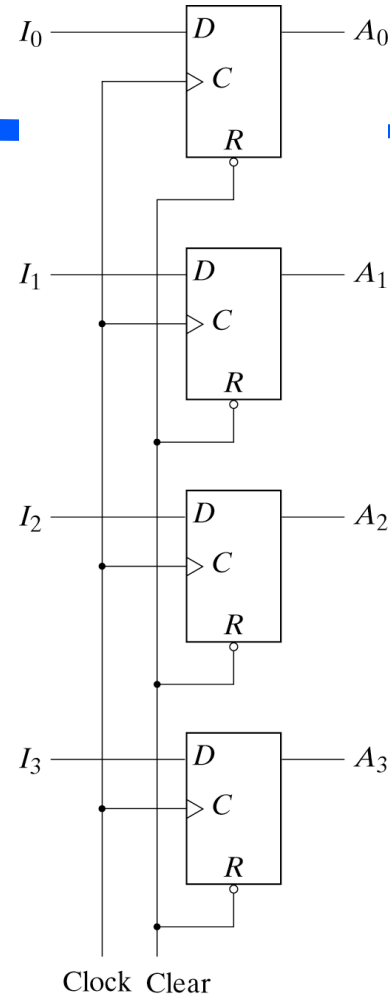- A **register** is a group of flip-flops
 - n -bit register consists of n flip-flops capable of storing n bits
- Example
 - 4-bit register
- A register is a sequential circuit *without* any combinational logic
- Registers are used to store binary information (data/instructions) inside a processor



[Mano,
Digital
Design,
3rd ed.]

Shift Register

- A shift register is a register which is capable of shifting its binary information in one or both directions
- Example:

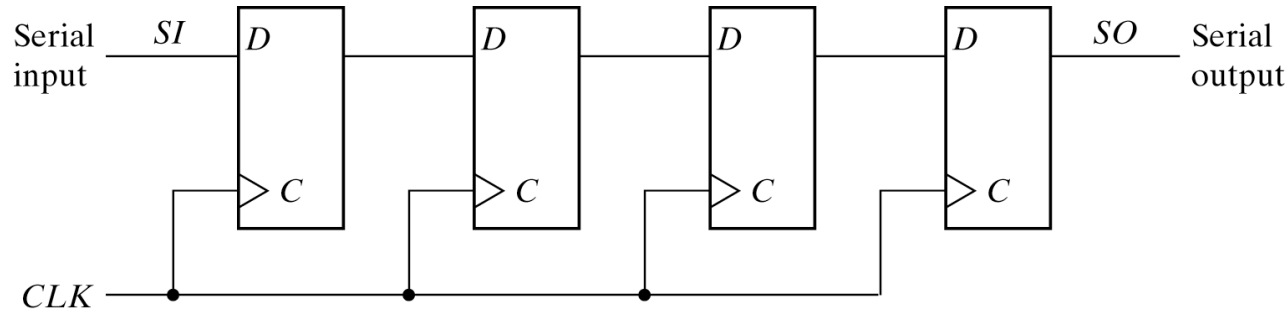


Fig. 6-3 4-Bit Shift Register


Serial ⇔ Parallel Conversion

- Shift registers can be used to do serial to parallel conversion (and vice-versa)
- *(Figure to be drawn in class)*

Parallel to Serial and Serial to Parallel


Short Break

- Stand up and stretch

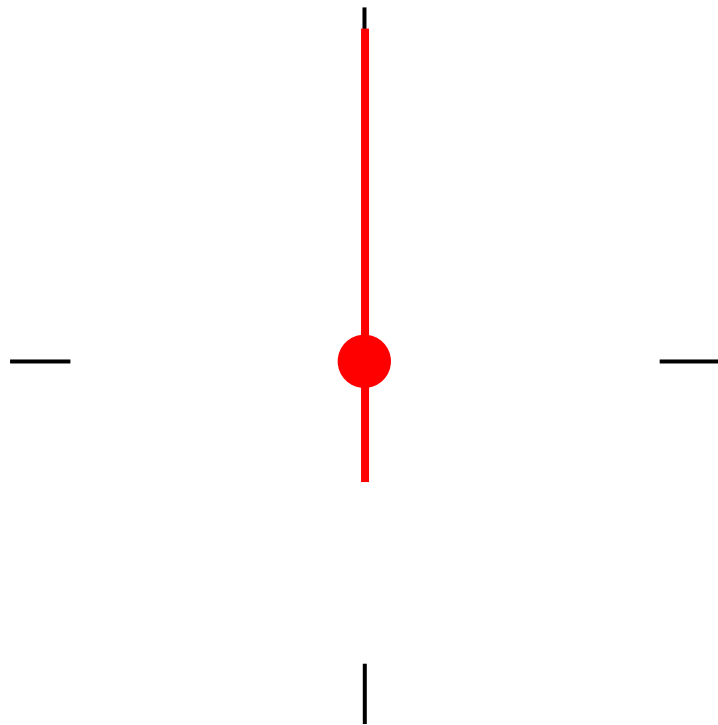

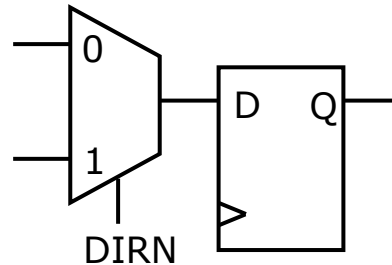Exercise: Bidirectional shift register

- Using same multiplexer concept, draw a 3-bit shift register which allows data to be shifted in either direction
- Hint: consider this element, where DIRN will be 0 for left shift, 1 for right shift



You have 2 minutes

Exercise:


Bidirectional shift register

- Using same multiplexer concept, draw a 3-bit shift register which allows data to be shifted in either direction

Universal Shift Register

8-bit Wide Shift Register

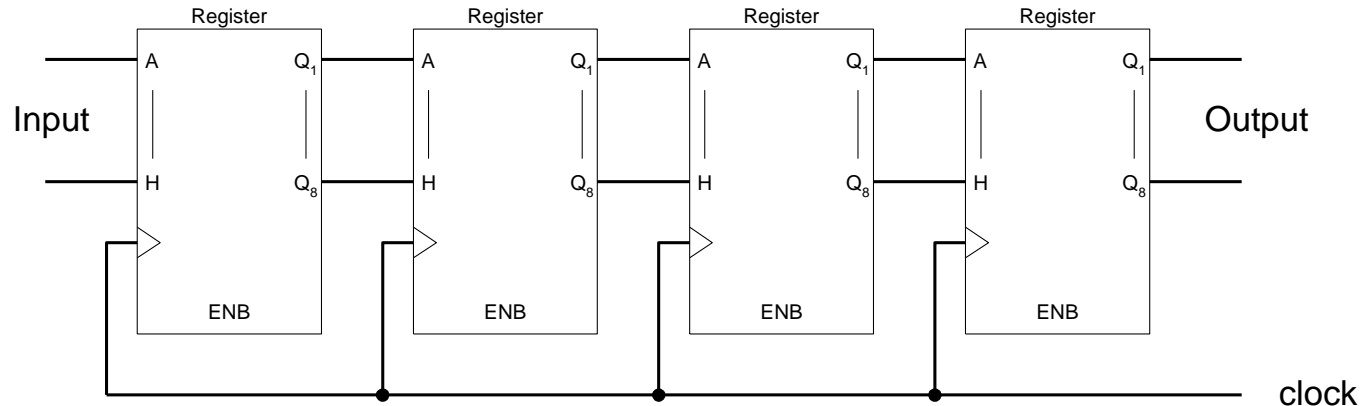- Multiple bits shifted at a time
- Example 4-stage 8-bit queue:



Lab 06 Preparation Task – to be discussed in class

Reminders

- Quiz 2 due Friday 4pm
- Lab 6/7 preparation tasks for next week