

CSSE2010/CSSE7201

Learning Lab 5



Logisim & Flip-flops

School of Information Technology and Electrical Engineering
The University of Queensland

Learning Lab 5 - Flip-flops

- Recall: there are two types of logic circuits. **Combinational** and **sequential**
- The basic building block of sequential circuits are flip flops (stores 1-bit of information)
- Today's lab: simulate circuits having D-flip flops using Logisim

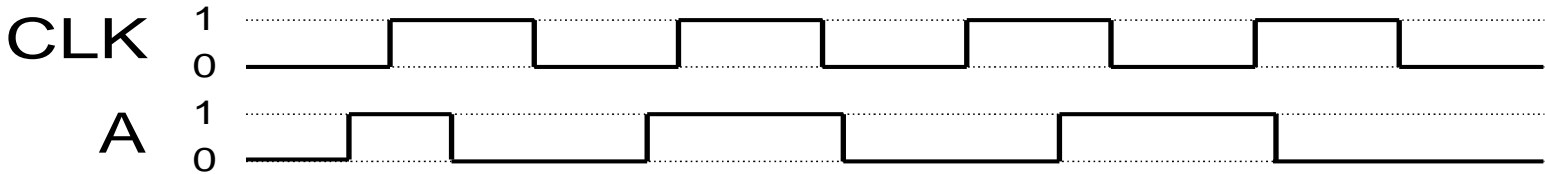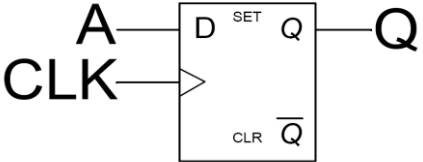
Which diagram captures the behaviour of this circuit?



- 0% (a)
- 0% (b)
- 0% (c)
- 0% (d)


Logisim

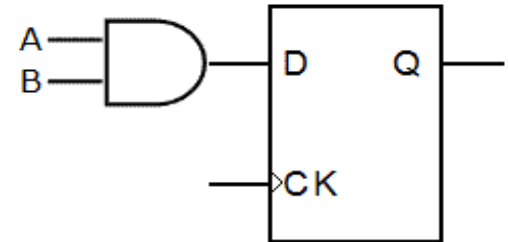- Go through the Logisim tutorial if you haven't done already
- 3 Tasks
- Draw and simulate
 1. A 2-input NOR gate
 2. An RS-Latch (two cross coupled NOR gates)
 3. A D-Flip-flop circuit:
 - Make sure you work out what all of the inputs on the Logisim D Flip-flop do



D-Flip-flop circuit

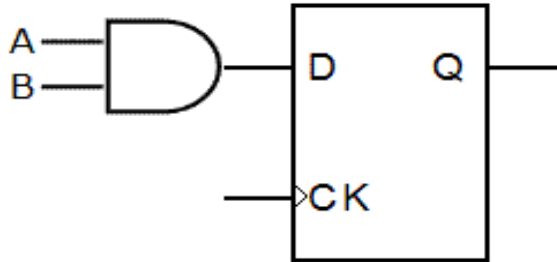- Consider Circuit (below)
- Draw a circuit schematic diagram that
 - Uses a 74HCT74 (and other chips as needed)
 - Uses pushbuttons for CLK (CK), PRE and CLR inputs
 - Consider inverters between buttons and PRE/CLR inputs. Why?
 - Uses switches for A and B inputs
 - Uses LEDs for Q and Q' outputs
- Have schematic checked by a tutor
- Build/simulate the circuit & test it



Latch circuit

- Design a latch out of cross-coupled NAND gates
- Predict its behaviour
 - How can you set it or reset it?
- Draw a circuit schematic
- Build/simulate it
- Test it