

CSSE2010 / CSSE7201 – Introduction to Computer Systems

Exercises – Week Two

Logic Gates and Functions

Exercises

Many of the problems below are taken from or based on questions in Tanenbaum, Structured Computer Organisation, 5th edition, Appendix A and Chapter 3. A number of questions are taken from “Digital Design”, 3rd edition by M. Morris Mano, Prentice-Hall, 2002.

1. Perform the following calculations on 8-bit two’s complement numbers.

$$\begin{array}{r}
 00101101 \\
 + 01101111 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 11111111 \\
 + 11111111 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 00000000 \\
 - 11111111 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 11110111 \\
 - 11110111 \\
 \hline
 \end{array}$$

Verify the results by converting the numbers to decimal.

2. Consider the following addition problems for 3-bit binary numbers in two’s complement. For each sum, state

- (a) Whether the sign bit of the result is 1.
- (b) Whether the low-order 3-bits are 0.
- (c) Whether an overflow occurred.

$$\begin{array}{r}
 000 \\
 + 001 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 000 \\
 + 111 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 111 \\
 + 110 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 100 \\
 + 111 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 100 \\
 + 100 \\
 \hline
 \end{array}$$

3. Show how a 4-input NOR gate and a 3-input XOR gate (i.e. the odd function) can be implemented with only
 - (a) 2 input NAND gates
 - (b) inverters and 2 input NOR gates
4. There are four possible Boolean functions of one variable (A). These are $X = 0$, $X = 1$, $X = A$ and $X = \bar{A}$.
 - (a) Write down the equations for the 16 possible functions of two variables (A, B).
 - (b) How many possible functions of three input variables exist? of n variables?
5. A *literal* in a Boolean function is a single variable (which may or may not be complemented). For example, in the function $F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$ there are 8 literals. In the equivalent function, $F = \bar{X}Y + XZ$, there are 4 literals. The literal count can be thought of as the number of gate inputs in a logic diagram representation of the function. Using Boolean algebra, modify each of the following functions to a logically equivalent function using as few literals as possible:
 - (a) $XY + X\bar{Y}$
 - (b) $(\bar{B}\bar{C} + \bar{A}D)(\bar{A}\bar{B} + \bar{C}\bar{D})$
 - (c) $\bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD)$
6. Given the Boolean function $F = X\bar{Y}Z + \bar{X}\bar{Y}Z + \bar{W}XY + W\bar{X}Y + WXY$
 - (a) Obtain the truth table of the function
 - (b) Draw the logic diagram using the original Boolean expression
 - (c) Simplify the function to a minimum number of literals using Boolean algebra
 - (d) Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part (a)
 - (e) Draw the logic diagram from the simplified expression and compare the total number of gates with the diagram of part (b)

7. Write a sum-of-products Boolean expression for the function defined by the following truth table. Draw the logic diagram equivalent also. Can you simplify the expression? If so, draw the equivalent logic diagram.

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

8. By using truth tables, prove
 (a) DeMorgan's laws for three variables: $\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$ and $\overline{A+B+C} = \overline{A}\overline{B}\overline{C}$
 (b) the distributive law: $A + BC = (A+B)(A+C)$
9. Find the complement of the following expressions:
 (a) $\overline{X}Y + X\overline{Y}$
 (b) $(A\overline{B} + C)\overline{D} + E$
10. Use a truth table to show that $P = PQ + P\overline{Q}$.
11. Using Boolean algebra, modify each of the following functions to a logically equivalent function using as few literals as possible:
 (a) $(X + Y)(X + \overline{Y})$
 (b) $(\overline{A} + C)(\overline{A} + \overline{C})(A + B + \overline{C}D)$
12. Write down the function table and draw the logic symbol for an 8-to-1 multiplexer. Draw a logic circuit which implements this function.
13. Show how a 4-to-1 multiplexer can be used to implement a 2-input XOR gate. (Hint: compare the function table of a 4-to-1 multiplexer with the truth table of a 2-input XOR gate, and consider how you can make them the same.) Is there any logic function of 2 variables which can NOT be implemented using a 4-to-1 multiplexer?
14. Write down a sum-of-products function representation of a full-adder's outputs in terms of its inputs. Draw the logic circuit equivalent. (This is an alternative way to build a full-adder instead of using two half-adders and an OR gate.)
15. A comparator is a circuit which compares two input words. Draw a logic diagram of a comparator which takes two 8-bit input words ($A_7A_6A_5A_4A_3A_2A_1A_0$ and $B_7B_6B_5B_4B_3B_2B_1B_0$) and produces a 1 if they are equal and 0 if they are not equal. (Hint: consider the two-input equivalence circuit shown in the lecture.)
16. Draw the logic diagram of a 2-bit encoder, a circuit with four input lines, exactly one of which is high at any instant, and two output lines whose 2-bit binary value tells which input is high.
17. Implement a full adder with two 4-to-1 multiplexers.