

Welcome!

CSSE2010/CSSE7201

Learning Lab 7

Counter Circuits

<http://responsewaresg.net>

Session ID: CSSE2010EXT

School of Information Technology and Electrical Engineering
The University of Queensland


Today

- Counter Circuits
 - Review of Preparation Task
 - Polling questions
 - Design
 - Build and test or Simulation (Logisim)
- Don't forget preset/clear inputs on flip-flops


Peer Review of Circuit Schematics

- Check the circuit schematic
 - Naming of inputs and outputs
 - Identification of chips (U1, U2 etc) and gates within chips where applicable (:A, :B etc)
 - Identification of types of chips (74HCT00 etc.)
 - Numbering of pins (including for IO board)
 - Power supply connections
 - ✓ ■ **Circuit functionality – will it do what was asked?**
- Check schematic guide and device pinouts on Blackboard for more detail
- Ask a tutor if necessary
- Online sessions – talk to other people in your breakout room and discuss among yourselves and make sure you have a correct design on paper

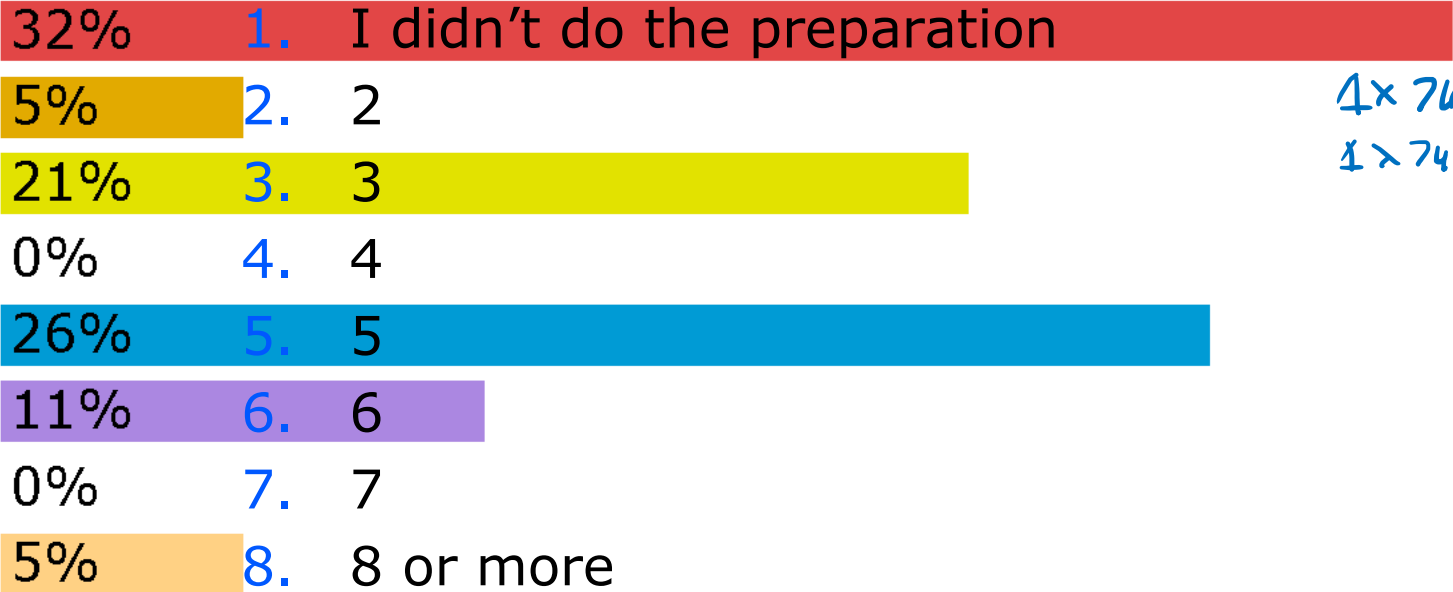Preparation Survey: How many 74 series logic chips did your circuit schematic use?



 4x 74HC175 Quad DPM
1x 74HC86 Quad XOR gate



Prep Task

Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	0	1	1
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	1
1	0	1	<u>X</u>	X	X
1	1	0	1	0	0
1	1	1	0	0	0

$$\begin{aligned}
 D_2 &= \bar{Q}_2 \bar{Q}_1 Q_0 + \bar{Q}_2 Q_1 \bar{Q}_0 + Q_2 Q_1 \bar{Q}_0 + Q_2 \bar{Q}_1 Q_0 \\
 &= \bar{Q}_2 (\bar{Q}_1 Q_0 + Q_1 \bar{Q}_0) + Q_2 (Q_1 \bar{Q}_0 + \bar{Q}_1 Q_0) \\
 &= \bar{Q}_2 (Q_1 \oplus Q_0) + Q_2 (Q_1 \oplus Q_0) \\
 &= (Q_1 \oplus Q_0) (\bar{Q}_2 + Q_2) = Q_1 \oplus Q_0 \\
 &= \bar{Q}_2 (Q_1 \oplus Q_0) + Q_2 \bar{Q}_0
 \end{aligned}$$

$$\begin{aligned}
 D_1 &= \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 + \bar{Q}_2 \bar{Q}_1 Q_0 + \bar{Q}_2 Q_1 \bar{Q}_0 + \bar{Q}_2 Q_1 Q_0 \\
 &= \bar{Q}_2 (\bar{Q}_1 \bar{Q}_0 + \bar{Q}_1 Q_0 + Q_1 \bar{Q}_0 + Q_1 Q_0) \\
 &= \bar{Q}_2 (\bar{Q}_1 (\bar{Q}_0 + Q_0) + Q_1 (\bar{Q}_0 + Q_0)) \\
 &= \bar{Q}_2
 \end{aligned}$$

Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	0	1	1
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	1
1	0	1	x	x	x
1	1	0	1	0	0
1	1	1	0	0	0



NAND





AND

$$\begin{aligned}
 D_0 &= \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 + \bar{Q}_2 \bar{Q}_1 Q_0 + Q_2 \bar{Q}_1 \bar{Q}_0 + Q_2 \bar{Q}_1 Q_0 \\
 &= \bar{Q}_2 \bar{Q}_1 (\bar{Q}_0 + Q_0) + Q_2 \bar{Q}_1 (\bar{Q}_0 + Q_0) \\
 &= \bar{Q}_2 \bar{Q}_1 + Q_2 \bar{Q}_1 = \bar{Q}_1 \rightarrow 1 \text{ XOR gate}
 \end{aligned}$$

$$D_1 = \bar{Q}_2 \rightarrow 1 \text{ XOR gate}$$

$$D_2 = Q_1 \oplus Q_0 \rightarrow 1 \text{ XOR gate operation}$$


A	B	\oplus
0	0	0
0	1	1
1	0	1
1	1	0

  

Which of the following best describes the behaviour of a 2-bit up/down binary counter? (U is an input)

- 0%
- ✓ 100%
- 0%
- 0%
- 0%
1. U=1: Q_1Q_0 : 00→01→10→11→00
U=0: Q_1Q_0 : 00→01→10→11→00
2. U=1: Q_1Q_0 : 00→01→10→11→00 ✓
U=0: Q_1Q_0 : 00→11→10→01→00 ✓
3. U=1: Q_1Q_0 : 00→11→10→01→00
U=0: Q_1Q_0 : 00→01→11→10→00
4. U=1: Q_1Q_0 : 00→01→10→11→00
U=0: Q_1Q_0 : 00→10→11→01→00
5. I don't know

U=1 → count up
U=0 → count down

 

Up/Down Counter

- Complete the truth table for a 2 bit up/down binary counter
 - (U=1 counts up, U=0 counts down)✓
- Work out logic functions for D1 and D0 in terms of U, Q1, Q0
 - Sum of products✓
 - Simpler expression?✓

Down {

Up {

Input	Current State		Next State	
U	Q1	Q0	D1	D0
0	0	0	1	1
0	1	0	0	0
0	2	1	0	1
0	3	1	1	0
1	0	0	1	1
1	1	0	2	0
1	2	1	3	1
1	3	1	0	0

Input	Current State		Next State	
U	Q1	Q0	D1	D0
0	0	0	3	1
0	1	0	0	0
0	2	1	1	1
0	3	1	2	0
1	0	0	1	1
1	1	0	2	0
1	2	1	3	1
1	3	1	0	0


$$\begin{aligned}
 D_1 &= \bar{U} \bar{Q}_1 \bar{Q}_0 + \bar{U} Q_1 Q_0 + U \bar{Q}_1 Q_0 + U Q_1 \bar{Q}_0 \\
 &= \bar{U} (\underbrace{\bar{Q}_1 \bar{Q}_0 + Q_1 Q_0}_{\text{XOR}}) + U (\underbrace{\bar{Q}_1 Q_0 + Q_1 \bar{Q}_0}_{\text{XOR}}) \\
 &= \bar{U} (\overline{Q_1 \oplus Q_0}) + U (Q_1 \oplus Q_0) \\
 &= \overline{U \oplus (Q_1 \oplus Q_0)} = \overline{U \oplus Q_1 \oplus Q_0}
 \end{aligned}$$

$$D_0 = \bar{Q}_0 \text{ by inspection}$$


$$\begin{aligned}
 D_0 &= \bar{U} \bar{Q}_1 \bar{Q}_0 + \bar{U} Q_1 \bar{Q}_0 + U \bar{Q}_1 \bar{Q}_0 + U Q_1 \bar{Q}_0 \\
 &= \bar{U} \bar{Q}_0 (\cancel{\bar{Q}_1 + Q_1}) + U \bar{Q}_0 (\cancel{\bar{Q}_1 + Q_1}) \\
 &= \bar{U} \bar{Q}_0 + U \bar{Q}_0 \\
 &= \bar{Q}_0 (\bar{U} + U) \\
 &= \bar{Q}_0
 \end{aligned}$$

Consider a 4-bit up/down counter built out of a 4-bit adder (e.g. 74HCT283) and 4 flip-flops (e.g. 74HCT175)

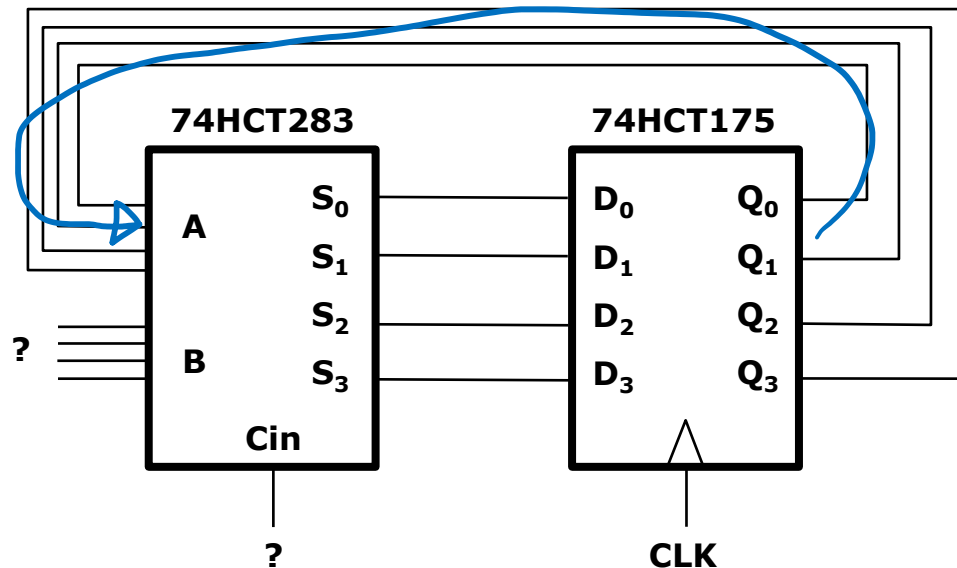- Adder output is connected to flip-flop inputs ✓
 - Current count (flip-flop outputs) connected to one 4-bit adder input (A) ✓
 - What needs to be on the other 4-bit adder input (B) & Cin?
 - When counting up? ✓
 - When counting down? ✓
- Clicker question



 If Cin is 0, what needs to be on the B input?



5%	1. Up: 1000	Down: 0001
5%	2. Up: 0001	Down: 1000
74%	3. Up: 0001	Down: 1111
5%	4. Up: 1111	Down: 0001
11%	5. Up: 0001	Down: 1110
0%	6. Up: 0001	Down: 0001

unsigned

5: 0 0 0 1

+ 15: + 1 1 1 1
20: 0 1 0 0 = 4

0

Tasks

- 4 bit up/down counter built from 4-bit adder
 - Draw the circuit in Logisim
 - Use the “Adder” component ✓
 - Work out how splitters work for wiring ✓
 - Simulate it & verify behaviour is as expected ✓
 - Draw a circuit schematic diagram
 - Use button for clock, switch for up/down input ✓
 - Have it checked by a tutor then build & test it
- Build/simulate your preparation task 3-bit counter and test it ✓
- Draw a circuit schematic for your 2-bit up/down counter
 - Test this 2-bit up/down counter either in simulation or by building the circuit ✓