

**CSSE2010 / CSSE7201**  
**Lecture 3** ✓

**Binary Arithmetic**

School of Information Technology and Electrical Engineering  
The University of Queensland

# Today...


- Admin
- Recap on signed number representations in binary
- Logic gates revisited – from previous lecture
- Binary Arithmetic
- Arithmetic Circuits
- Questions: please put them on to the padlet and I will answer them after the lecture

# Admin

- ✓ Contact [eait.mytimetable@uq.edu.au](mailto:eait.mytimetable@uq.edu.au) if not yet signed up or you're unable to attend the labs you are signed on to
- Two lab sessions per week from this week. Refer to week-by-week teaching outline on Blackboard.
- ✓ All labs are now online due to SEQ lockdown. Zoom information is on Blackboard.
- ✓ Weekly exercises (not assessed) are available on Blackboard
- ✓ Quiz 1 – due this week Friday 4pm. Single attempt and need to submit (not auto submitted)

# Quick Recap – Week 1 Lectures & Learning Lab

## Number bases

 

## Binary Formats

$2^{N-1}$	$2^{N-2}$	$2^1$	$2^0$	Excess- $2^{N-1}$	$-2^{N-1} \leq x \leq (2^{N-1} - 1)$
$-2^{N-1}$	$2^{N-2}$	$2^1$	$2^0$	2's comp	$-2^{N-1} \leq x \leq (2^{N-1} - 1)$
$-2^{N-1}-1$	$2^{N-2}$	$2^1$	$2^0$	1's comp	$-(2^{N-1} - 1) \leq x \leq (2^{N-1} - 1)$
$\pm$ No mag.	$2^{N-2}$	$2^1$	$2^0$	Sign-Mag	$-(2^{N-1} - 1) \leq x \leq (2^{N-1} - 1)$
$2^{N-1}$	$2^{N-2}$	$2^1$	$2^0$	Unsigned	$0 \leq x \leq 2^N - 1$
<div>MSB</div>	<div>...</div>	<div>LSB</div>			

## Logic Gates

NOT, AND, OR, XOR, NAND, NOR, XNOR  
Symbols, Truth table, Boolean expression

Logic diagrams, schematic diagrams  
Logic expressions, SOP, Simplification using Boolean algebra

What is -32 (base 10) expressed in  
**8-bit signed magnitude format?**

94%

A. 10100000 ✓

1%

B. 10100001

1%

C. 11011111

1%

D. 11100000

1%

E. I don't know

# What is -32 (base 10) expressed in 8-bit two's complement format?

6%

A. 10100000

28%

B. 11011111

8%


C. 10100001

59%

✓ D. 11100000 ✓

0%







E. I don't know

 
      
# Equivalent Circuits









- All circuits can be constructed from NAND or NOR gates
  - These are called **complete** gates
- Examples:



- Reason: Easier to build NAND and NOR gates from transistors
      
# Which of the following is a NOR only implementation of





# Binary Arithmetic

- Addition is quite simple in binary
- We shall see circuits that implement the addition operation later

Addend	0	0	1	1
Augend	+0	+1	+0	+1
Sum	0	1 ✓	1 ✓	0 ✓
Carry	0	0 ✓	0 ✓	1 ✓

✓  
 ↶  
 1  
 10

- Above ignores carry in

# Binary Addition

Decimal	8-bit Unsigned
10 ✓	00001010
+ 243 ✓	+ 11110011 } +
<hr/>	
253 ✓	1111101 ✓

Decimal	8-bit 2's complement
10 ✓	00001010
+ (-13) ✓	+ 11110011 } +
<hr/>	
-3 ✓	1111101 ✓

1's comp  
= 10100  
0111...  
XXXXX

- Format matters when you interpret the numbers
- Whatever the format is the bit-wise addition (which leads to the hardware circuit we will be looking at) is the same
- **Two's complement** – you don't need to do anything with the carry out from the MSB to get the correct result
- But in **one's complement** you will **have to add the carry out from the MSB back to the result** to get the correct answer – this is one drawback of one's complement representation – check by yourself


-2 ?

0000010  
0000011

3

# Short Break

- Stand up and stretch

 

# Overflow in Binary Addition

**Decimal**

$$\begin{array}{r} 15 \\ + 243 \\ \hline 258 \end{array}$$

**8-bit Unsigned**

$$\begin{array}{r} 00001111 \\ + 11110011 \\ \hline 10000010 \end{array}$$

Handwritten notes:   
 - Red circle around "8-bit Unsigned"   
 - Red bracket and "+" sign next to the second binary number   
 - Green circle around the result   
 - Red "1" in a box next to the MSB of the result   
 - Red arrow pointing to the MSB with text "Carry out for MSB"   
 - Red "255" written next to the result

**Decimal**

$$\begin{array}{r} 125 \\ + 4 \\ \hline 129 \end{array}$$

**8-bit 2's complement**

$$\begin{array}{r} 01111101 \\ + 00000100 \\ \hline 10000001 \end{array}$$

Handwritten notes:   
 - Green circle around "8-bit 2's complement"   
 - Green bracket and "+" sign next to the second binary number   
 - Green circle around the result   
 - Green "1" in a box next to the MSB of the result   
 - Green arrow pointing to the MSB with text "Carry in to MSB"   
 - Green "127" written next to the result   
 - Green "125 + 4" written next to the result   
 - Green "127" written next to the result   
 - Green "128" written next to the result   
 - Green "127" written next to the result

**Overflow: Not enough bits to represent the answer. The result goes out of range. Thus, you get a wrong answer.**

**How is overflow detected:**

☒ **Unsigned:** carry-out from the MSB → overflow

☒ **2's comp:** carry-in to the MSB and carry-out from the MSB are different → overflow

☐ Equivalently, overflow occurs if (in 2's comp)

☒ Two negatives added together give a positive, or

☐ Two positives added together give a negative

$$\text{overflow} = C_{in} \oplus C_{out}$$

What is the result of adding the two 6-bit two's complement numbers **110101** and **001111** in 6-bits?

73% **A. 000100** ✓

3% **B. 000101**

2% **C. 001010**

6% **D. 111010**

16% **E. 1000100**

$$\begin{array}{r} \boxed{1} \ 1 \ 1 \ 1 \ 1 \\ 1 \ 1 \ 0 \ 1 \ 0 \ 1 \\ 0 \ 0 \ 1 \ 1 \ 1 \ 1 \\ \hline \boxed{1} \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \end{array}$$

⇒ No overflow.

# What's the truth table for an adder?

Inputs = A, B

Outputs = S(Sum), C(Carry)

1.

A	B	C	S
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

2.


A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

3.

A	B	C	S
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0


4.

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


 
# Binary Addition

- A device which adds 2 bits (with no carry-in) is called a **half-adder**


  
# Binary Addition

- We have to deal with carry-in. There might be a carry-in from the previous stage.





# Addition of Binary Words


- Have to be able to deal with carry-in
- Truth table to be completed in class

A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

ODD

$$A \oplus B \oplus Cin$$

# Full Adder

 

$$S = A \oplus B \oplus C_{in}$$



$$C_{out} = AB + C_{in}(A \oplus B)$$

# Binary Adder

- Can cascade full adders to make binary adder
  - Example: for 4 bits...

$A - B$

 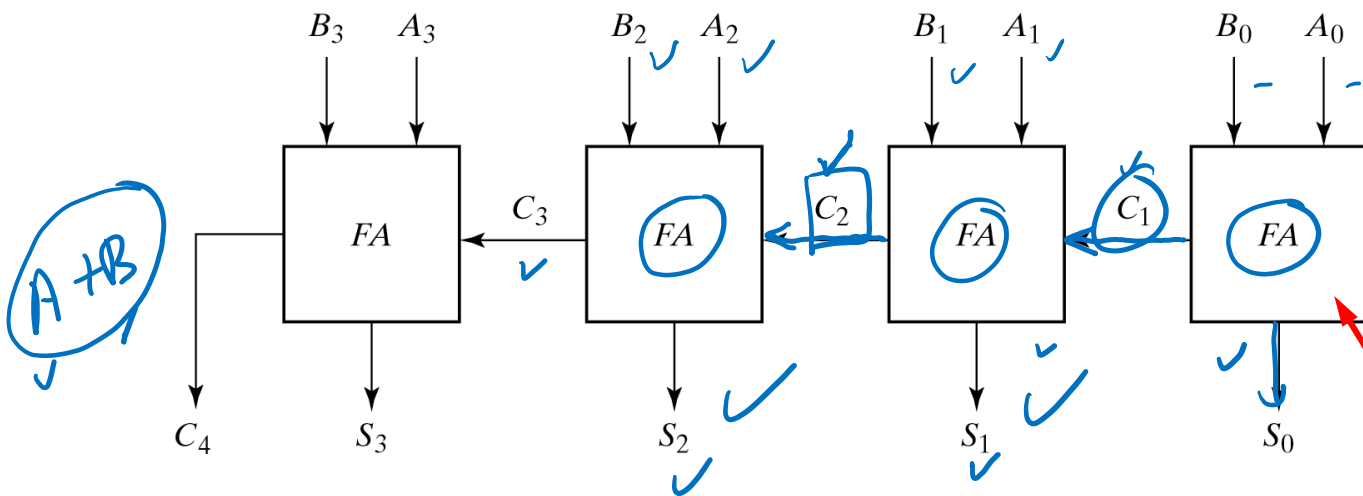For addition  
initial carry-in  
will be 0



- This is a **ripple-carry adder**

4 bit adder.

Full-adders

# Reminders for this week

- Lab classes
  - Mon-Tue: Lab 2 (Logic Gates) ✓
  - Wed-Fri: Lab 3 (Binary Arithmetic) ✓
- ✓ ● Quiz due this week Friday 4pm
- This week's labs
  - ≡ – IN students: if you have borrowed kits then use the kits. Otherwise use the Logisim software to simulate the logic circuits.
  - EX students: Use Logisim software to simulate the logic circuits. Start acquiring Arduino based hardware required in week 6.