

CSSE2010/CSSE7201

Lecture 8

Sequential Circuits 3

State Machines



School of Information Technology and Electrical Engineering
The University of Queensland

Outline


- Admin
- State machines
 - State diagrams
 - State tables
 - State encoding

Admin


- Quiz 3 is due on Friday 4pm this week

Sequential Circuits

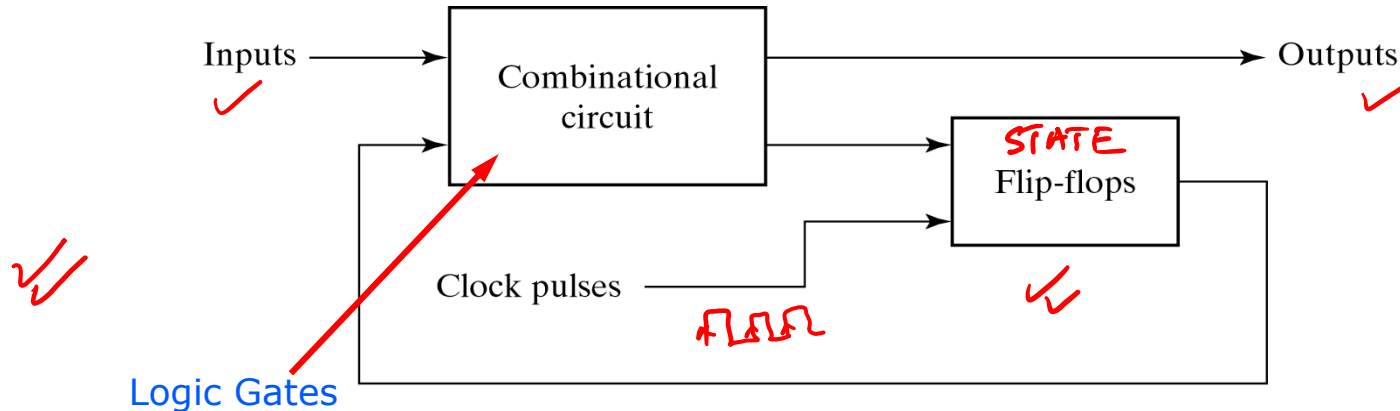- **State** = value stored in flip-flops
- Output depends on input and state
- Next state depends on inputs and state




State Machines

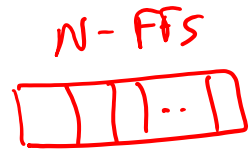

- Sequential circuits can also be called
 - state machines
 - finite state machines (FSMs)
- State machine has
 - Finite number of possible states
 - Only one **current state**
 - Can **transition** to other states based on inputs and current state

N -FFS
 $= 2^N$ possible states

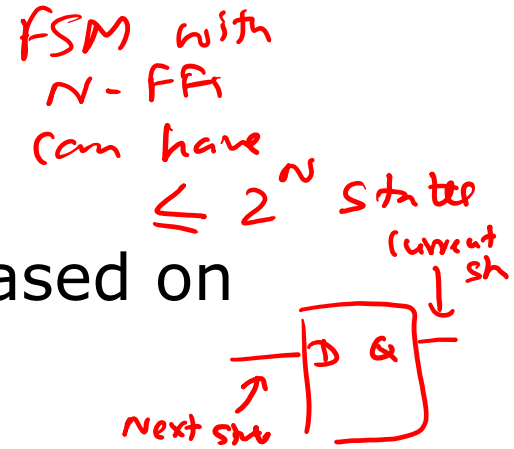

State Machines

- The states can be defined based on the problem:

✓ E.g. a vending machine accepting 5 cents and 10 cents coins to dispense a candy when it receives 15 cents in total. What can be the different states?

11

0

5

10

15

✓

State \equiv Money received so far

$$2^2 = 4$$

Types of State Machines

FSM

Two types

~~Mealy machines~~ ✓✓



- Outputs depend on current state and inputs

~~Moore machines~~ ✓

- Outputs depend only on current state (flip-flop values)


- Outputs can only change when state changes

discards only this

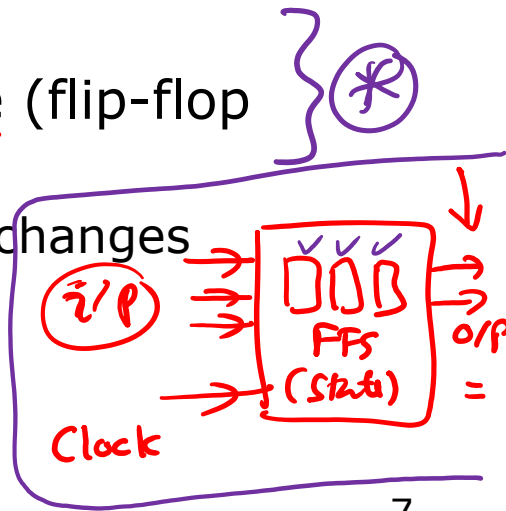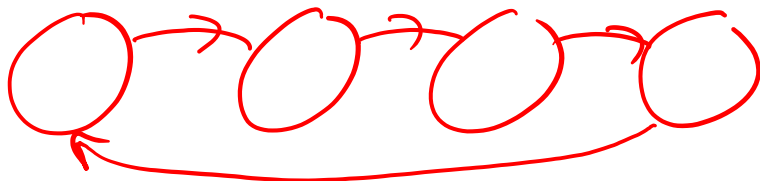


Moore vs Mealy Machine

Mealy Machine

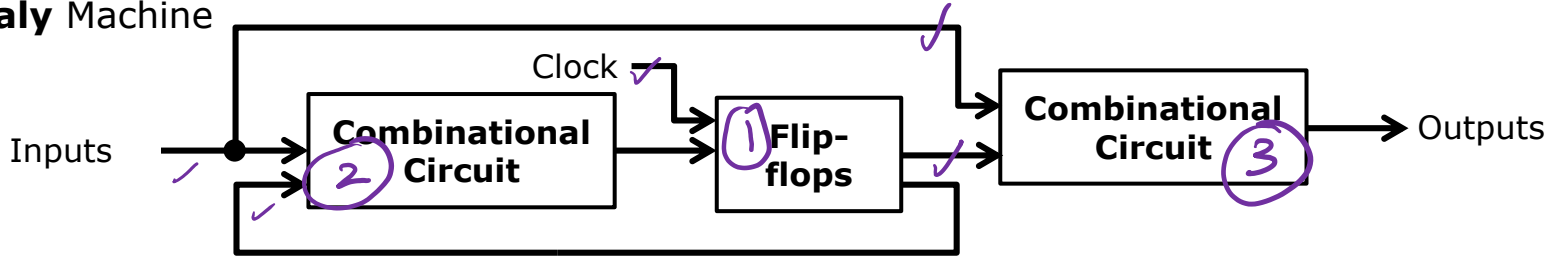

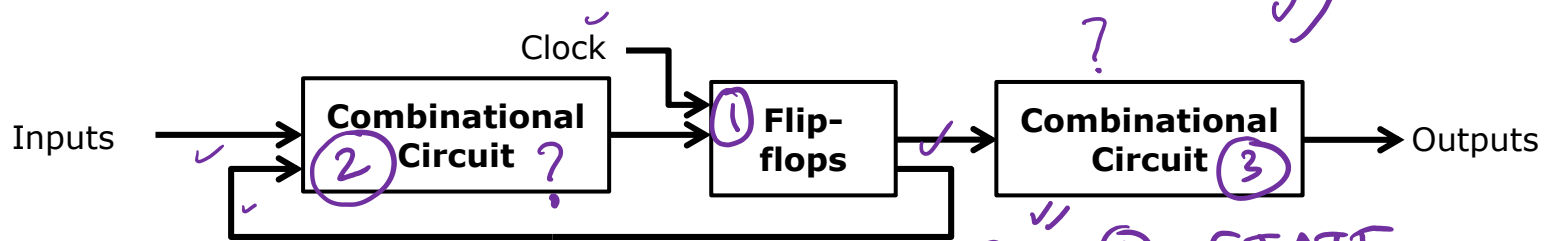Moore Machine – special case of a Mealy Machine



we only discuss this.

① STATE
② State transition logic
③ Output logic



We'll stick to Moore machines in this course

2

State Diagram

- To be illustrated in class

2 state lock

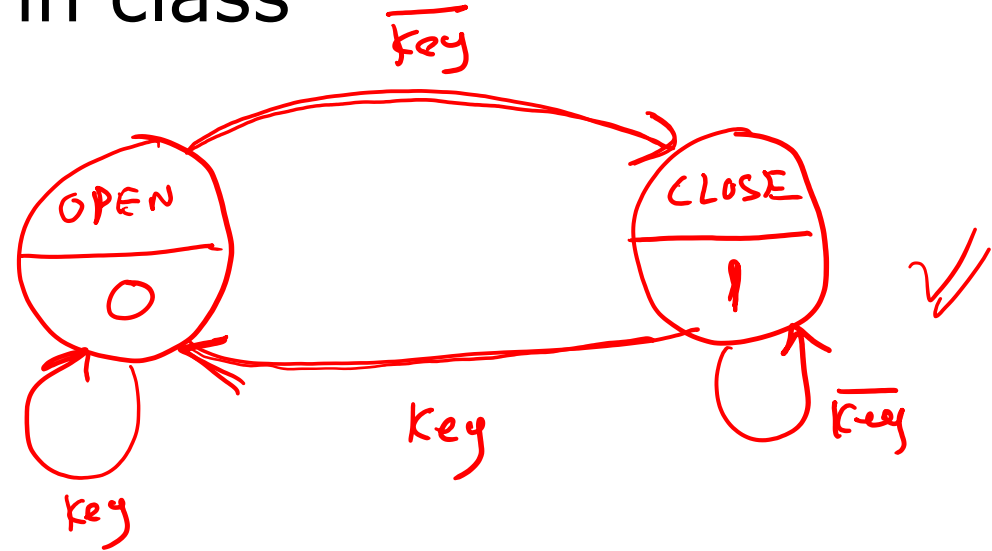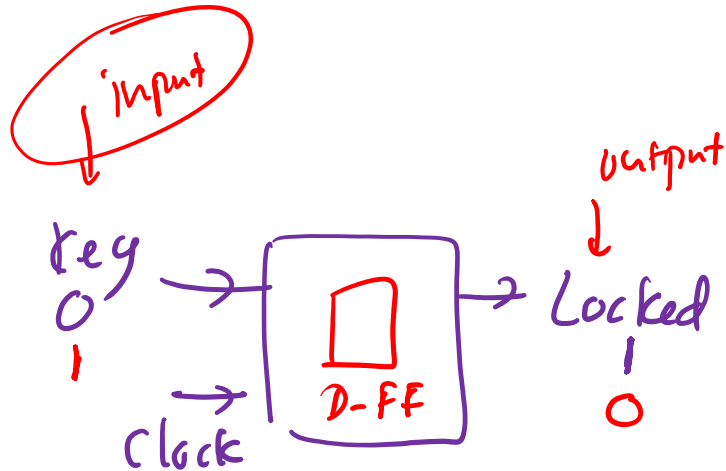


o/p inside the state → "Moore"



State Diagram (cont.)

● Notation

■ State

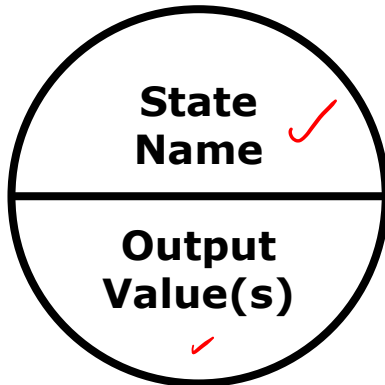


Examples:

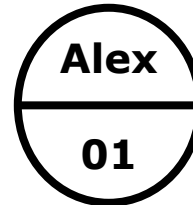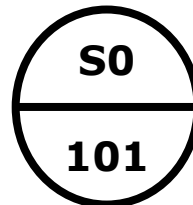

■ Transition

Logic expression →



or

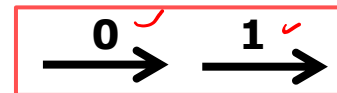

**Special case
for only one
input**

- If expression is true, state transition is made
- No label means "true" – i.e. always transition


● Examples

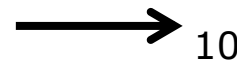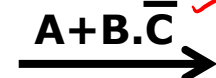

10

Example – to be worked out in class

- Binary counter with 2-bit output

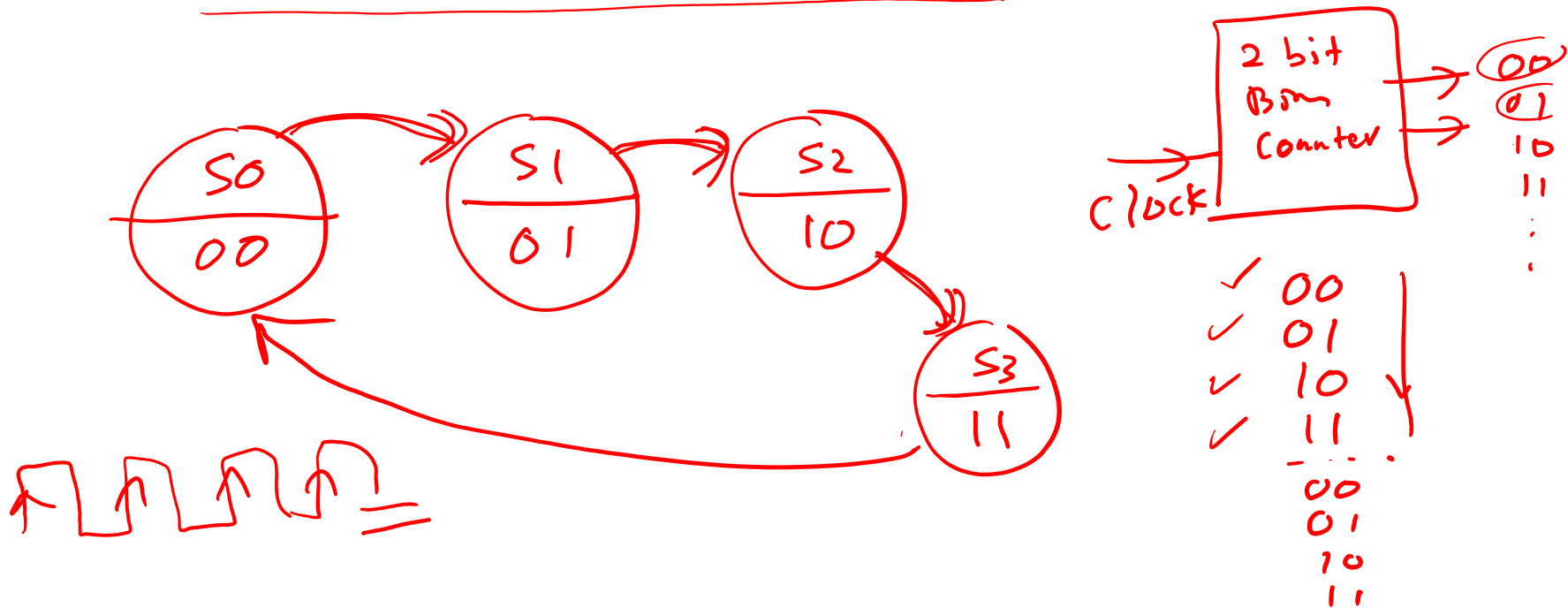


Example


● Binary up/down counter with 2-bit output

■ One input: U

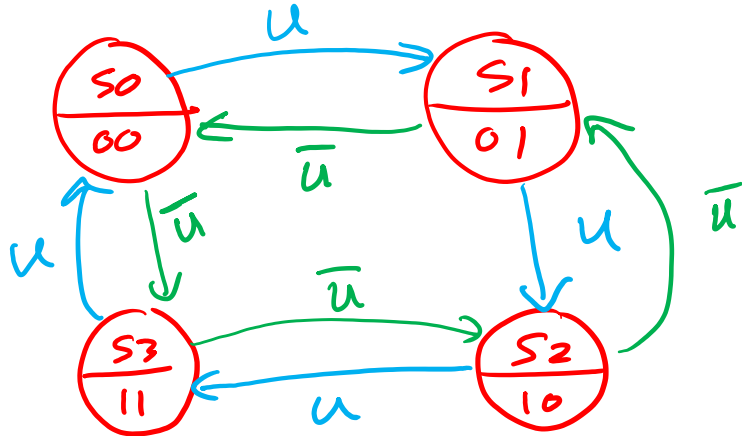- ✓ ● 1 means count up
- ✓ ● 0 means count down



"complete"

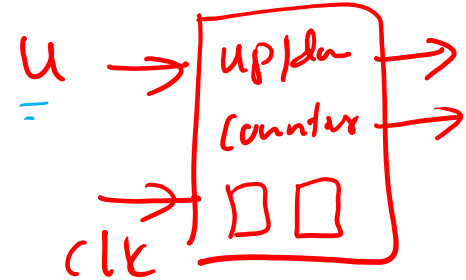





✓ 00	11
✓ 01	10
✓ 10	01
11	00
✓ U=1	U=0
==	==



Example

- Binary up/down counter with 2-bit output

- Two Inputs: U,D

-  $U=1, D=0$ means count up ✓
-  $U=1, D=1$ means set to 11 ✓

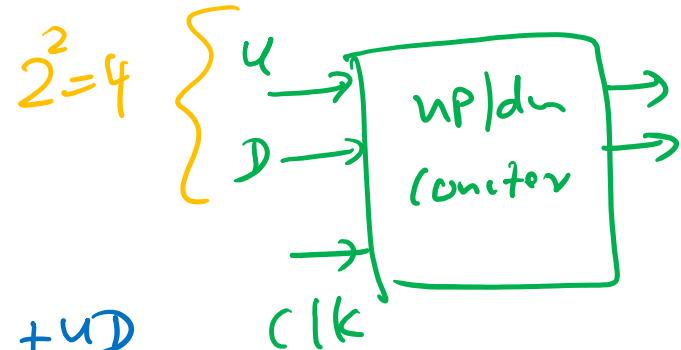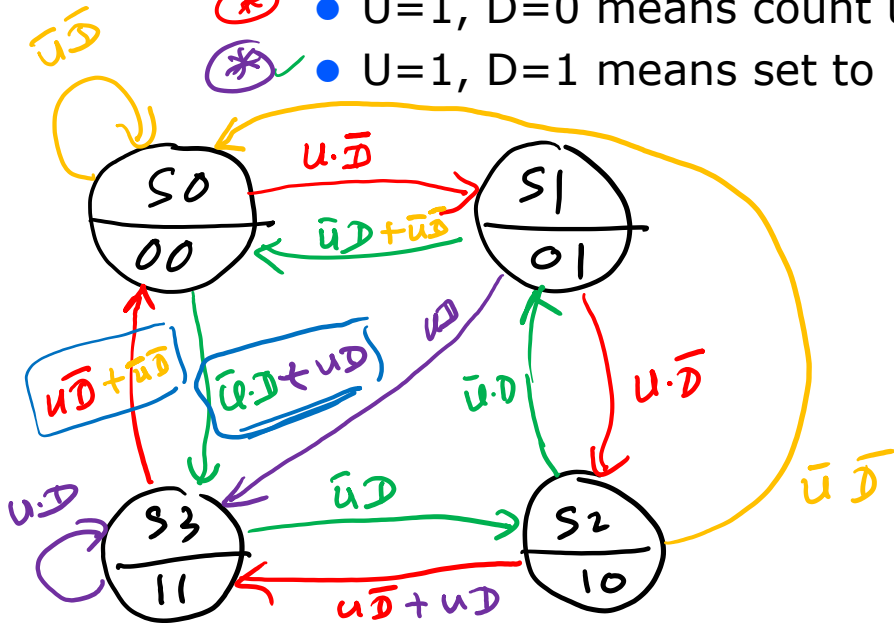-  $U=0, D=1$ means count down ✓
-  $U=0, D=0$ means reset to 00 ✓



$$\bar{U}D + UD$$

$$D(U + \bar{U}) = \underline{\underline{D}}$$

- Binary up/down counter with 2-bit output
 - U=1, D=0 means count up
 - U=0, D=1 means count down
 - U=1, D=1 means set to 11
 - U=0, D=0 means reset to 00



Completeness

- Each possible combination of inputs should be addressed exactly once for each state
 - i.e. transition arrows from each state must encompass all possibilities (exactly once)
- Example:

$$\begin{array}{cc}
 \begin{array}{c} u\bar{D} \\ \hline 00 \\ 01 \\ 10 \\ 11 \end{array} & \begin{array}{c} \checkmark \\ \bar{u}\bar{D} \\ \bar{u}D \\ u\bar{D} \\ uD \end{array}
 \end{array}$$

3

State Table

- State diagrams can also be represented in a state table
- Example - binary up/down counter with 2-bit output and single input U (1 means up, 0 means down)
- One dimensional state table:

u=0
u=1

Current State *	Input U	Next State	Outputs	
			Q1	Q0
S0	0	S3	0	0
S0	1	S1	0	0
S1	0	S0	0	1
S1	1	S1 S2	0	1
S2	0	S1	1	0
S2	1	S3	1	0
S3	0	S2	1	1
S3	1	S0	1	1

1D

Every combination of state and inputs

00
01
10
11

3 State Table (cont.)

- Two-dimensional state table
- Same example ~~3~~

Every combination of inputs

Current State	Next State		Outputs	
	\bar{U} ✓	U ✓	Q1	Q0
S_0	S_3	S_1	0	0
S_1	S_0	S_2	0	1
S_2	S_1	S_3	1	0
S_3	S_2	S_0	1	1

2D
Format

One row per state

✓

✓

4

State encoding

50
51

- Must encode each state into flip-flop values
- Choose
 - Number of flip-flops
 - Bit patterns that represent each state
- Ideally
 - Choose state encoding to make combinational logic simple, for both
 - ✓ ● Output logic ✓
 - ✓ ● Next state logic ✓

{


 Binary encoding ✓

 Gray code encoding

 One-hot encoding
 }

Example


- Binary counter with 2-bit output

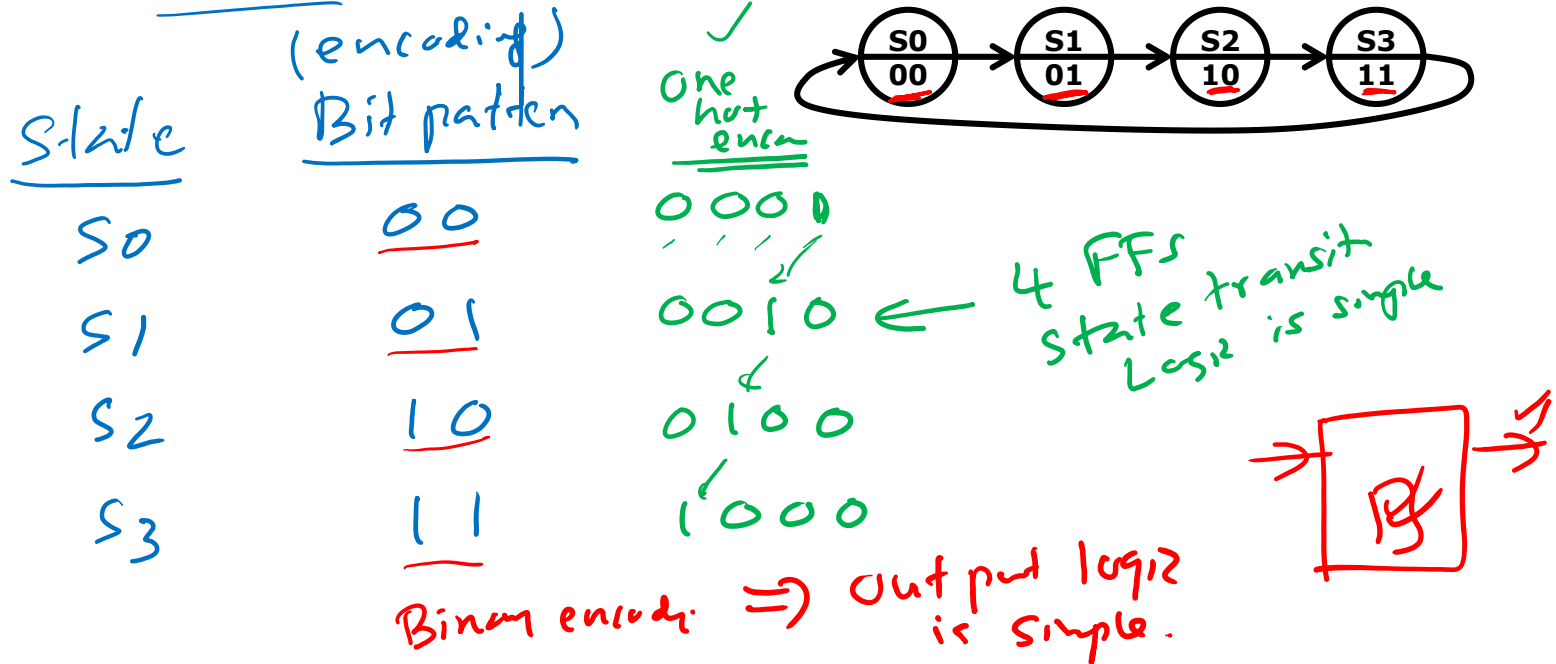

One-hot coding

- Use one flip-flop per state
- Only one flip-flop has 1 at any time
- Example – binary counter with 2-bit output

State	Q_3	Q_2	Q_1	Q_0	
S_0	0	0	0	1	0
S_1	0	0	1	0	1
S_2	0	1	0	0	2
S_3	1	0	0	0	3




Sequence Detector Example

- Design a state machine which detects the pattern 101 in an incoming bit stream and outputs a 1 whenever it detects this pattern

- Output is 1 for one clock cycle after the third digit is clocked in

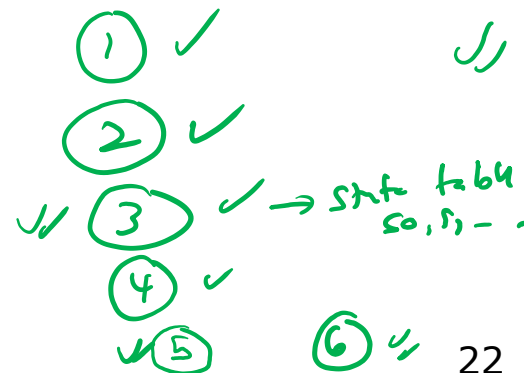Example:

- Input: 0010111010100
 - Output: 0000100010100



① → defining the states

② → Draw the state diagram (Moore)

③ → state table $\begin{matrix} ID \\ 2D \end{matrix}$ } still have state names e.g. S_0, S_1, \dots

④ → state encoding → i.e. binary, one-hot

⑤ → state table again with encoding.

⑥ → get the expressions for state trans & output
 & draw the logic diagram

⇒ watch the example for steps ⑤ & ⑥.

A pre-recorded example will be provided on Blackboard