

Welcome!

CSSE2010/CSSE7201

Learning Lab 4

Combinational Logic Circuits

School of Information Technology and Electrical Engineering
The University of Queensland

Learning Lab 4

Combinational Logic

- Complete the lab 4 preparation tasks.✓
- Make sure that you have correctly drawn circuit schematics for the 3 circuits mentioned in the preparation task.✓
- Get tutor help to verify your schematic diagrams.✓
- **IN students**: construct the circuits on breadboard and verify the functionality or use Logisim
- **EX students**: Create the circuits in Logisim and verify the functionality in simulation.✓

Circuit Construction Advice

- Try to keep circuits neat ✓
 - Use the shortest wires you can ✓
- Turn the power off before you change the circuit ✗
- Debugging
 - ✗ Use the logic probe (PR pin on the IO board)
 - Be systematic ✓
 - ✗ Check power/ground connections first
 - Start at the inputs, work towards outputs ✓
- **EX students:** keep your Logisim files organised as you will be doing this for ✓
the coming labs and you will need your files to revise things for assignment 1.
- **IN students:** You may take photos/videos of your circuit before disconnecting
as this might help you to revise things for your lab assignment 1. If you don't
have a kit, use Logisim and keep your design files organised.



For Each Circuit

- ✓ ● Make sure you have a correct schematic before you build ✓
- ✓ ● ^{Slack} Decide your test procedure – what truth table are you expecting?
- ✓ ● Build/simulate your circuit
- ✓ ● Test systematically

Don't expect things to always work in the first instance. If things don't work, troubleshoot systematically. Troubleshooting is also a part of your learning. A neatly drawn circuit schematic will always help when troubleshooting.

Circuit Construction Advice

- Try to keep circuits neat
 - Use the shortest wires you can
- Turn the power off before you change the circuit
- Debugging
 - Use the logic probe (PR pin on the IO board)
 - Be systematic
 - Check power/ground connections first
 - Start at the inputs, work towards outputs