

CSSE2010/CSSE7201
Lecture 10A

Memory and CPU
Control Unit

School of Information Technology and Electrical Engineering
The University of Queensland


Outline

- Admin
- Main Memory
- Fetch-Decode-Execute Cycle
- Controlling the CPU

Admin


- Week 5 labs:
 - Tuesday – Lab 8 (state machines)
 - **Thursday/Friday – Catch up labs**
- Assignment 1:
 - **Part 1:** Timed 1-hour quiz, single attempt, 25 MCQs, must be completed before **Friday 3 Sep 4:00PM AEST**. Practice material: past mid-semester exams and practice test. Non-invigilated and open book.
 - **Part 2:** Design and Logisim simulation of a digital circuit. Submission due on **Monday 6 Sep 4:00 PM AEST**. Blackboard submission only.
- Week 6 – no new labs. You are supposed to work on assignment 1 during whole week 6. Get tutor support during lab sessions to clarify any doubts.
- Quiz 4 is due this week Friday 27 Aug 2021 4:00PM AEST
- No Quiz on week 6

Where Are We Heading To?

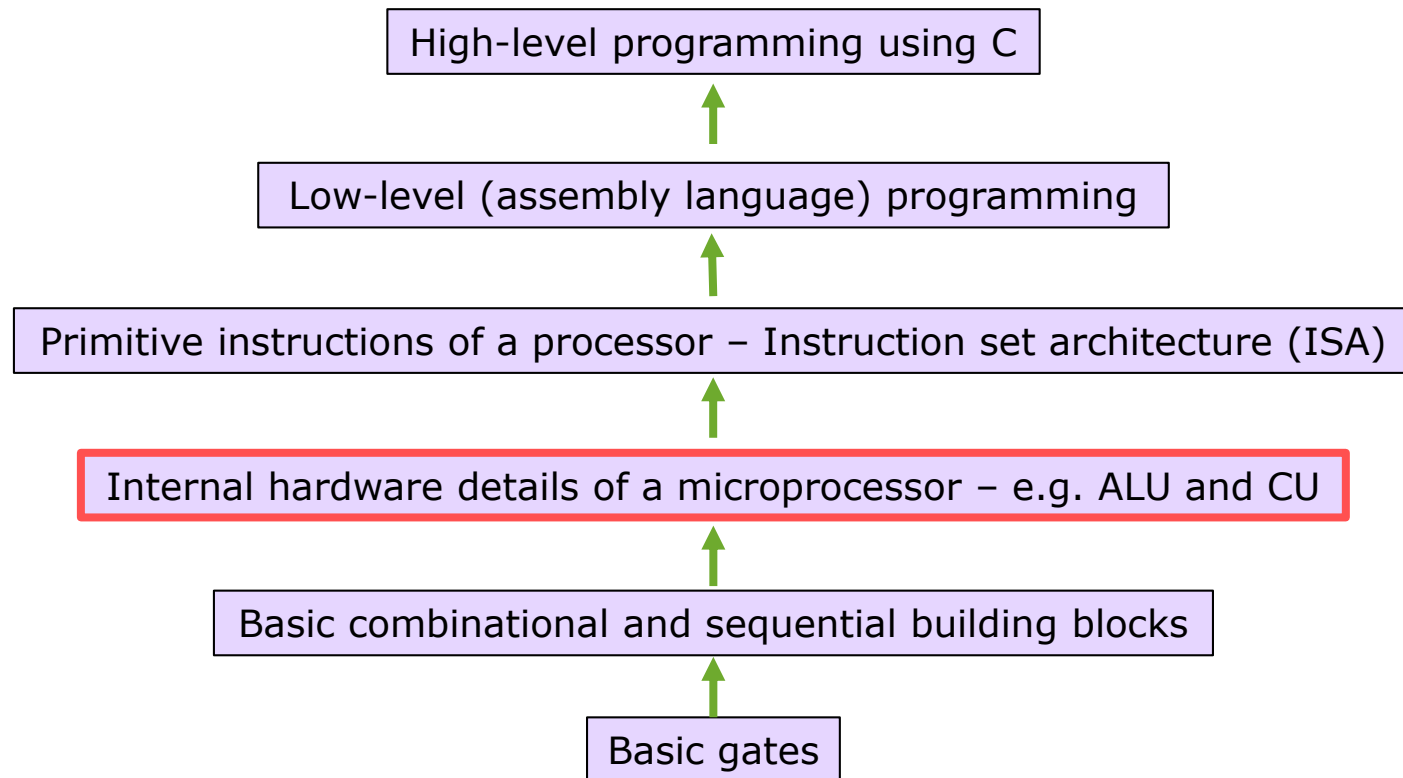

Computer Organisation

- **Simplified** view:

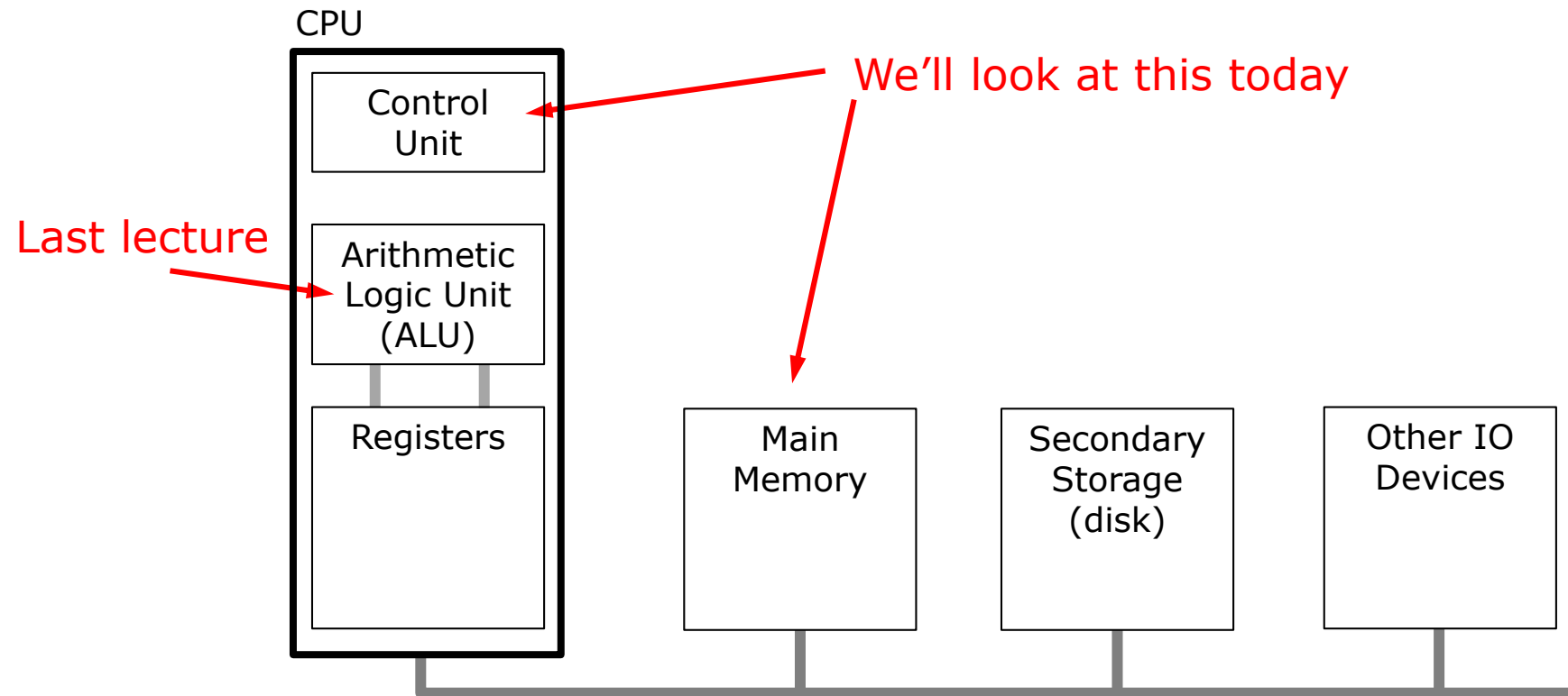


Computer Memory

- Computers need memory to
 - Store temporary results
 - Store programs
 - Remember settings when power off
- Many different types
 - Volatile vs. non-volatile
 - Random access
 - Read-only
 - Static vs. dynamic
 - Primary vs. secondary
- We'll return to different types of memory in more detail in week 12


Memory Organisation

 - Computer memory is conceptually a set of addressable cells
 - Cells usually 8-bits wide (i.e. hold one byte)
 - Various cell widths have been used in past




- Next slide shows 4 x 3 memory
 - 4 addresses, 3-bit cells

4 x 3 Memory

 

Fetch-Decode-Execute Cycle

 - Control Unit operates in continuous cycle on the datapath:



Fetch: fetch an instruction from memory and bring it inside the CPU. Two special purpose registers involved – PC and IR


Decode: resolve the operation (opcode) and operands (variables)

Execute: Control signals are issued and operation takes place in data path

Fetch-Decode-Execute Cycle (cont.)

1. **Fetch** next instruction from memory into Instruction Register (**IR**)
2. Change Program Counter (**PC**) to point to the next instruction
3. Determine type of (**decode**) instruction just fetched (i.e. look at OpCode)
4. **Execute** the instruction
5. Return to step 1


Fetch-Decode-Execute: Data Path

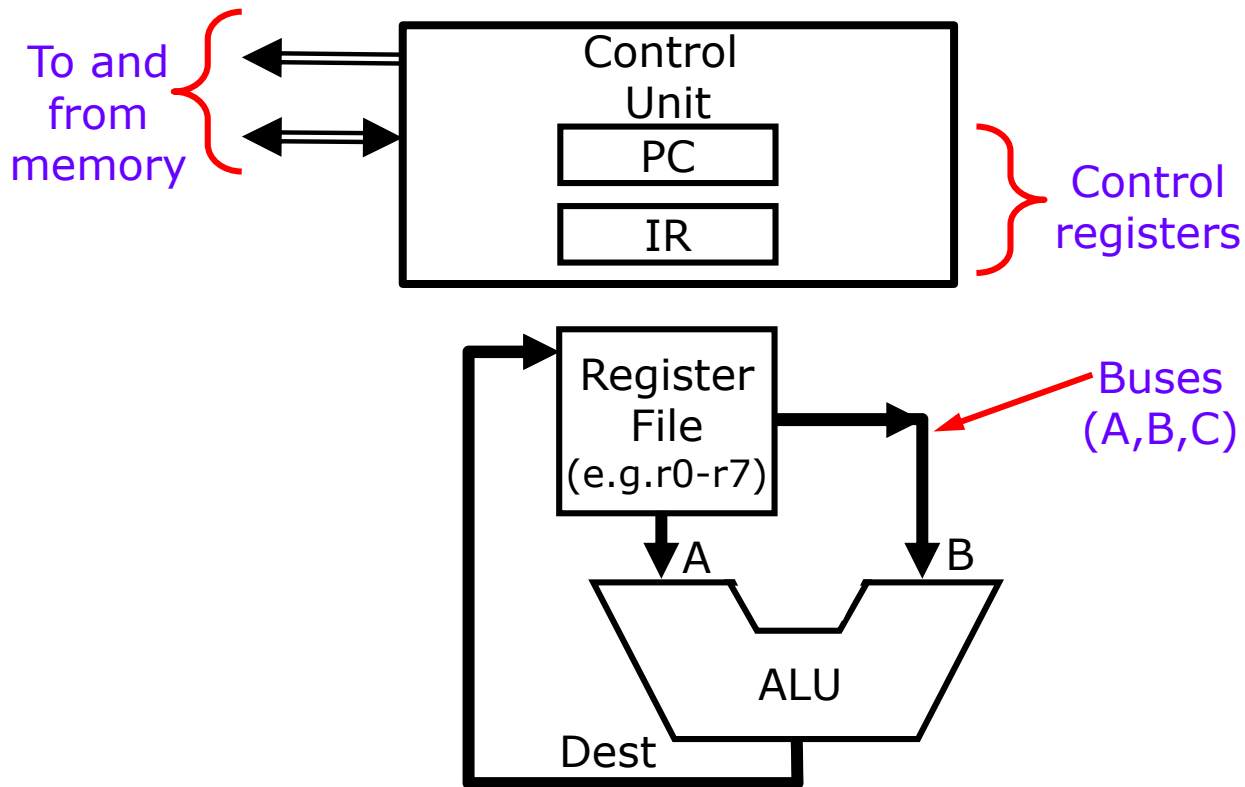


How do we control this?

Specifically

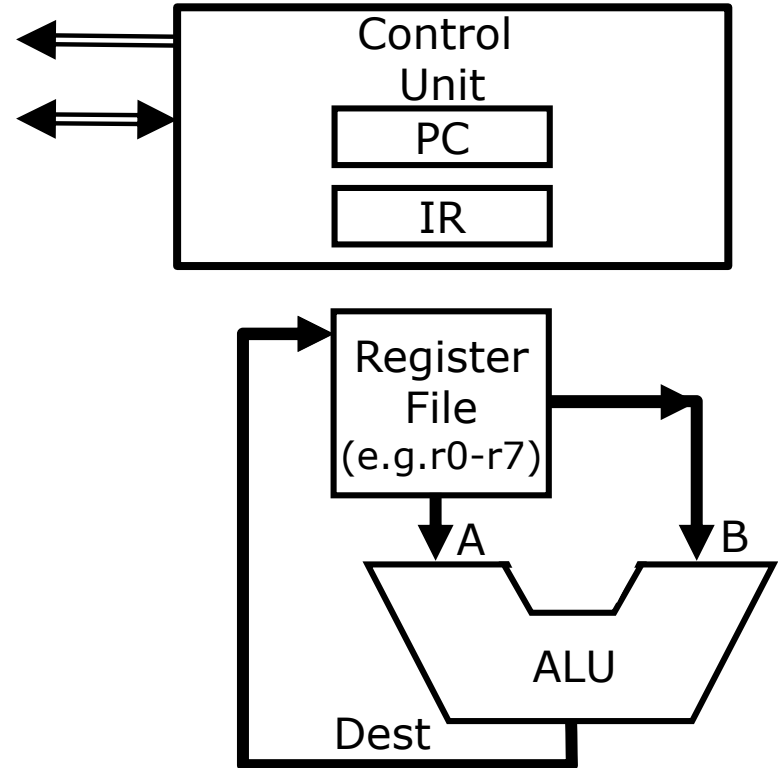- How do we tell the ALU what to do?
- How do we choose what register values are placed on the A and B buses?
- How do we choose which register receives the result from the Destination bus?
- How do we know when to read or write memory?



Control Signals

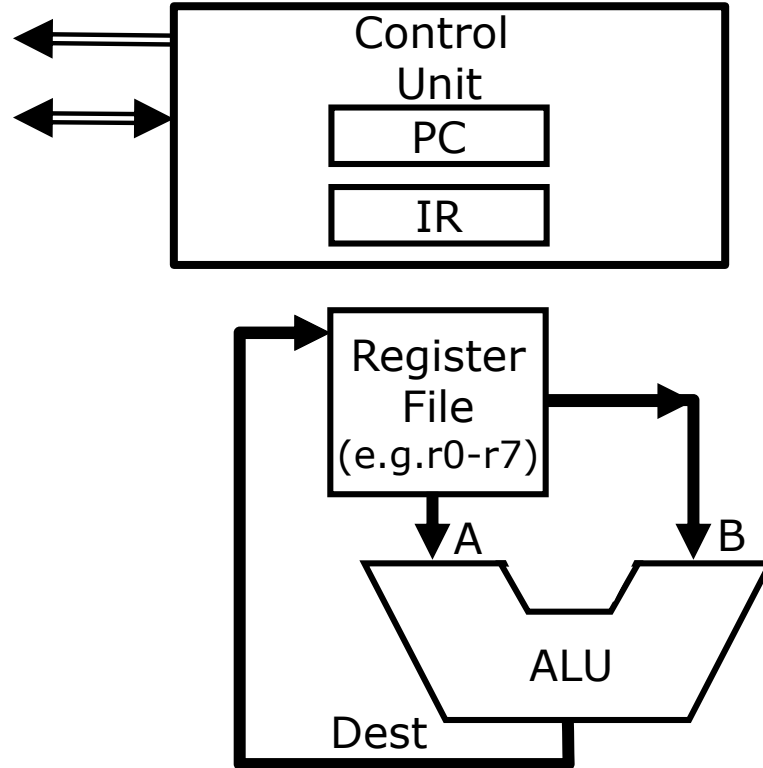

(Figure to be annotated in class.)

Control Unit

- Control signals come from the **control unit**
- Control unit must generate the control signals in the right order for a given instruction
 - Instruction determined by contents of the Instruction Register (IR)


Data influencing control

- Need to know more than what's in the instruction register
- Control unit can't operate without knowing something about the data
 - e.g. if a for-loop variable is supposed to go from 10 to 0, how does the control unit know when it gets there?

→ Status Register

- Determined by ALU operations
- Stores status of last ALU operation

ALU Status

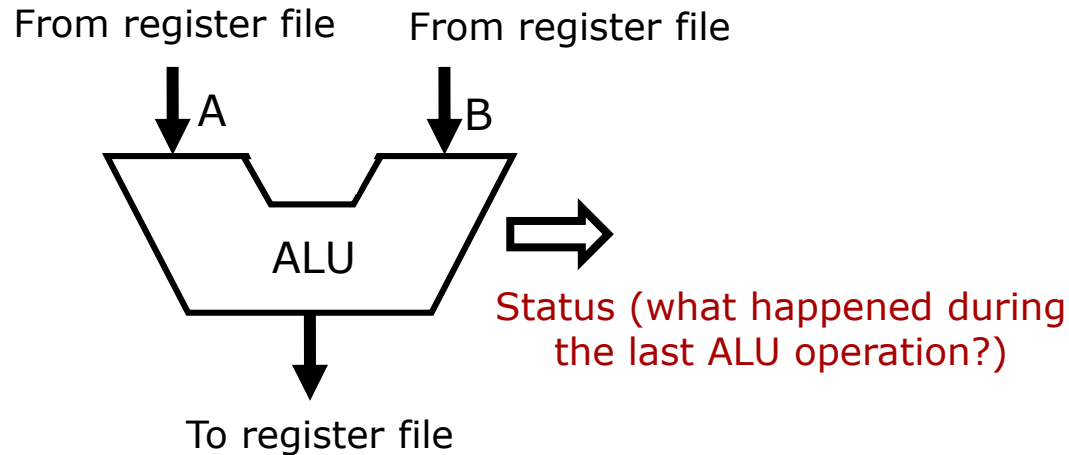

ALU status flags:

Z – Zero flag

V – Overflow flag

C – Carry flag

N – Negative flag

Typically stored in a special purpose register called STATUS register which is available to control unit.

(Figure to be annotated in class.)

Status Register

- Typically includes
 - **Z** – zero bit – was the last result 0?
 - **V** – overflow bit – did the last addition/subtraction operation overflow (assuming it was a two's complement operation)?
 - **C** – carry bit – was a carry out generated?
 - **N** – negative bit – was the result negative if considered as two's complement (i.e. what's the sign bit)?

Example

- What values are in the status register after operation $8_{10} - 9_{10}$ for a 5 bit ALU?

What values are in the status register after operation $110 + 010$ (binary addition) for a 3-bit ALU?

14%1. **Z=0 V=0 C=1 N=1**

14%2. **Z=0 V=1 C=1 N=0**

14%3. **Z=0 V=1 C=0 N=1**


14%4. **Z=1 V=0 C=1 N=0**

14%5. **Z=1 V=1 C=0 N=0**

14%6. **Z=1 V=0 C=0 N=0**

14%7. **Z=1 V=1 C=1 N=0**

Control Unit

 

(Figure to be annotated in class.)