

CSSE2010/CSSE7201

Lecture 5

Flip-flops

School of Information Technology and Electrical Engineering
The University of Queensland

Today

- Admin
- Recap from week 2
- Circuits that remember values
 - Flip-flops
 - Latches

Admin


- Weekly quizzes:
 - Quiz 1 – closed – xxx attempts, xx/17 average, xx/17 median
 - Quiz 2 – open now and due Friday 13-Aug 4pm AEST
- Labs:
 - **IN students** – use Logisim to simulate logic circuits and also construct on breadboard if you have borrowed a kit
 - **EX students** – use Logisim to simulate the logic circuits. Start acquiring your Arduino based hardware items required from week 7. Details on Blackboard

Prac Equipment - IN students


- Treat it carefully
- Report damage / missing parts
- Don't use parts you're not familiar with and wait until we get into the relevant prac activity.
- Pay extra attention to the I/O board USB connector when you are using it
- Switch the power off before you build/change circuits
 - Check your wiring before you apply power

Recap from Last Week


4-bit Ripple carry adder

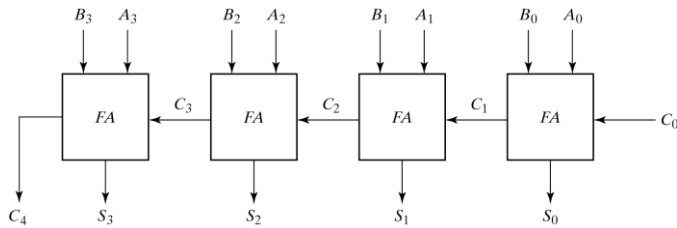


4-bit Adder/subtractor

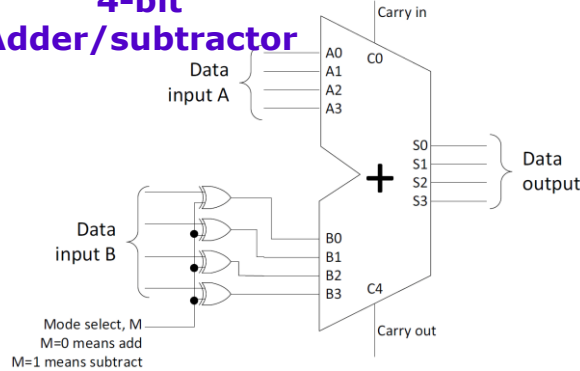

4:1 MUX

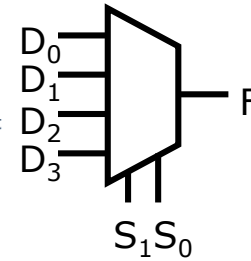

3:8 Decoder

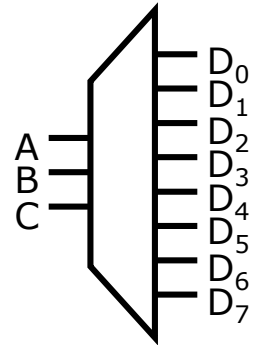

Combinational Logic Circuits – Adder, Adder/subtractor, Multiplexer, Decoder




Logic Gates – NOT, AND, OR, NAND, NOR, XOR, XNOR and Boolean algebra



Binary representations – unsigned, sign-mag, 1's comp, 2's comp, excess-2^{N-1}



Recap from Last Week (cont...)

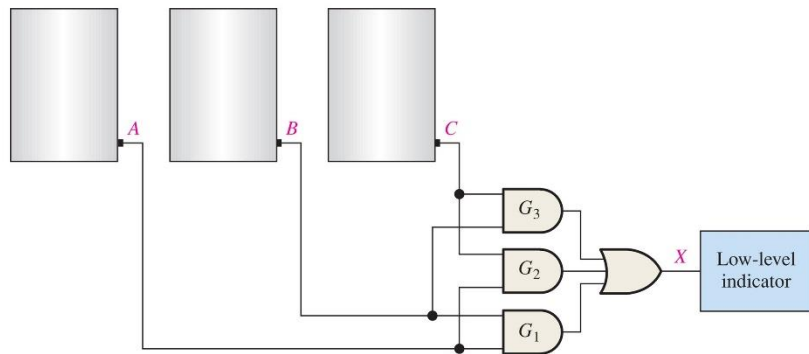

Practical application of the 3-input majority function $X = AB + BC + AC$

When a majority of tanks is low the output will be driven high indicating low-level of water

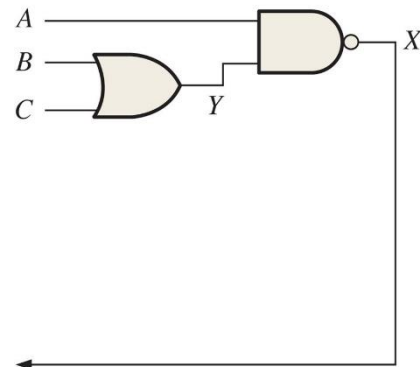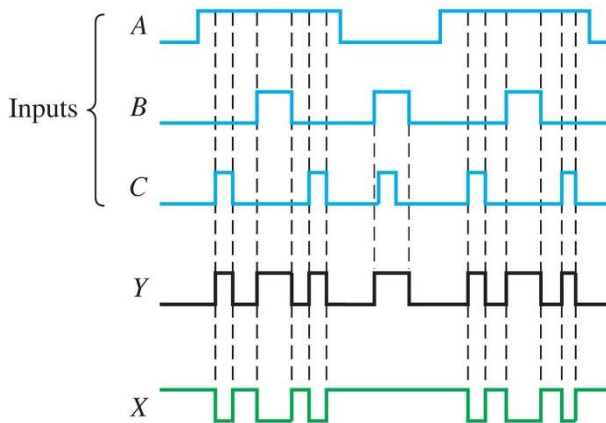Timing diagrams to represent logic circuits




$$X = \overline{A(B + C)} = \overline{AB} + \overline{AC}$$

Clicker Question

Consider the multiplexer shown.
What must the inputs A,B,C,D be
so that the multiplexer output is

$$X = S_1.S_0 + \overline{S_1}.G$$

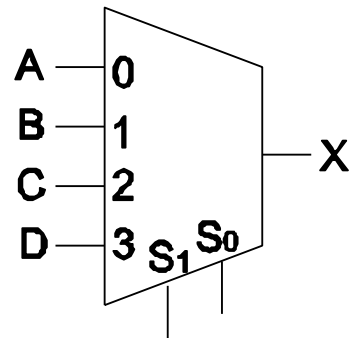

171% A=0, B=0, C=0, D=1

172% A=G, B=G, C=0, D=1

173% A=G, B=0, C=0, D=1

174% A=0, B=G, C=0, D=1

173% None of the above


176% I don't know

Circuits that remember values


- The output of any logic gate or **combinational circuit** is dependent on the **current value of inputs only**
- If an input changes, the output can also change and the previous value is lost forever
- **Sequential circuits**: the current output depends not only on the current inputs but also on the past outputs.
- Circuits with **memory** can remember values, even if the input changes

Memory element: D Flip Flop

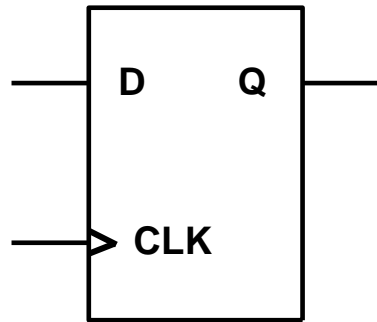- **D** is input
- **Q** is output
- **CLK** (clock) is control input
- How does it work?
 - Q copies the value of D (and remembers it) whenever CLK goes from 0 to 1 (*rising edge*)



D Flip Flop

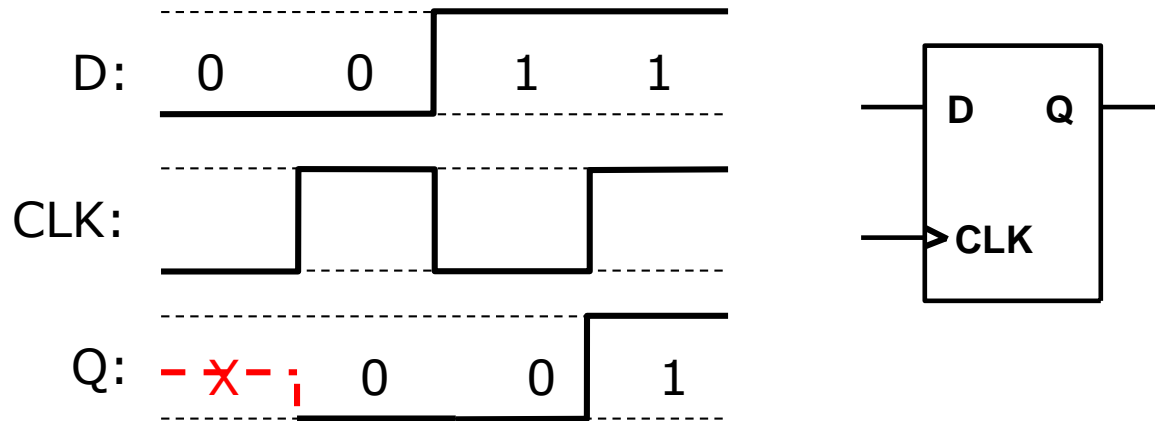

- Remember: Q changes ONLY when clock (CLK) goes from 0 to 1

Characteristic Tables

- **Characteristic table** defines operation of flip-flop in tabular form
 - D flip-flop

D	Q(t+1)
0	0
1	1



Reset

Set

Input

What the output will be on the next clock edge (i.e., CLK goes from 0 to 1).

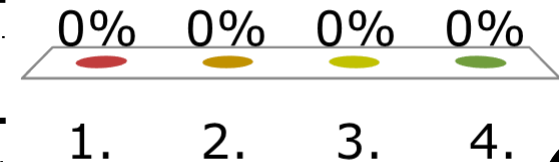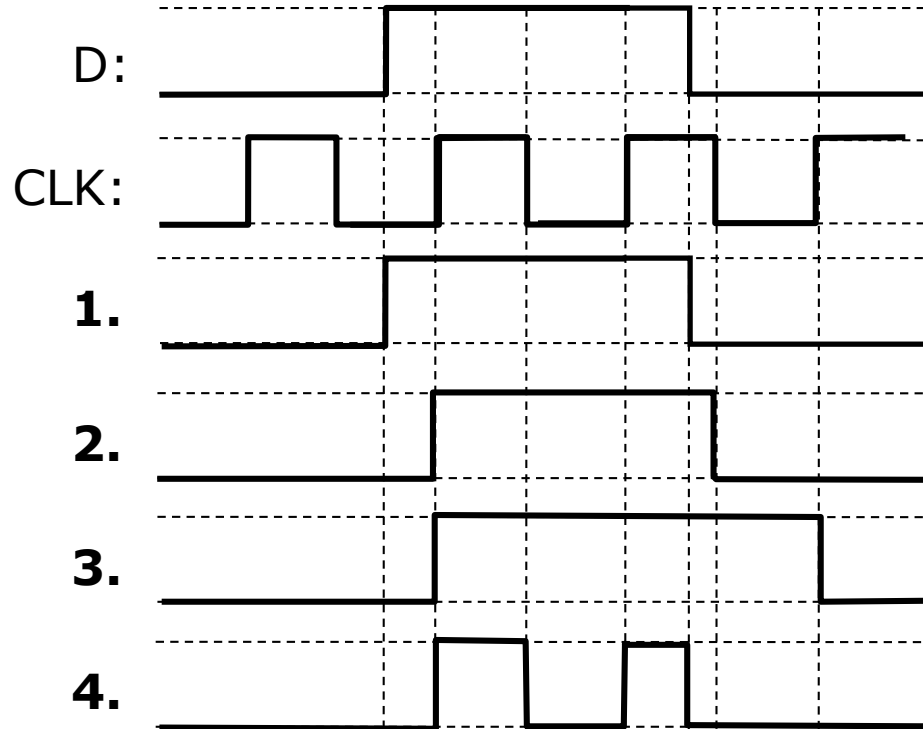Using the D flip-flop presented previously, what is the output waveform for Q?




D Flip-flops

- Summary: D flip-flop remembers either a "1" or "0" – i.e. a single bit. That is the flip-flop remembers the value till the next clock edge, upon which the D input is transferred to output Q.
- So to remember n bits, you will need n D flip-flops
- Definition: A n -bit **register** can be made using n D flip-flops
- There are other types of flip-flops, e.g.
 - JK flip-flops
 - T flip-flops
- Flip-flops can be made out of logic gates

Short Break


- Stand up and stretch

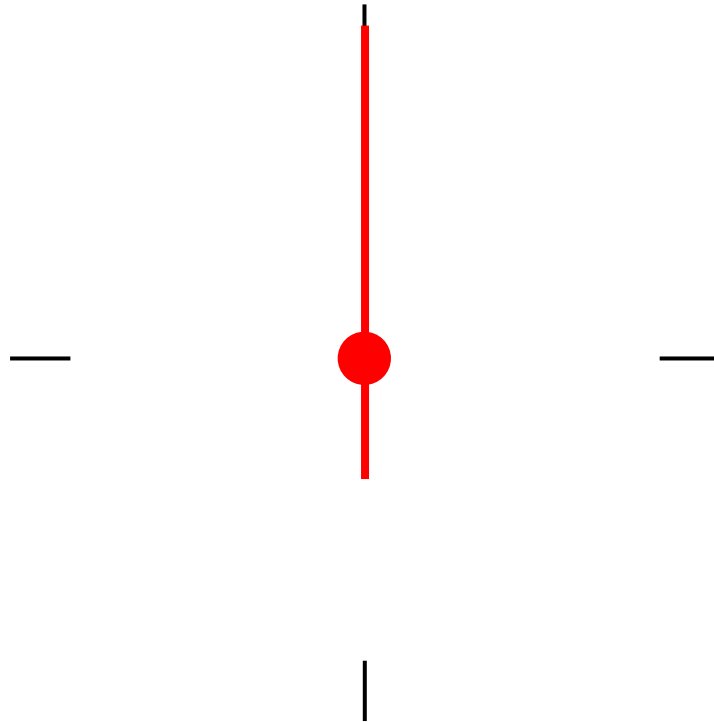

SR Latch – to be completed in class

Try to complete this at home before the lecture. You can assume an initial value for Q output or treat it generic as Q and work out the rest for different combinations of inputs S and R

S	R	Q	\bar{Q}

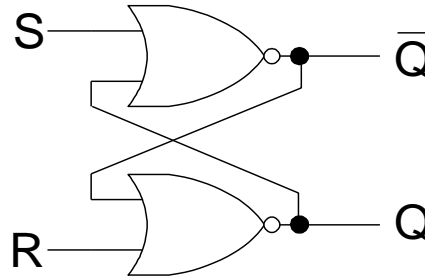

Remember, this is what a NOR gate does

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0


Latches from NAND gates

Homework: Analyse the S-R latch circuit in the previous slide when NOR gates are replaced with NAND gates and complete the truth table.


Flip-Flops vs Latches

- **Latches** are **level triggered** devices – i.e. able to latch the output and respond to changes of logic levels on the inputs
- Latch circuits can be modified such that they become sensitive to an **edge** (i.e. **momentary transitions**) of a control input (i.e. a clock signal)
- Such circuits are called “**flip flops**” and a flip flop can **store 1 bit of information while being sensitive to a clock edge** (i.e., flip flop will change its output only at the clock edges, based on the inputs)
- **Latches are level triggered** devices while **flip flops are edge triggered** devices
- A clock signal has two edges
 - Positive edge – 0 to 1 transition
 - Negative edge – 1 to 0 transition
- There are different types of flip flops
 - **D flip flop – we will only discuss this**
 - JK flip flop – not covered in this course
 - T flip flop – not covered in this course
- So, a D flip flop can be positive edge triggered or negative edge triggered
- **Positive edge triggered D flip flop → Input D is copied to output Q at the positive edge of the clock. In between the clock edges, flip flop is not responsive, thus stores the value.**

A Real D Flip-flop

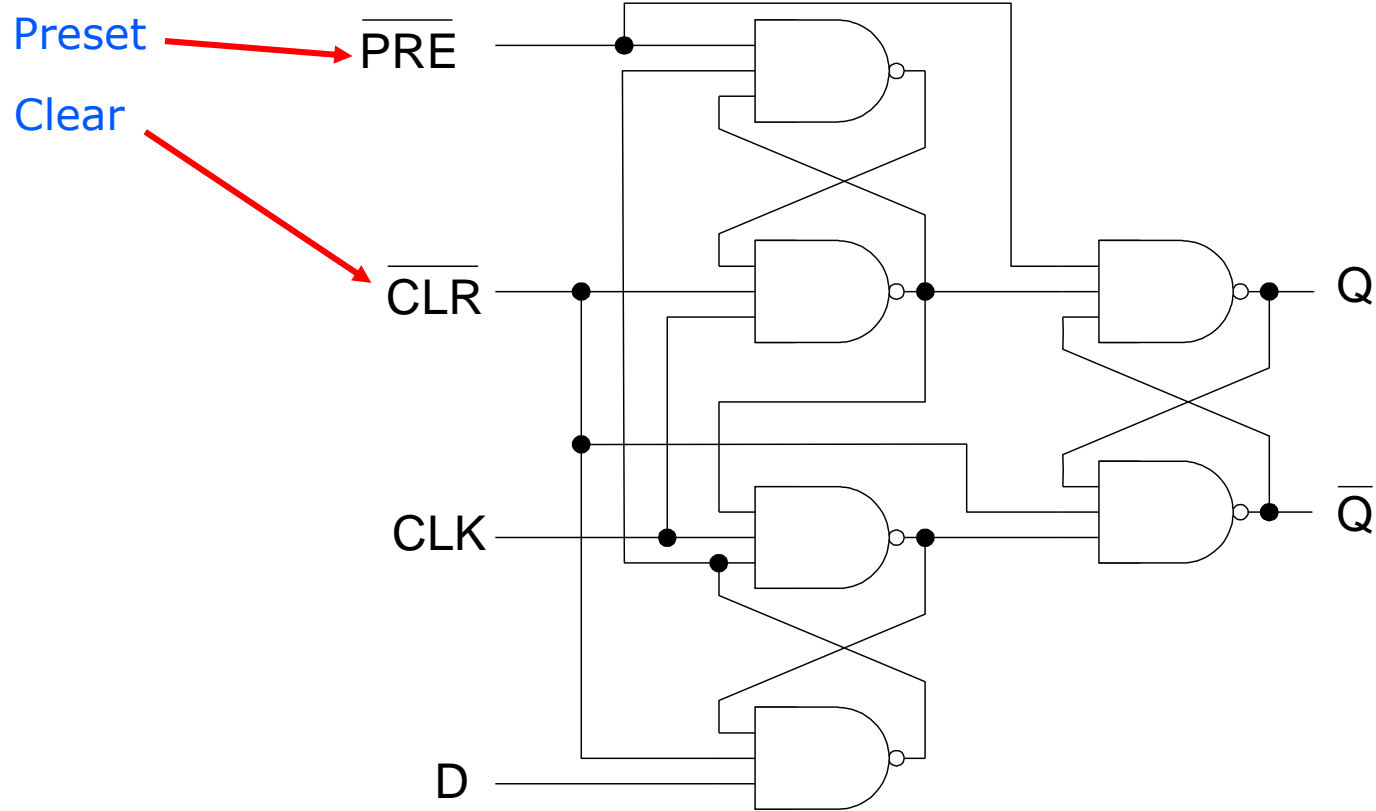

D Latches and Flip-flops – Symbols Used

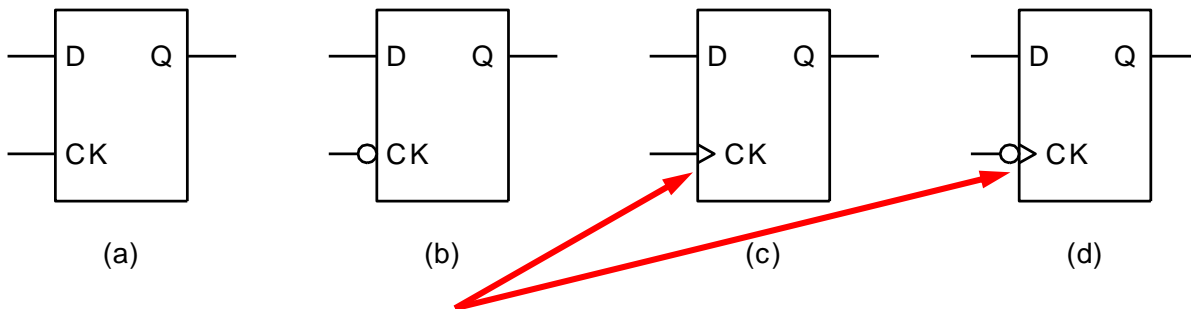


- Triangle indicates edge-triggered (therefore flip-flop)
 - (c) sensitive to rising edge of clock
 - (d) to falling edge
- **State** of a flip-flop is the value stored
- Flip-flops more useful than latches


D Flip-flop Chips

- (a) 74HCT74 chip
(Dual D flip-flop)
- (b) 74HCT273 chip
(Eight D flip-flops)
 - can hold one byte of information (8 bits).

**See device symbols PDF on
Blackboard**

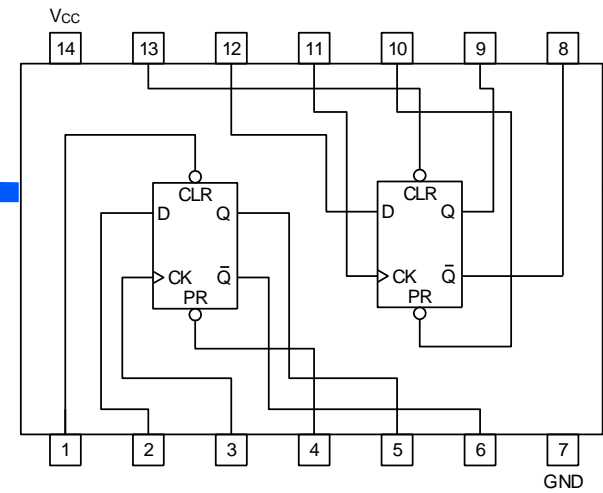

(a)

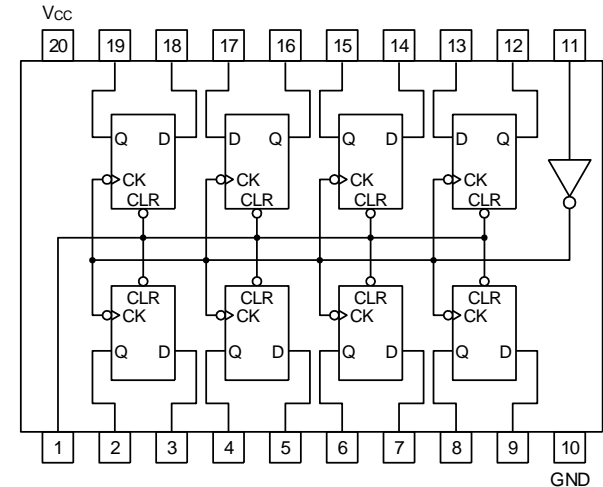


(b)

Combinational vs. Sequential Circuits

- **Combinational** Circuits (last week)

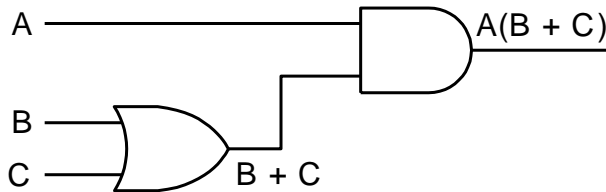- Logic gates only (no flip-flops)
- Output is uniquely determined by the inputs
 - i.e. you'll always get the same output for a given set of inputs
- Example from previously:



- **Sequential** Circuits


- Include flip-flops
- Output determined by current inputs and current **state** (values in the flip-flops)
- Output can only change when clock 'ticks'

Adders
Multiplexers
Decoders
Demultiplexers
Encoders

Counters
Registers


Sequential Circuits

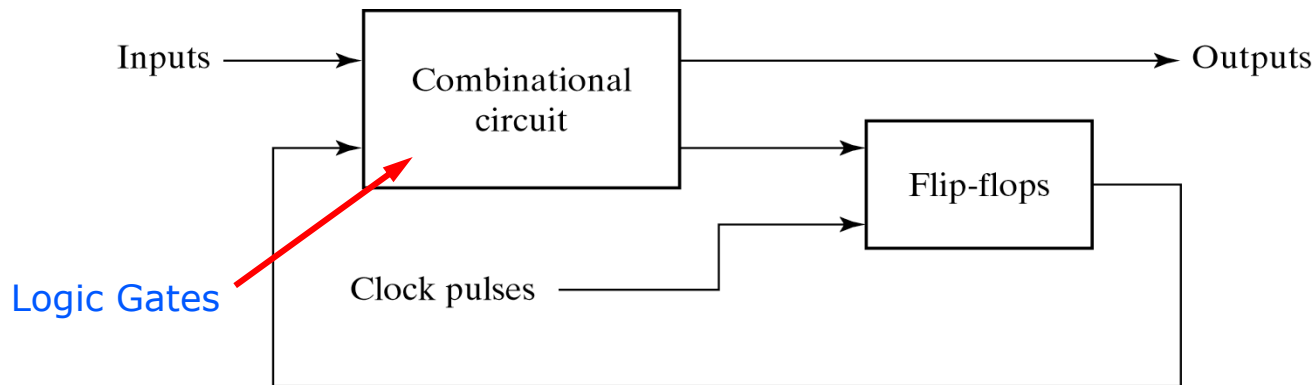- **State** = value stored in flip-flops
- Output depends on input and state
- Next state depends on inputs and state



Synchronous Sequential Circuit

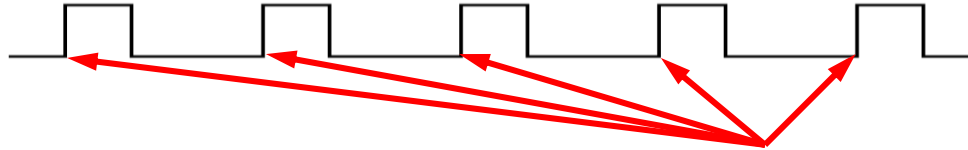
- Storage elements (flip-flops) can only change at discrete instants of time
- Assume
 - We have a clock signal:



- Output of storage elements change only on the edges of control signal
 - (compare with logic gates whose output changes whenever the input changes)

Registers

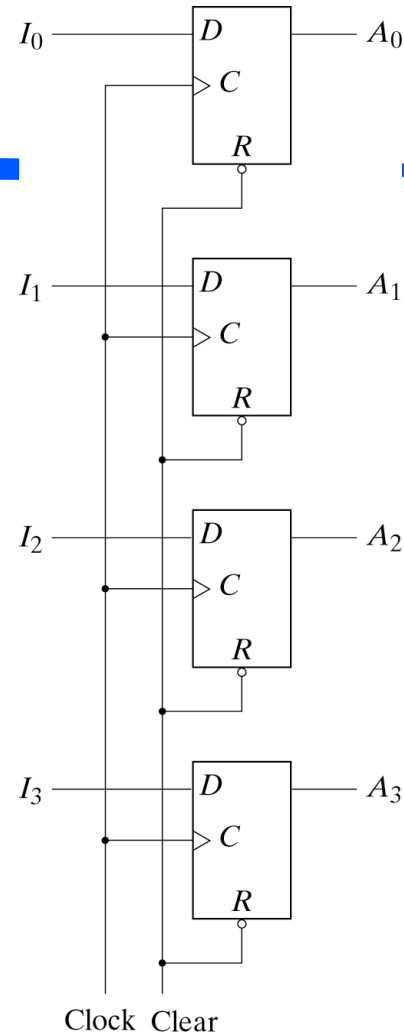- A **register** is a group of flip-flops
 - n -bit register consists of n flip-flops capable of storing n bits
- Example
 - 4-bit register
- A register is a sequential circuit *without* any combinational logic



[Mano,
Digital
Design,
3rd ed.]

Coming up...

- Quiz 2 – due Friday 4pm this week
- Lab 4
 - Combinational Logic
 - Make sure you attempt the preparation task
 - Use logic ICs or Logisim software to test your circuits
- Lab 5
 - Flip-flops
 - Use Logisim software to test the circuits