

CSSE2010/CSSE7201

Lecture 9

From Digital Logic to Processors - ALU

School of Information Technology and Electrical Engineering
The University of Queensland

Outline

- Recap of what's covered so far
- Part of a CPU – mainly ALU

What We've Covered So Far

✓ Binary number representation

- Unsigned/signed
- Two's complement
- Binary addition

✓ Combinational logic circuits

- Adder/subtractors
- MUX/DEMUX
- Encoders/decoders

*Digital
Logic*

✓ Basic logic gates


- NOT/AND/OR/NAND/NOR/XOR/XNOR
- Boolean expressions
- Logic diagrams and schematic diagrams
- Truth tables, timing diagrams

✓ Sequential logic circuits

- Latches and Flip-flops
- Shift registers ✓
- Counters ✓
- State machines ✓

✓ We are now in a position to look at internal hardware details of a microprocessor


Where Are We Heading To?

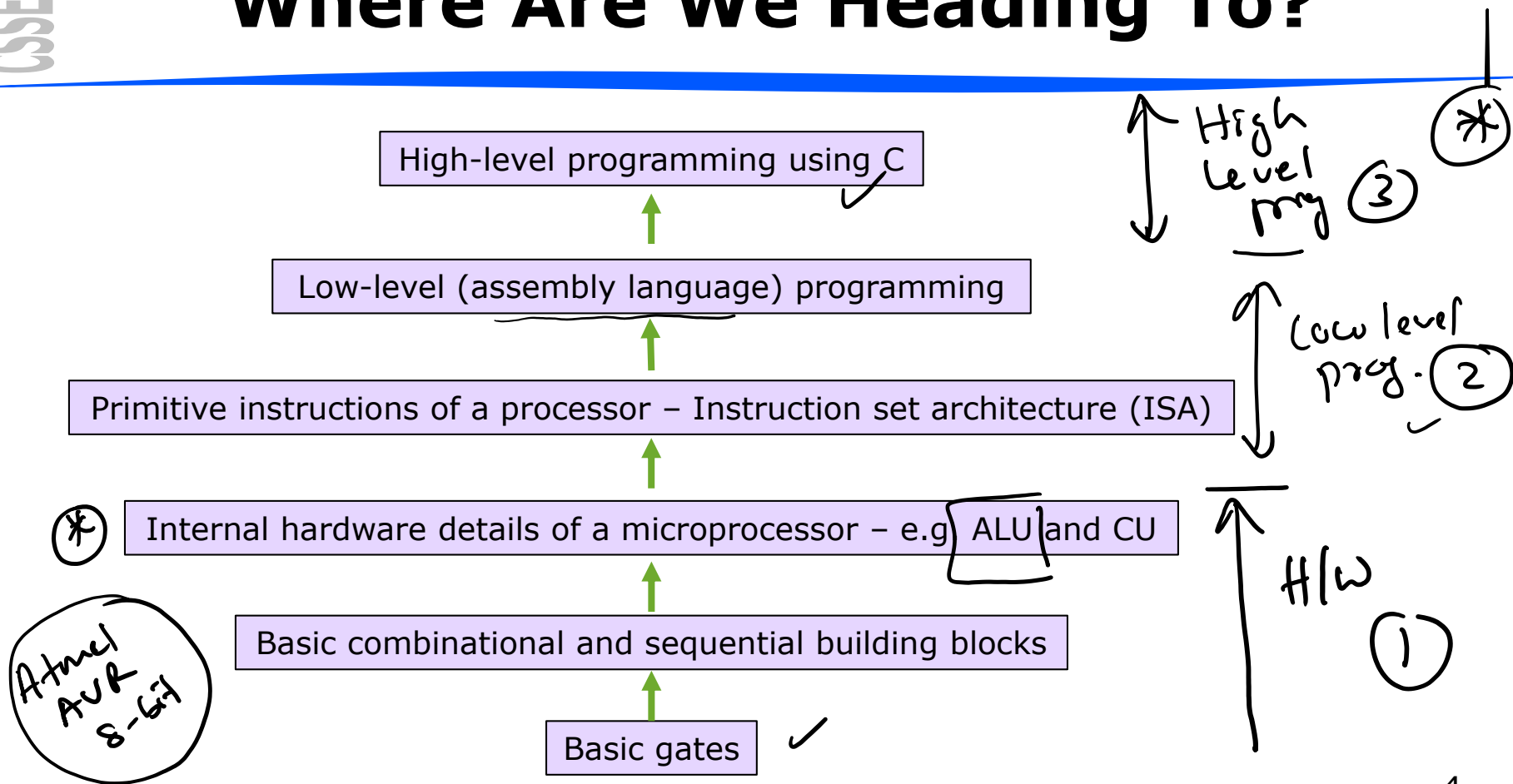

Wk	Day	Date	Lecture (date)		Learning Lab		Assessment due
1	Mon-Tue	26-27 Jul	1	Course Introduction and Binary numbers (26 Jul)		No labs (P2 sessions) on Mon-Tue on week 1	
	Wed-Fri	28-30 Jul	2	Logic gates (28 Jul)	1	Signed number representations	
2	Mon-Tue	2-3 Aug	3	Binary Arithmetic (2 Aug)	2	Logic Gates	Quiz 1 (4pm, 6 Aug)
	Wed-Fri	4-6 Aug	4	Combinational Logic (4 Aug)	3	Binary Arithmetic	
3	Mon-Tue	9-10 Aug	5	Flip flops (9 Aug)	4	Combinational Logic	Quiz 2 (4pm, 13 Aug)
	Wed-Fri	12-13 Aug	6	Sequential Circuits 1 - Shift Registers (11 Aug) Pre-recorded lecture due to public holiday on 11/08/21	5	Flip flops	
4	Mon-Tue	16-17 Aug	7	Sequential Circuits 2 - Counters (16 Aug)	6	Sequential Circuits 1	Quiz 3 (4pm, 20 Aug)
	Wed-Fri	18-20 Aug	8	Sequential Circuits 3 - State Machines (18 Aug)	7	Sequential Circuits 2	
5	Mon-Tue	23-24 Aug	9	From Digital Logic to Processors, ALU (23 Aug)	8	Sequential Circuits 3	Quiz 4 (4pm, 27 Aug)
	Wed-Fri	25-27 Aug	10A	Memory and Control Unit (25 Aug)	Cath-up labs, Assignment 1 release end of week 5		
6	Mon-Tue	30-31 Aug	10B	Introduction to C language (pre-recorded) ✓ Review session for Assignment 1 part 1 (30 Aug) ✗	Assignment 1 working time Part 1: 1-hour timed quiz ✓ Part 2: Digital logic design		Assignment 1 - part 1 due date (4pm, 3 Sep) ✓
	Wed-Fri	01-03 Sep	11	Introduction to AVR and Assembly Language (1 Sep)			
7	Mon-Tue	06-07 Sep	12	Instruction Set Architecture 1 (06 Sep)	9	C Programming	Assignment 1 - part 2 submission (4pm, 6 Sep) ✓ Quiz 5 (4pm, 10 Sep)
	Wed-Fri	08-10 Sep	13	Instruction Set Architecture 2 (08 Sep)	10	Atmel Assembly	
8	Mon-Tue	13-14 Sep	14	C for AVR Microcontroller (13 Sep)	11	AVR Hardware Introduction	Quiz 6 (4pm, 17 Sep)
	Wed-Fri	15-17 Sep	15	Flow Control and AVR Timers (15 Sep)	12	AVR C Programming	
9	Mon-Tue	20-21 Sep	16	Pulse Width Modulation (PWM) (20 Sep)	13	AVR Timers	Quiz 7 (4pm, 24 Sep)
	Wed-Fri	22-24 Sep	17	Interrupts (22 Sep)	14	AVR PWM	

Computer Organisation

- Simplified view:**

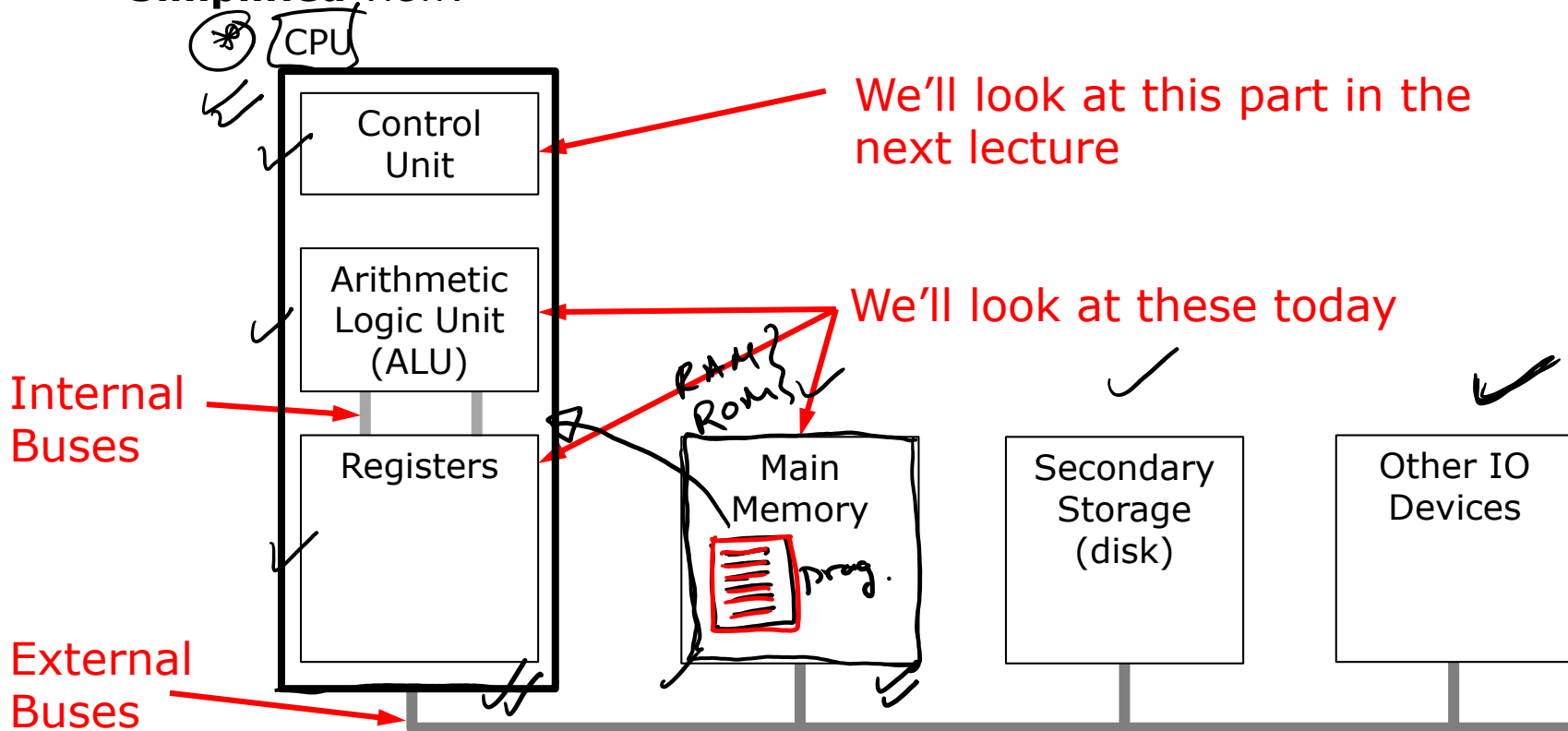

Parts of a CPU

✓ Control Unit

- Fetches instructions from memory, makes the ALU and the registers perform the instruction

→ The topic of next lecture


✓ ALU

- Performs arithmetic and logical operations

✓ Registers

- High speed memory – stores temporary results and control information
- e.g. small CPU may have 8 x 8-bit registers
- large CPU may have 64 x 32-bit registers

MEM
□

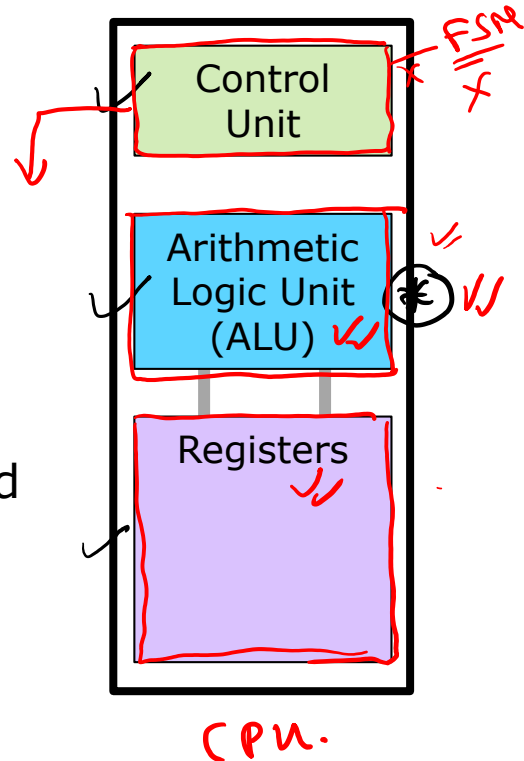


Registers

$$\checkmark \underline{\underline{A + B}}$$

- Registers are temporary storage locations inside the CPU.
- Two types of registers
 - **General Purpose Registers**
 - Contains data to be operated on (e.g. data read from memory), results of operations,
 - Also known as register file. Width is the CPU word size
 - **Special Purpose Registers**
 - Used by the system
 - **Program Counter (PC)** – stores the address of the next instruction to be fetched from the memory
 - **Instruction Register (IR)** – stores the current instruction


Atmel AVR
R0 - R31
 8 bit reg.

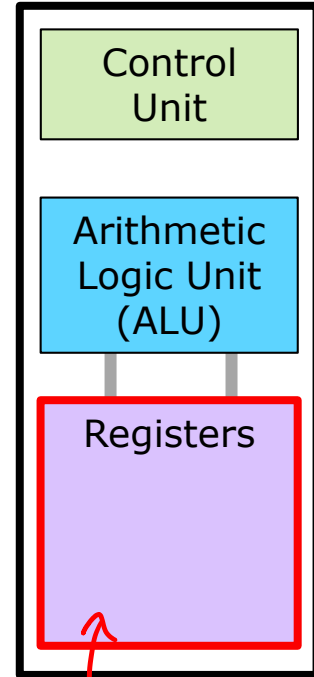

D FFs

Buses


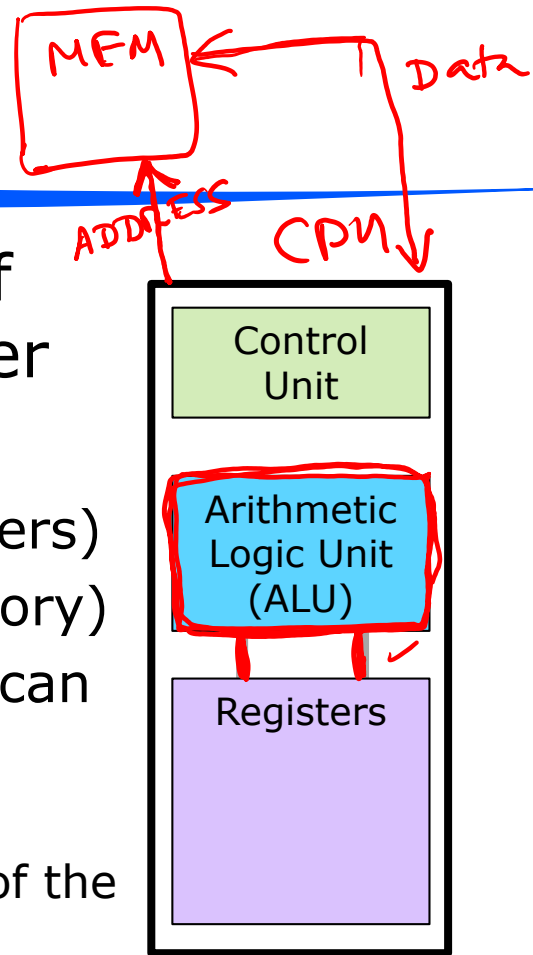
- **Bus** = Common pathway (collection of "wires") connecting parts of a computer
- Characteristics
 - Can be **internal** to CPU (e.g. ALU to registers)
 - Can be **external** to CPU (e.g. CPU to memory)
 - Buses have a **width** – number of bits that can be transferred together over a bus
 - e.g. 1-bit, 8-bits or 32-bits
 - May not always be the same as the word size of the computer



Binary Adder (From Three Weeks Ago)

✓
A₃ A₂ A₁ A₀
B₃ B₂ B₁ B₀

 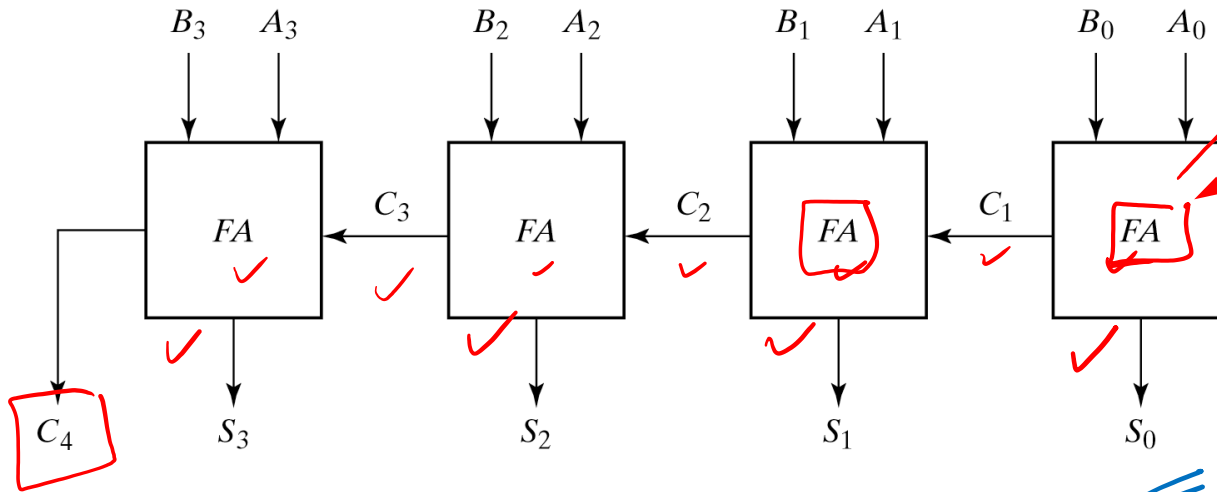- Can cascade full adders to make binary adder
 - Example: for 4 bits...




Bit-slice architecture

- This is a ripple-carry adder

Simplifying Representation

 - To simplify representation we group bits together
- **Bus**
 - collection of wires
- **Bus width**
 - number of bits transferred together (in parallel)
 - 4 in this example



Arithmetic Logic Unit (ALU)


- Does more than adding...
- **Function/control** input indicates the operation that the ALU is to perform, e.g.

Versatile hardware which can perform various operations based on some control inputs

- Addition $\rightarrow A + B$
- Increment (+1) $\rightarrow A + 1, B + 1$
- Subtraction $\rightarrow A - B$
- Bitwise AND $A \text{ and } B$
- Bitwise OR $A \text{ or } B$
- ...

Bitwise Logical op.

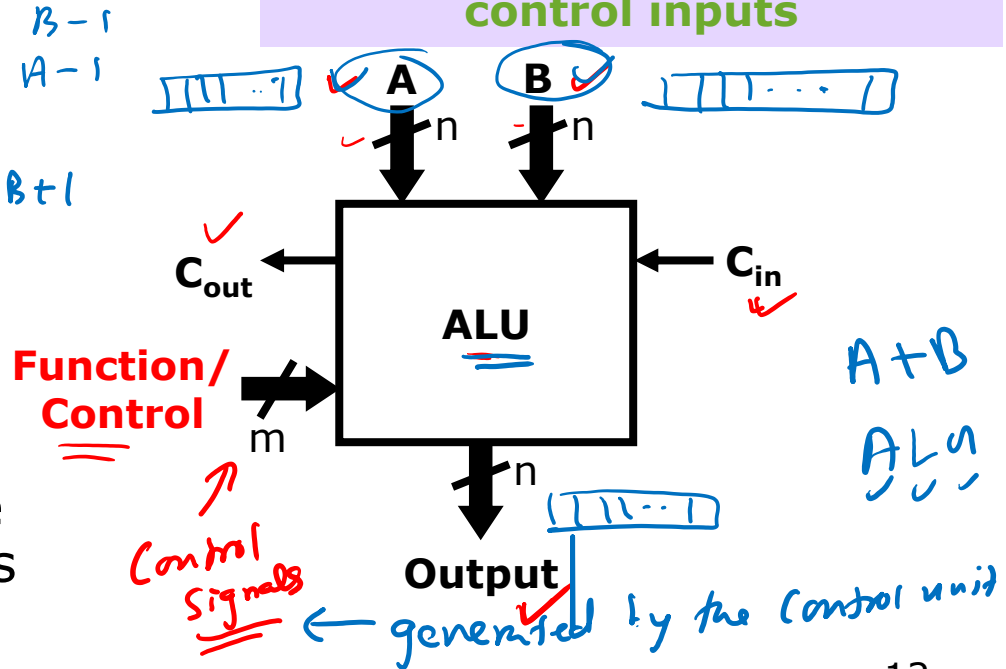
- Like adders, ALUs can be made up from 1-bit slices



Bitwise Operations

- Operate on corresponding bits, e.g. 8 bits

bitwise A and B

 

10011011
 01001011

A and B
 ↑
 bitwise

Clicker question: What is the bitwise OR of 0x74 and 0x85?

11% **A.** 0x04

B. 0x74

9% **C.** 0x85

0% **D.** 0xF1


✓✓ 63% **E.** 0xF5

11% **F.** 0xF9

$A \equiv 01110100$

$B \equiv 10000101$


$\frac{10000101}{11110101}$
F 5 ✓

 


1-bit ALU (bit slice)

- F_1, F_0 select ALU function

- 00 \rightarrow A and B
- 01 \rightarrow invert B
- 10 \rightarrow A or B
- 11 \rightarrow A plus B \rightarrow (A)

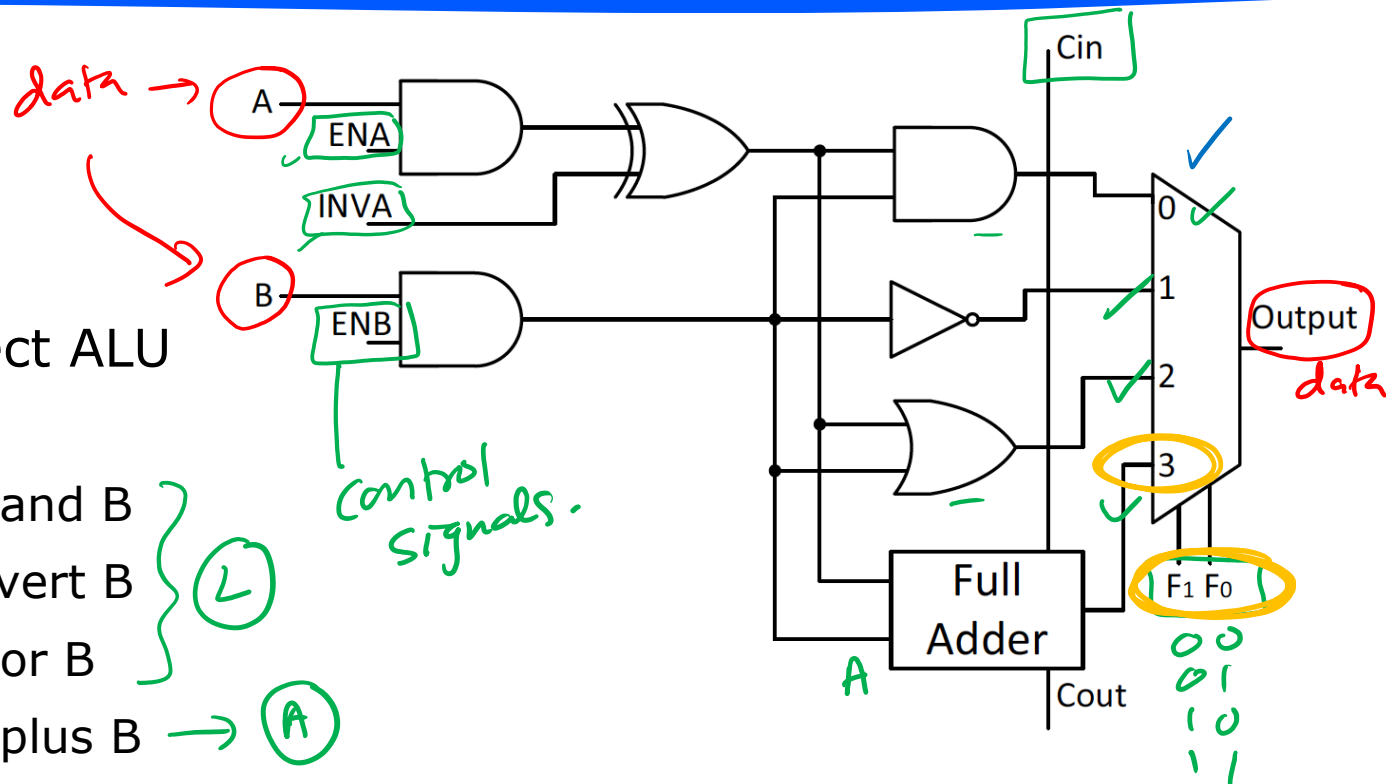

Example 1-bit ALU - Components

 

Data inputs – A, B

Control inputs

- ❑ INVA – invert A- inverts the corresponding input if set to 1
- ❑ ENA, ENB – enable A, enable B – enable the data input if set to 1
- ❑ Also some other function select control inputs (not shown above)


Two levels of control:

- Permutations of data inputs
- Function (operation)

Building the ALU

4 Functions

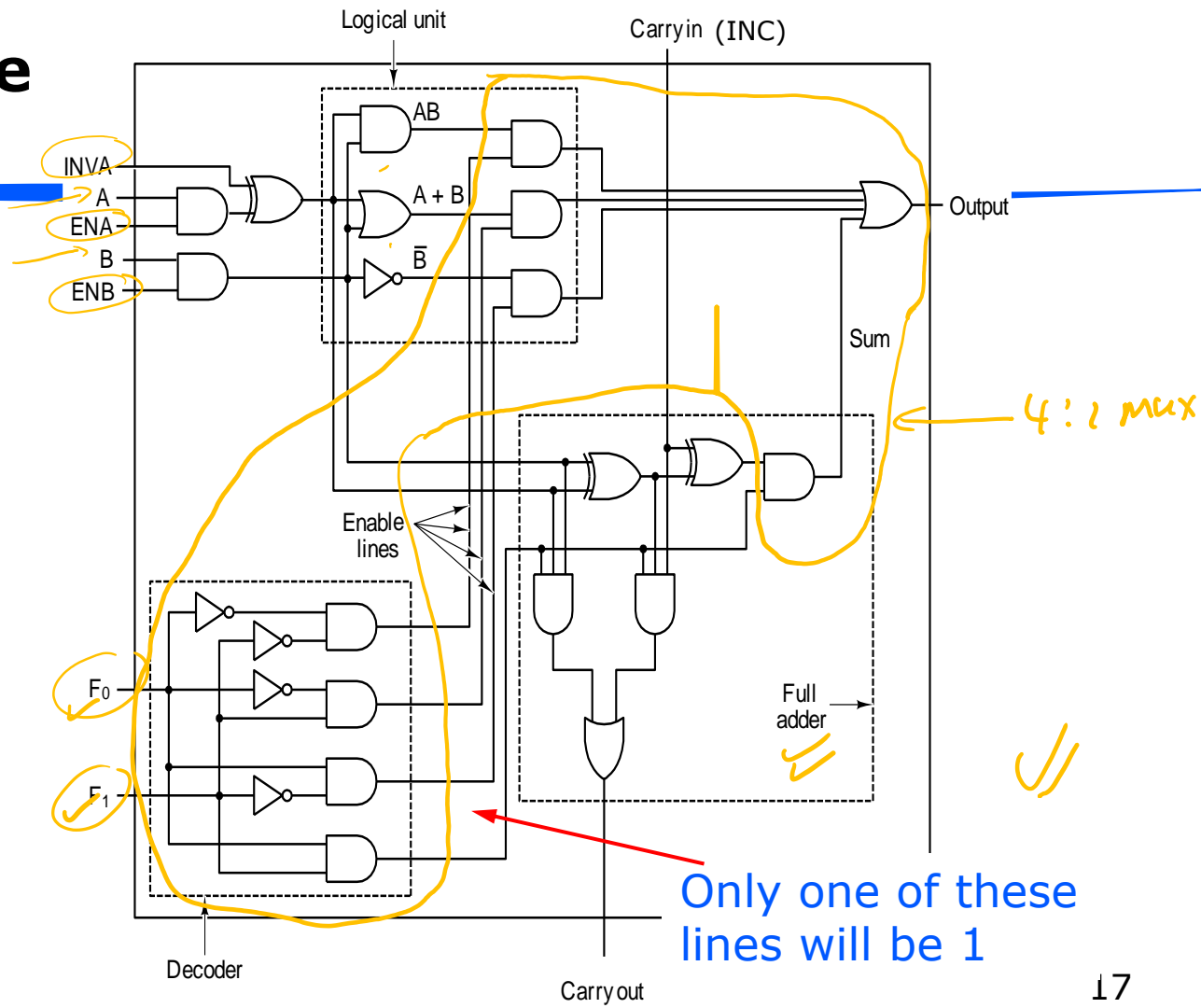
- A and B ✓
- \overline{B} ✓
- A or B ✓
- A plus B ✓




[Figure from
Tanenbaum, "Structured
Computer Organization"]

Arithmetic Logic Unit (ALU)

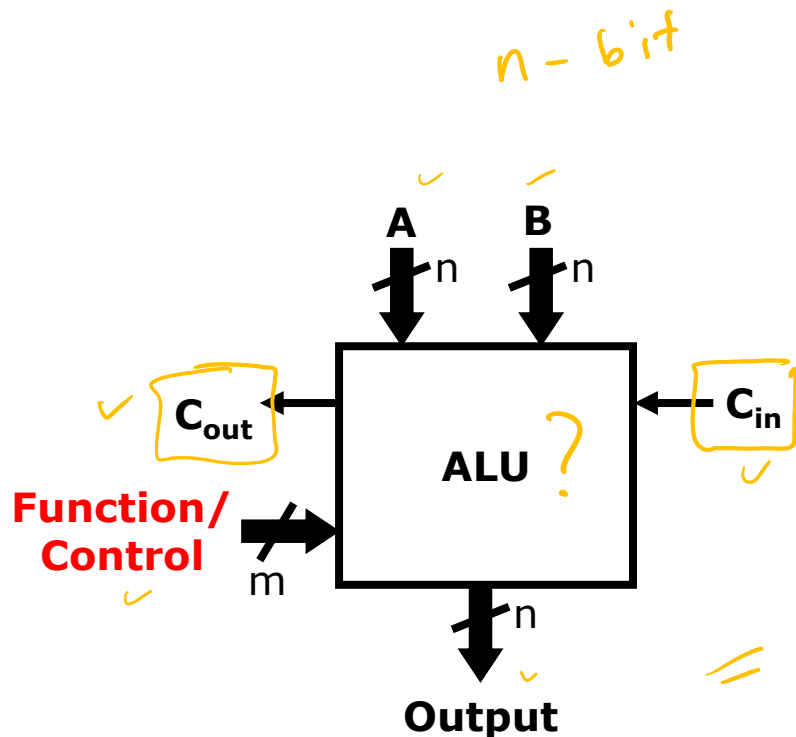- Remember, machine word = n bits
 - (often 8, 16, 32, ...)
- n -bit ALU can be built up of n identical circuits for the individual bit positions



- Example: 8 bits

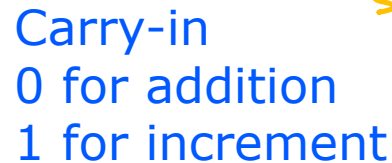

- $$\underline{\underline{A+1}}$$

Example

- How can we calculate $B-A$ using this ALU?

■ i.e. what are the values of $F_1, F_0, ENA, ENB, INVA, INC$

- Note: $B-A = B + (-A)$
 $= B + (\bar{A} + 1)$
 $= B + \bar{A} + 1$

Two's complement negation

$ENA = 1$ ✓
 $INVA = 1$ ✓

$F_1 = 1$
 $F_0 = 1$ }
 $ENB = 1$ ✓
 $INC = 1$ ✓

How can we calculate B+1 (B plus 1) using this ALU? *(Increment B)*


0% A. $F_0=0$ $F_1=1$ $ENA=0$ $ENB=1$ $INVA=1$ $INC=0$

2% B. $F_0=0$ $F_1=1$ $ENA=0$ $ENB=1$ $INVA=0$ $INC=1$


2% C. $F_0=1$ $F_1=1$ $ENA=0$ $ENB=1$ $INVA=1$ $INC=0$

0% D. $F_0=1$ $F_1=1$ $ENA=0$ $ENB=1$ $INVA=1$ $INC=1$

 ✓✓ 96% $F_0=1$ $F_1=1$ $ENA=0$ $ENB=1$ $INVA=0$ $INC=1$ ✓✓




← single bit slice of the ALU

 

Some Useful Combinations of ALU Inputs


F ₁	F ₀	ENA	ENB	INVA	INC	Function
1	0	1	0	0	0	A ✓
1	0	0	1	0	0	B ✓
1	0	1	0	1	0	\bar{A} ✓
0	1	1	1	0	0	\bar{B} ✓
1	1	1	1	0	0	A + B ✓
1	1	1	1	0	1	A + B + 1 ✓
1	1	1	0	0	1	A + 1 ✓
						B + 1 ✓
1	1	1	1	1	1	B - A ✓
1	1	0	1	1	0	B - 1 ✓
1	1	1	0	1	1	- A
0	0	1	1	0	0	A AND B
1	0	1	1	0	0	A OR B
1	0	0	0	0	0	0 ✓
1	1	0	0	0	1	1 ✓
1 ✓	0 ✓	0 ✓	0 ✓	1 ✓	0	- 1 ✓

 

Handwritten red notes and arrows pointing to the table and circuit diagram:

- Arrows pointing to the last row of the table (F₁=1, F₀=0, ENA=0, ENB=0, INVA=1, INC=0, Function=-1).
- Arrows pointing to the output of the Full Adder in the circuit diagram.
- Handwritten binary strings: 0000 0000, 0000 0001, and 1111 1111.
- Handwritten checkmarks (✓) next to several functions in the table.

How the ALU is used ... Data Path

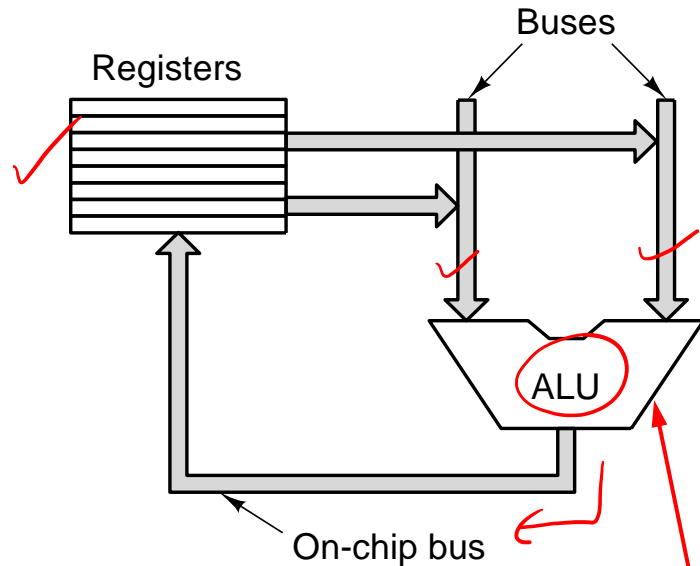

ALU inside a Central Processing Unit (CPU)

Conventional
ALU Symbol

- Operands come from register file
- Result written to register file
- Implements routine instructions such as arithmetic, logical, shift
- Width of registers/buses is the CPU word size

Data Path (Explanation)

- ALU performs operations on data from the register file
 - CPU control unit determines which registers the operands come from and which operation is performed
- Result returned to a register within the register file
 - Could overwrite one of the operands
- Register \Leftrightarrow memory transfers also possible
 - Read: load a register with data from a memory address
 - Write: store a register's contents to a memory address

ALU: In Reality

- Microprocessor may have a number of processing units, e.g.
 - One or more integer processing units
 - Floating point unit(s)
- Units may be capable of operating in parallel