

Welcome!

CSSE2010 / CSSE7201

Learning Lab 2

Logic Gates✓

{ <http://responsewaresg.net>
Session ID: CSSE2010EXT

School of Information Technology and Electrical Engineering
The University of Queensland

Today

Logic Gates

- Lecture revision ✓
- Introduction to Hardware/Simulation ✓ *Logisim*
- Circuit Schematics ✓
- Circuit Building → *Logisim*

What's the truth table for a 2 input XOR gate

<http://responsewaresg.net> ✓

"Exclusive OR"

Session ID: CSSE2010EXT ✓

A.

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

B.

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

C.

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

D.


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

E. I don't know.

n input XOR gate

→ 1 when odd number of 1 inputs

→ "odd function"

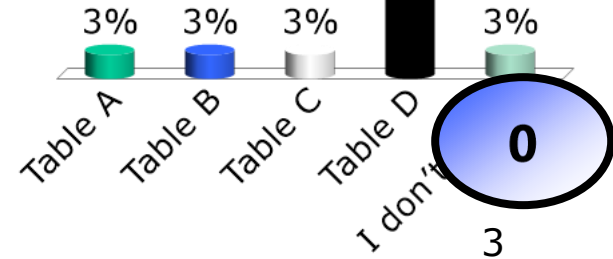


Which of the following circuits is equivalent to ...






$$A \oplus B = AB' + A'B$$

<http://responsewaresg.net>

Session ID: CSSE2010EXT

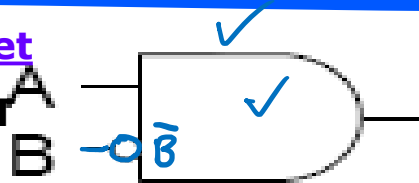

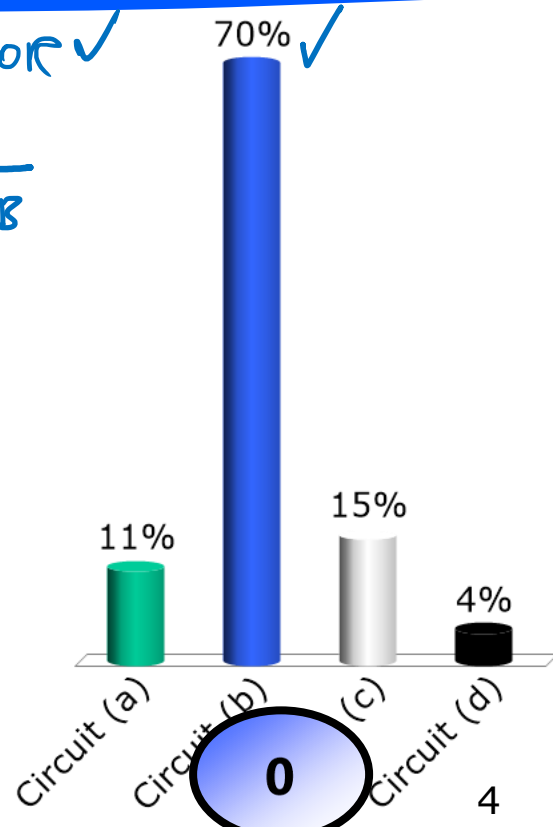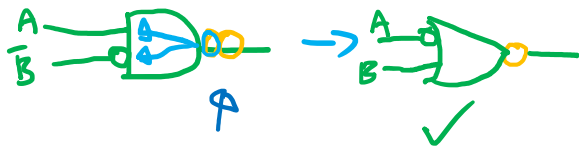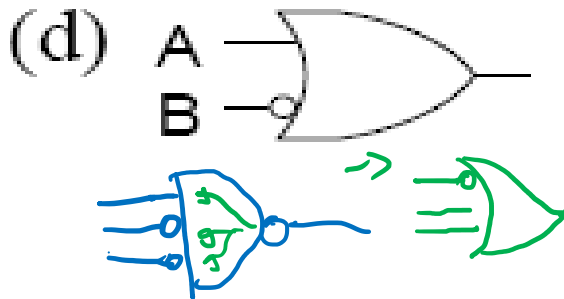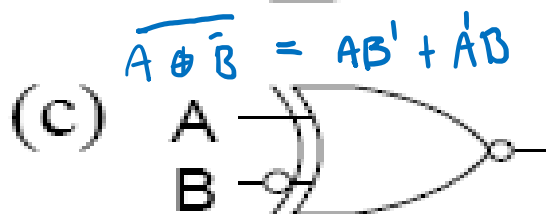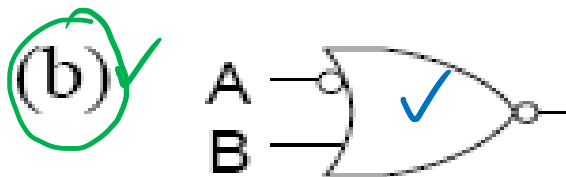AND \leftrightarrow OR ✓
 $X = A \cdot \bar{B}$
 $= \overline{\bar{A} + B}$



$$(A+B)(A+C) = A.A + A.C + B.A + B.C = A + A.B + A.C + B.C = A(1+B+C) + B.C = A(1) + B.C = A+B.C$$

Boolean Identities

(Reminder from lecture)

$$AB = \overline{\overline{A} + \overline{B}}$$

✓✗
✓✗

Name	AND form	OR form
Identity law ✓	$1A = A$ ✓ $1 \times 5 = 5$	$0 + A = A$ ✓ $0 + 5 = 5$
Null law ✓	$0A = 0$ ✓	$1 + A = 1$ ✓✓
Idempotent law ✓	$AA = A$ ✓	$A + A = A$ ✓
Inverse law	$A\overline{A} = 0$ ✓	$A + \overline{A} = 1$ ✓
Commutative law ✓	$AB = BA$ ✓	$A + B = B + A$ ✓
Associative law	$(AB)C = A(BC)$ ✓	$(A + B) + C = A + (B + C)$ ✓
Distributive law	$A + BC = (A + B)(A + C)$ ✓	$A(B + C) = AB + AC$ ✓
Absorption law	$A(A + B) = A$	$A + \underline{AB} = A$ ✓ $A(1+B) = A$
De Morgan's law	$\overline{AB} = \overline{A} + \overline{B}$ ✓ $\overline{AB} \rightarrow \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A}\overline{B} \rightarrow \overline{A} \cdot \overline{B}$

Invert inputs, invert outputs, flip operation AND \leftrightarrow OR

Objective

Main objective today:

Verify the functionality of a simple logic circuit either using a hardware circuit constructed with logic ICs or using simulations in Logisim software


IN students: Use logic chips on your kit or use Logisim if you haven't got your kit yet

EX students: Use Logisim software (it is free)


Hardware Overview

- Breadboard with IO board ✓
 - Be very careful with the USB connector ✗
- USB cable
- Hookup wire ✓
- Logic chip kit ✓
- IC Extractor


Breadboard

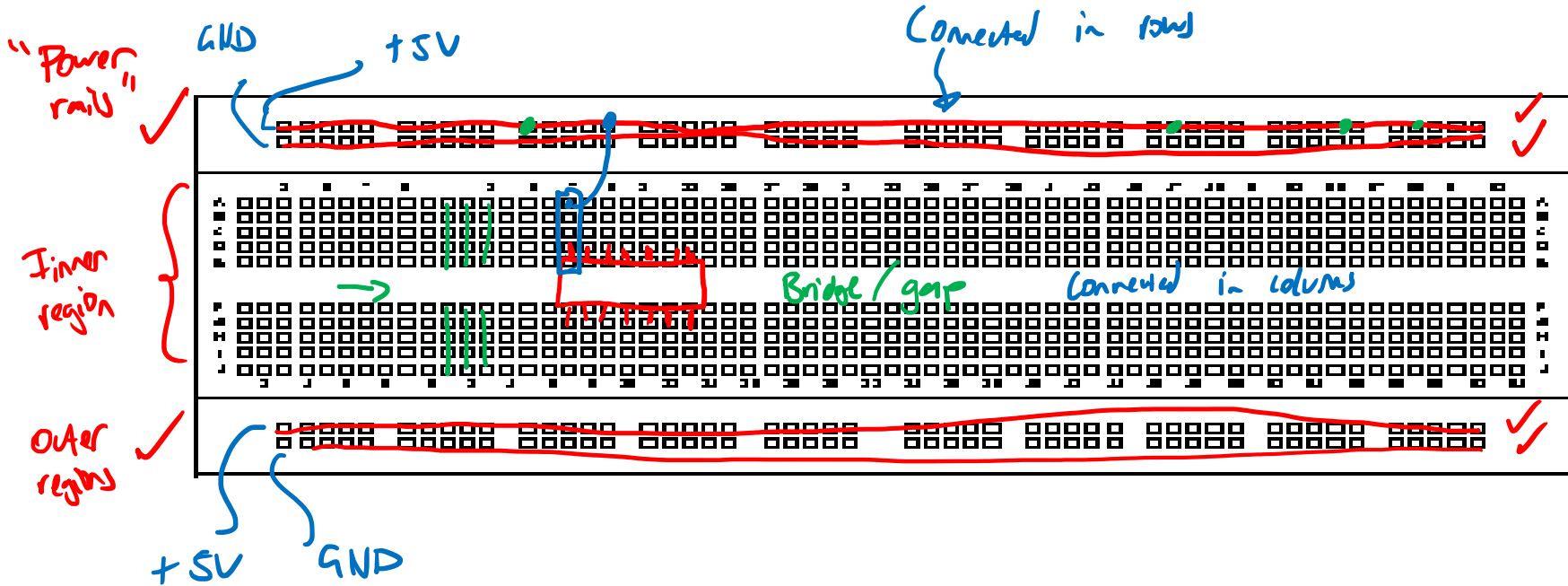

Logic Chips

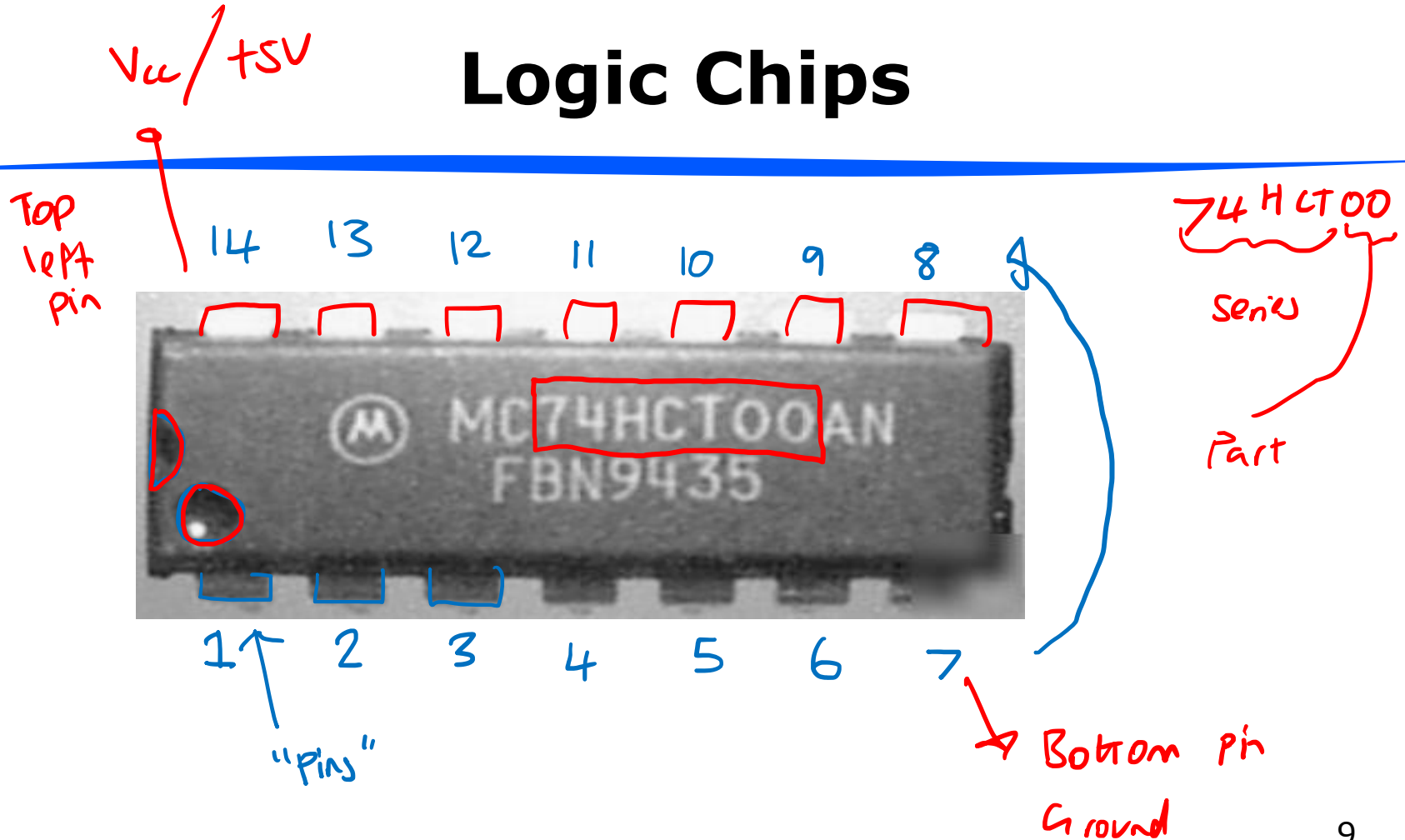


Breadboard with IO board

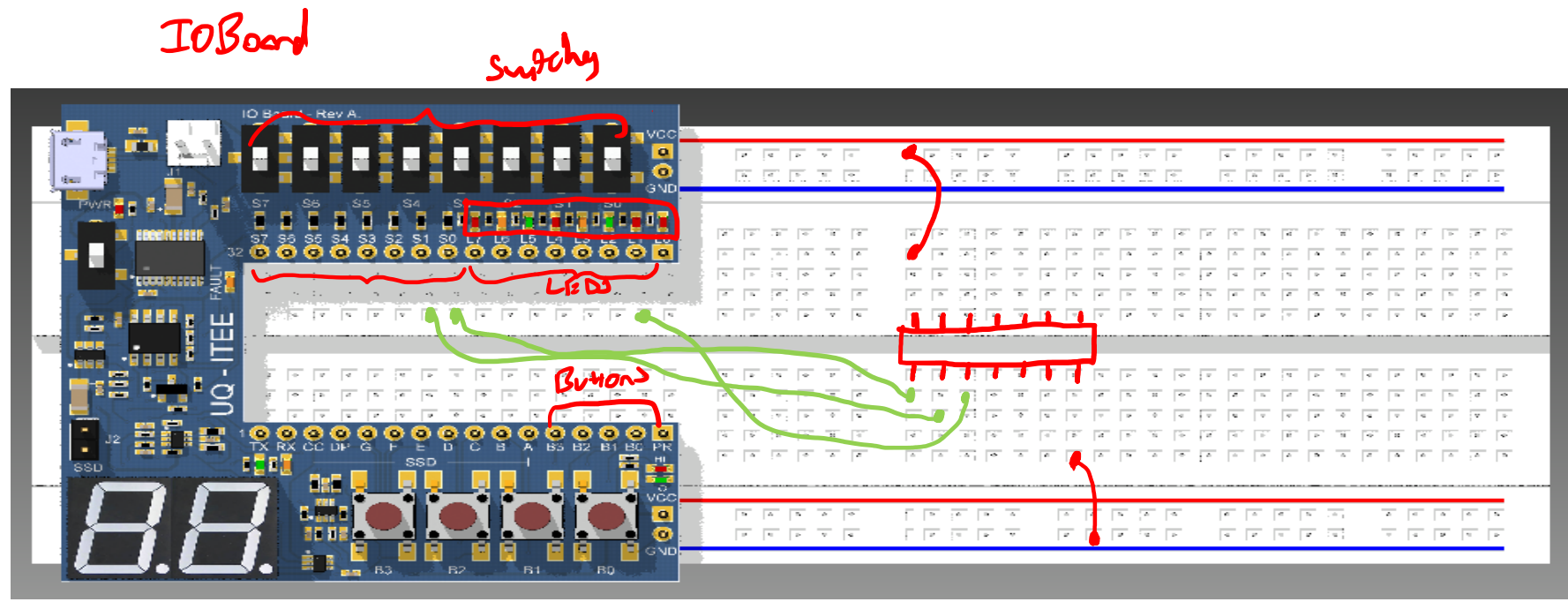


Wire neatly!

- Like this: ✓

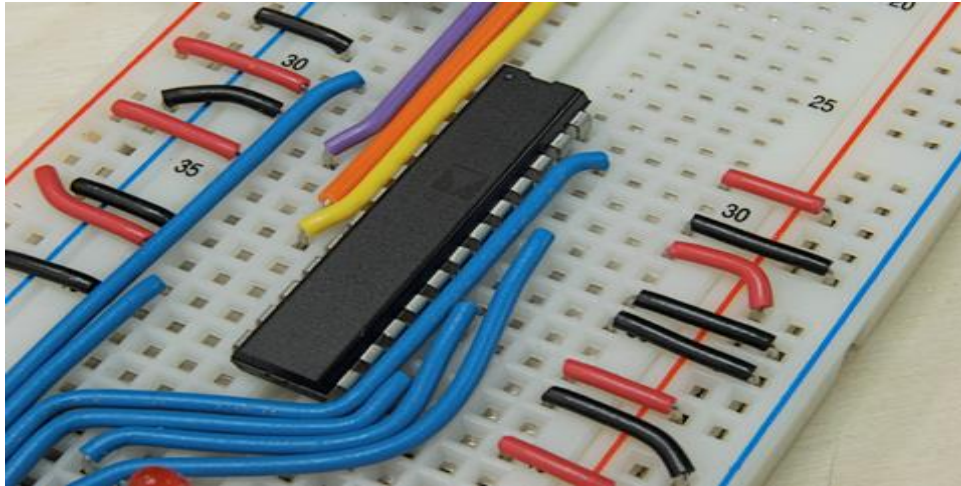

- Not this: ✗

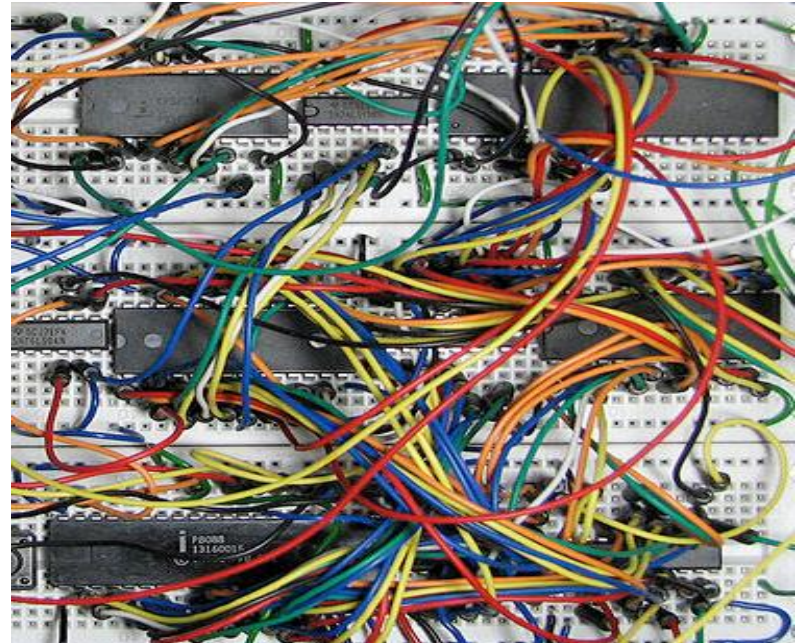


Device Information

- See course Blackboard site for
 - Guide to circuit schematics ✓✓
 - Examples coming up
 - Device pinouts ✓✓

Circuit Schematic Diagram


- More than a logic diagram, a circuit schematic tells you how to **build** the circuit ✓
- You'll need to draw these for pracs and exams ✓
- Schematics include
 - Labelled inputs ✓
 - Labelled outputs ✓
 - Labelled devices (logic chips & IO Board) ✓
 - Logic chips: U1, U2, U3, ...
 - Label gates within a chip (:A, :B, :C) ✓
 - IOBoard: IO1 ✓
 - Power supply connections for logic chips ✓
 - Pin numbers ✓

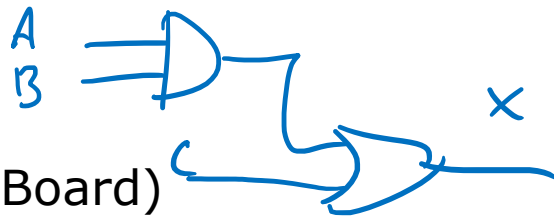

Circuit Schematic Example


Device Type (I/O)

From Blackboard guide

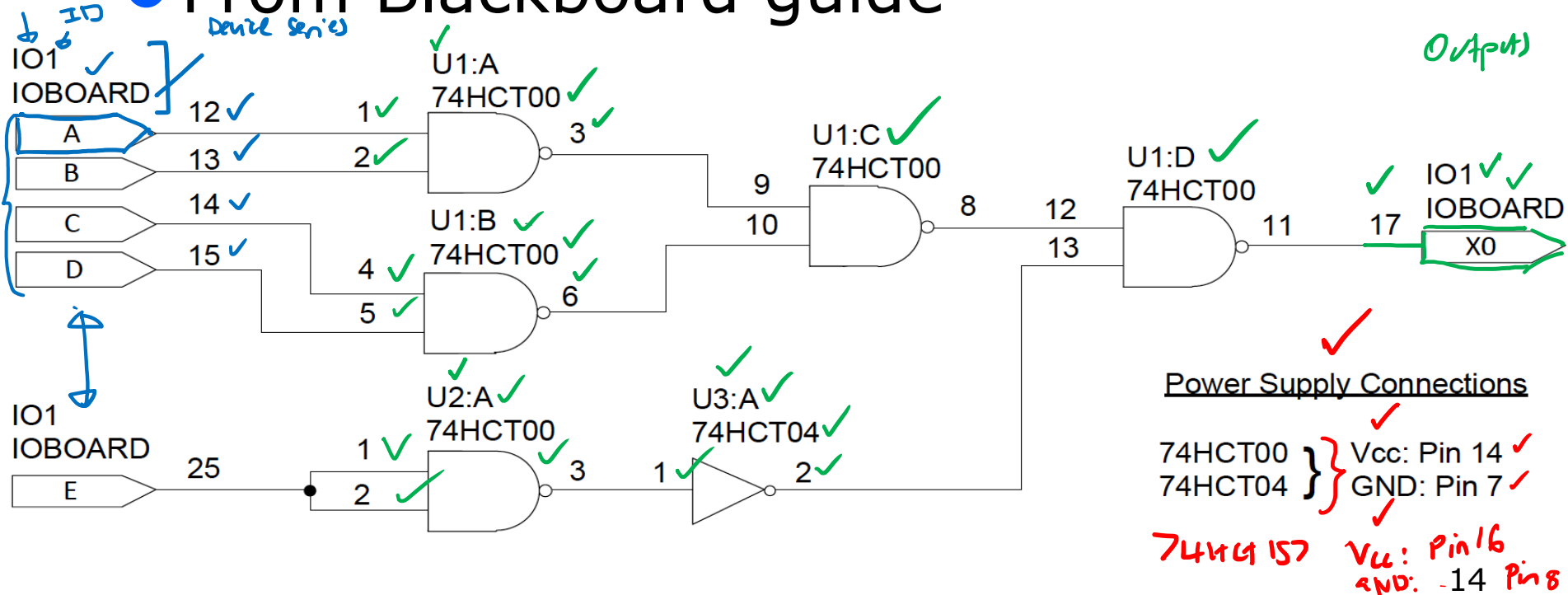


Circuit Schematic Example

- 3 input NOR gate

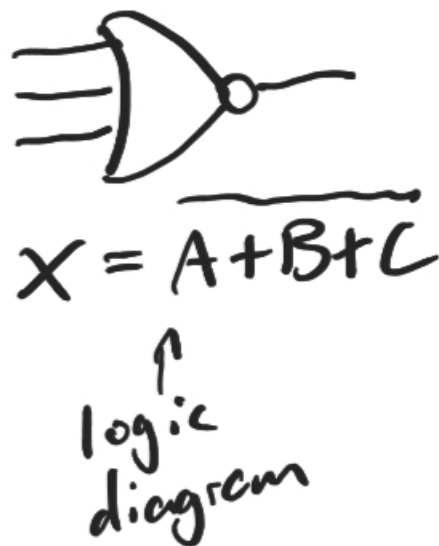

truth table

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

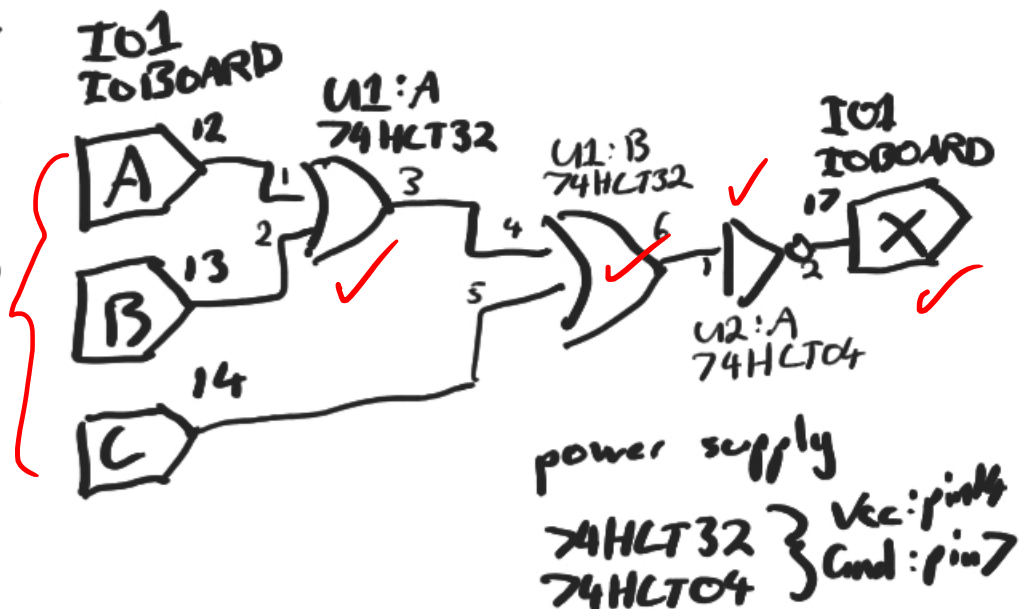

- Now – wire this up or simulate in Logisim software & systematically determine truth table
- If you are testing on hardware, double check your circuit (especially power and ground) before you power it on

$$Z = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \rightarrow Z = \bar{A}BC + \underbrace{ABC}_{\text{replicated terms}} + \underbrace{A\bar{B}C}_{\text{C idempotent law}} + \underbrace{AB\bar{C}}_{\text{C idempotent law}} + \underbrace{ABC}_{\text{C idempotent law}}$$

SOP

3-input Majority Function

Then group terms and apply distributive law


- True if at least two of the inputs (A,B,C) are true

■ $Z = A.B + A.C + B.C$

- This function was shown in lecture 2 (though not in this form)
- Truth Table:

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Logic Diagram:

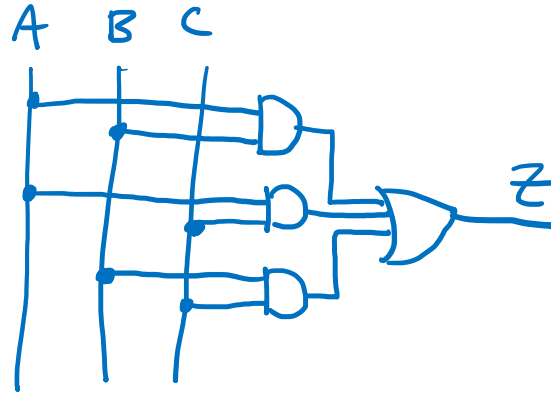

$$Z = (A + B)C + (A + C)B + (B + C)A = AB + AC + BC$$

- Convert to NAND only circuit using Boolean algebra
- Draw circuit schematic - inputs are switches, output is LED
- Wire up circuit/simulate in Logisim and determine truth table
- Repeat using AND and OR gates